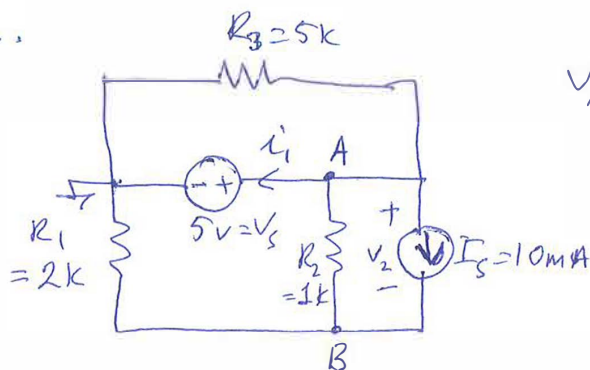


EEE 202 Homework 1 solution

Q1.



$$V_A = 5V$$

$$\frac{V_B - V_A}{R_2} - I_S + \frac{V_B}{R_1} = 0$$

$$\frac{V_B - 5}{1} - 10 + \frac{V_B}{2} = 0$$

$$2V_B - 10 - 20 + V_B = 0$$

$$3V_B = 30$$

$$V_B = 10V$$

To find i_1 :

$$i_1 + \frac{5-10}{1} + 10 + \frac{5}{2} = 0$$

$$i_1 = -6mA$$

∴ power of voltage source = $-6 \times 5 = -30mW < 0$

∴ voltage source is supplying power.


To find v_2 :

$$v_2 = V_A - V_B = 5 - 10 = -5V$$

∴ power of current source = $-5 \times 10 = -50mW < 0$

∴ Current source is supplying power.

Q2. a)

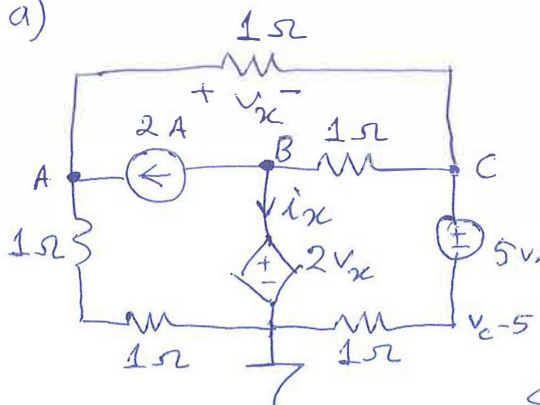

$$A: \frac{V_A - V_C}{1} + \frac{V_A}{1+1} - 2 = 0$$

$$3V_A - 2V_C = 4 \quad (\text{eqn. 1})$$

$$C: \frac{V_C - V_A}{1} + \frac{V_C - V_B}{1} + \frac{V_C - 5}{1} = 0$$

$$3V_C - V_A - V_B = 5$$

$$\text{Since } V_B = 2V_x = 2(V_A - V_C)$$

$$3V_C - V_A - 2(V_A - V_C) = 5$$

$$5V_C - 3V_A = 5 \quad (\text{eqn. 2})$$

Add eqn 1 and eqn 2

$$3V_C = 9 \Rightarrow V_C = 3$$

To find i_x : KCL at B

$$i_x + 2 + \frac{V_B - V_C}{1} = 0$$

$$i_x + 2 + \left(\frac{2}{3} - 3\right) = 0$$

$$i_x = +\frac{1}{3}A$$

To find V_x :


$$V_x = V_A - V_C = \frac{10}{3} - 3 = \frac{1}{3}V = V_x$$

$$\text{From eqn. 1 } V_A = \frac{4 + 2V_C}{3} = \frac{4 + 6}{3} = \frac{10}{3}V = V_A$$

$$V_B = 2V_x = 2(V_A - V_C) = 2\left(\frac{10}{3} - 3\right) = \frac{2}{3}V = V_B$$

$$\frac{1}{3}$$

b)

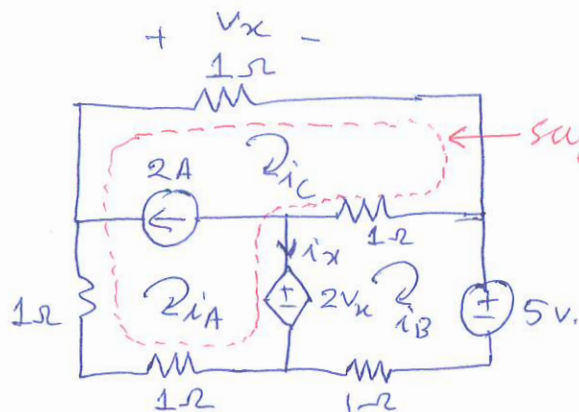

KVL at supermesh

$$i_c \times 1 + (i_c - i_B) \times 1 + 2V_x + i_A \times 1 + i_A \times 1 = 0$$

$$\text{Also } V_x = 1 \times i_c = i_c$$

KVL at mesh B:

$$(i_B - i_c) \times 1 + 5 + i_B \times 1 - 2V_x = 0$$

Since $V_x = i_c$

$$\boxed{2i_B - 3i_c = -5 \text{ eqn. 2}}$$

$$\text{Also } i_c + i_c - i_B + 2i_c + 2i_A = 0$$

$$2i_A - i_B + 4i_c = 0$$

$$\text{Also } i_c - i_A = 2A, \Rightarrow i_A = i_c - 2$$

$$\text{Also } 2(i_c - 2) - i_B + 4i_c = 0$$

$$\boxed{-i_B + 6i_c = 4 \text{ eqn. 1}}$$

Multiply eqn. 2 by 2 and add to eqn. 1.

$$3i_B = -10 + 4 = -6 \Rightarrow \boxed{i_B = -2A}$$


$$\text{From eqn. 1 } i_c = \frac{4 + i_B}{6} = \frac{4 - 2}{6} = \frac{1}{3}A = i_c$$

$$i_A = i_c - 2 = \frac{1}{3} - 2 = \boxed{-\frac{5}{3}A = i_A}$$

$$i_x = i_A - i_B = -\frac{5}{3} - (-2) = -\frac{5}{3} + 2 = \frac{-5 + 6}{3} = \boxed{\frac{1}{3}A = i_x}$$

$$V_x = i_c \times 1 = \frac{1}{3} \times 1 = \boxed{\frac{1}{3}V = V_x}$$

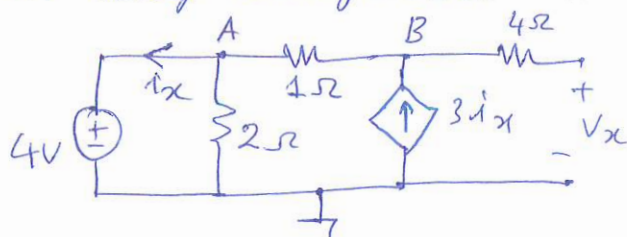Q3. a) step 1: Keep voltage source and kill current source



$$V_A = 4V.$$

$$\text{KCL at B: } \frac{V_B - 4}{1} - 3i_x = 0 \Rightarrow V_B - 3i_x = 4 \quad \text{eqn.1}$$

$$\text{KCL at A: } \frac{4 - V_B}{1} + \frac{4}{2} + i_x = 0 \Rightarrow -V_B + i_x = -6 \quad \text{eqn.2}$$

From eqn.2, $i_x = V_B - 6$. Put this in eqn.1 $V_B - 3(V_B - 6) = 4$


$$-2V_B + 18 = 4$$

$$\therefore V_{x,1} = V_B = 7V, \quad (i_x = 7 - 6 = 1A)$$

$$-2V_B = -14$$

$$\boxed{V_B = 7V}$$

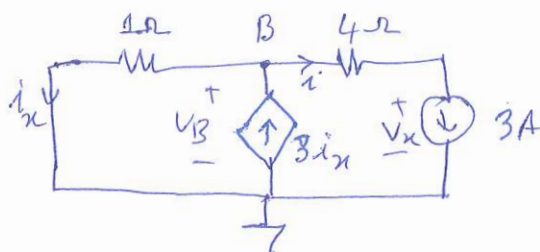Step 2: Keep the current source and kill the voltage source



$$\text{B: } i_x - 3i_x + 3 = 0$$

$$\Rightarrow i_x = \frac{3}{2} A.$$

$$V_B = i_x \times 1 = \frac{3}{2} V.$$

$$i = 3i_x - i_x = 2i_x = 2 \times \frac{3}{2} = 3A.$$

$$\therefore 4i + V_x - V_B = 0 \Rightarrow V_x = V_B - 4i = \frac{3}{2} - 4 \times 3$$

$$\Rightarrow V_{x,2} = 1.5 - 12 = -10.5V.$$

Overall result is the sum of results in step 1 and step 2.

$$V_x = V_{x,1} + V_{x,2} = 7 - 10.5 = -3.5V.$$

b) 4V voltage source: $i_x = i_{x,1} + i_{x,2} = 1 + \frac{3}{2} = 2.5A.$

P of 4V voltage source = $4 \times 2.5A = 10W$ receiving power

3A current source: $p = 3 \times V_x = 3 \times (-3.5) = -10.5W$ supplying power


$3i_x$ current source: $V_B = V_{B,1} + V_{B,2} = 7 + \frac{3}{2} = 8.5V.$

$p = 8.5 \times (-3i_x) = 8.5 \times (-3 \times 2.5) = -63.75W$ supplying power

c) From linearity

$$V_x = \frac{8}{4} \times V_{x,1} + \frac{-5}{3} \times V_{x,2} = 2 \times 7 - \frac{5}{3} \times (-10.5) = 14 + 17.5 = 31.5V.$$

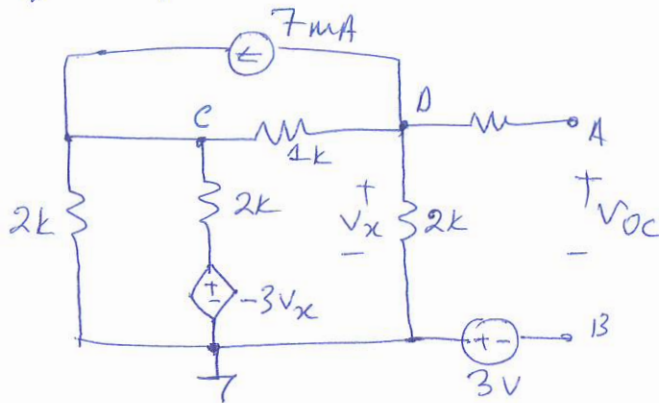Q4. To find the Thevenin equivalent circuit let us first find the open-circuit voltage



Node equation at C:

$$\frac{V_C}{2} + \frac{V_C - (-3V_x)}{2} + \frac{V_C - V_D}{1} - 7 = 0$$

Since $V_x = V_D$

$$\frac{V_C}{2} + \frac{V_C + 3V_D}{2} + \frac{V_C - V_D}{1} = 7$$

$$V_C + V_C + 3V_D + 2V_C - 2V_D = 14$$

$$\boxed{4V_C + V_D = 14} \quad \text{eqn. 1}$$

Node equation at D:

$$\frac{V_D}{2} + 7 + \frac{V_D - V_C}{1} = 0$$

$$V_D + 14 + 2V_D - 2V_C = 0$$

$$\boxed{3V_D - 2V_C = -14} \quad \text{eqn. 2}$$


Multiply eqn. 2 by 2 and add to eqn. 1:

$$7V_D = -14 \quad V_D = -2V$$

$$\therefore V_{OC} = V_D + 3 = -2 + 3 = \boxed{1V = V_{TH}}$$

To find R_{TH} , let us kill the independent sources and apply a test source between A and B:

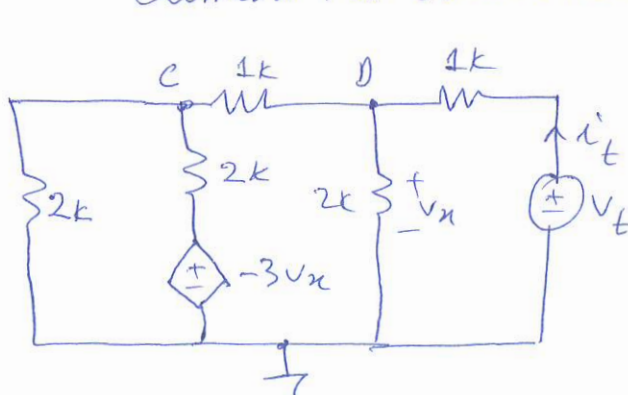Note: We may apply a voltage test source or a current test source. Both are acceptable.



$V_D = V_x$

C: $\frac{V_C}{2} + \frac{V_C + 3V_D}{2} + \frac{V_C - V_D}{1} = 0$

$$V_C + V_C + 3V_D + 2V_C - 2V_D = 0$$

$$4V_C + V_D = 0 \quad (*)$$

D: $\frac{V_D - V_C}{1} + \frac{V_D}{2} + \frac{V_D - V_t}{1} = 0$

$$2V_D - 2V_C + V_D + 2V_D = 2V_t$$


$$5V_D - 2V_C = 2V_t \quad (**)$$

Multiply (**) by 2 and add to (*)

$$11V_D = 4V_t \Rightarrow V_D = \frac{4}{11}V_t$$

$$i_t = \frac{V_t - V_D}{1} = V_t - \frac{4}{11}V_t = \frac{7}{11}V_t$$
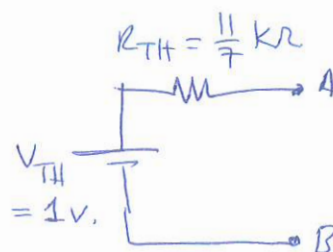
$$R_{TH} = \frac{V_t}{i_t} = \frac{V_t}{\frac{7}{11}V_t} = \frac{11}{7}k\Omega$$



Q5. a) $n = 4$
 $b = 6$

$n-1 = 3$ KCL equations

$$\begin{aligned} i_1 + i_2 - i_5 &= 0 \\ -i_2 + i_3 + i_6 &= 0 \\ -i_3 + i_4 + i_5 &= 0 \end{aligned}$$

$b-n+1 = 6-4+1 = 3$ KVL equations

$$\begin{aligned} v_2 + v_6 - v_1 &= 0 \\ v_3 + v_4 - v_6 &= 0 \\ -v_5 - v_3 - v_2 &= 0 \end{aligned}$$

b element equations

$$\begin{aligned} v_1 - R_1 i_1 &= 0 \\ v_2 - R_2 i_2 &= 0 \\ v_3 - R_3 i_3 &= 0 \\ v_4 - R_4 i_4 &= 0 \\ i_5 &= 10 \\ v_6 &= 5 \end{aligned}$$

$$\underbrace{\begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 1 & 1 & 0 & 0 & -1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & -1 & 1 & 1 & 0 \\ -1 & 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 1 & 0 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & -1 & -1 & 0 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 & 10 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 10 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 10 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 10 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}}_A \underbrace{\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \\ i_6 \end{bmatrix}}_x = \underbrace{\begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 10 \\ 5 \end{bmatrix}}_b$$

$Ax = b$

$$x = A^{-1}b = \begin{bmatrix} 52.5 \\ 47.5 \\ 52.5 \\ -47.5 \\ -100 \\ 5 \\ 5.25 \\ 4.75 \\ 5.25 \\ -4.75 \\ 10 \\ -0.5 \end{bmatrix}$$

Specifically

$v_5 = -100 \text{ V}$

$i_6 = -0.5 \text{ mA}$

b) $V_B = 5V$.

$$\frac{V_A - 5}{10} + \frac{V_A}{10} - 10 = 0 \Rightarrow V_A - 5 + V_A = 100 \Rightarrow V_A = \frac{105}{2} = 52.5V$$

$$\frac{V_C - 5}{10} + \frac{V_C}{10} + 10 = 0 \Rightarrow V_C - 5 + V_C = -100 \Rightarrow V_C = \frac{-95}{2} = -47.5V$$

∴ $V_5 = V_C - V_A = -47.5 - (52.5) = -100V$. ✓

$$\begin{aligned} i_6 &= i_2 - i_3 = \frac{V_A - V_B}{10} - \frac{V_B - V_C}{10} = \frac{52.5 - 5}{10} - \frac{5 - (-47.5)}{10} \\ &= \frac{52.5}{10} - \frac{5}{10} - \frac{5}{10} - \frac{47.5}{10} = \frac{5}{10} - \frac{5}{10} - \frac{5}{10} = -0.5V \end{aligned}$$

c)

$i_C = -10mA$

$$10(i_A - i_C) + 5 + i_A \times 10 = 0 \Rightarrow 20i_A - 10i_C + 5 = 0$$

$$20i_A + 100 + 5 = 0$$

$i_A = \frac{-105}{20} = -5.25mA$

$$10(i_B - i_C) + 10i_B - 5 = 0$$

$$20i_B - 10i_C - 5 = 0$$

$$20i_B + 100 - 5 = 0 \Rightarrow 20i_B = -95 \quad i_B = \frac{-95}{20} = -4.75mA$$

$$V_5 = -V_2 - V_3 = -10(i_A - i_C) - 10(i_B - i_C)$$

$$= -10i_A + 10i_C - 10i_B + 10i_C$$

$$= -10(i_A + i_B - 2i_C) = -10(-5.25 - 4.75 + 20)$$


$$= -10(-10 + 20) = -10 \times 10 = -100V \quad \checkmark$$

$$i_6 = i_2 - i_3 = (i_A - i_C) - (i_B - i_C) = i_A - i_C - i_B + i_C \Rightarrow i_A - i_B$$

$$= -5.25 - (-4.75)$$


$$= -5.25 + 4.75 = -0.5mA \quad \checkmark$$

d) step 1: kill current source

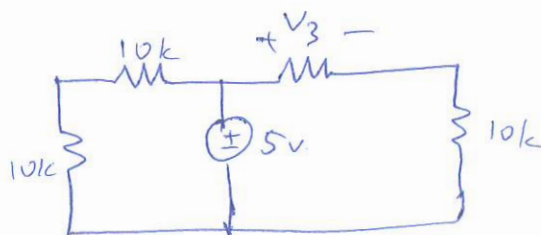

$$V_3 = \frac{10}{10+10} \times 5 = 2.5V$$

step 2: kill voltage source

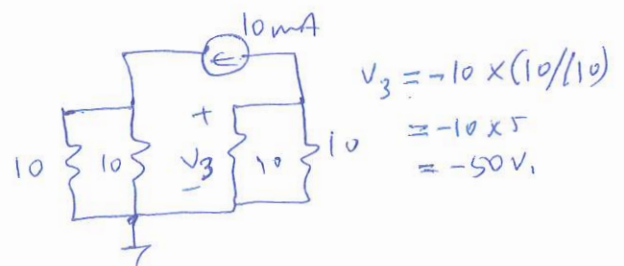


$$\begin{aligned} V_3 &= -10 \times (10/10) \\ &= -10 \times 5 \\ &= -50V \end{aligned}$$

Overall result is the sum of solutions in step 1 and 2.


$$V_3 = 2.5 + 50 = 52.5V \quad \checkmark \text{ Same as in (a).}$$

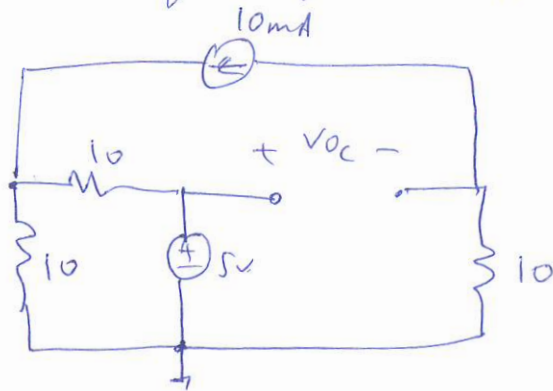e) Let us first find the open-circuit voltage.




Again superposition can be used:

Step 1:

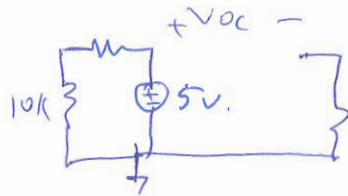

$$V_{OC,1} = 5V$$

Step 2:


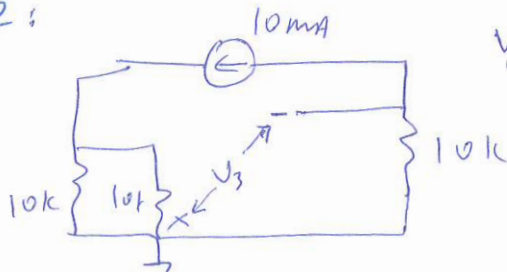


$$V_{OC,2} = +100V$$

$$V_{OC} = V_{OC,1} + V_{OC,2} = 5 + 100 = 105V$$

Now let us find R_{TH} :

$$R_{TH} = \frac{V_L}{I_L} = 10k\Omega$$

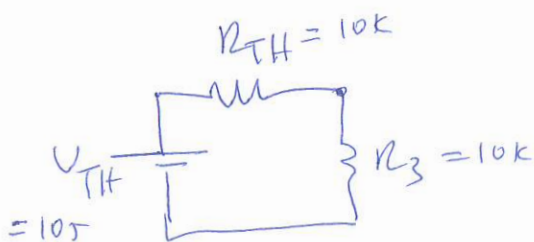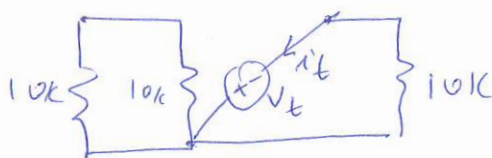

$$V_3 = \frac{10}{10} \times 105 = 52.5V \quad \checkmark$$

Same as in (a) and (d).

Q6. Since the circuit is linear we may write

$$V_0 = K_1 V_{s1} + K_2 V_{s2} + K_3 V_{s3} + K_4 V_{s4}$$

The data given in the Table can be collected into a matrix equation


$$\underbrace{\begin{bmatrix} 2 & 4 & -4 & 1 \\ 1 & 2 & 2 & 1.5 \\ 1 & 4 & 2 & 2 \\ 0 & 5 & 3 & -1 \end{bmatrix}}_A \underbrace{\begin{bmatrix} K_1 \\ K_2 \\ K_3 \\ K_4 \end{bmatrix}}_K = \underbrace{\begin{bmatrix} 20 \\ -4 \\ -1 \\ 3 \end{bmatrix}}_B \quad AK=B$$

Using Matlab the determinant of the coefficient matrix is $48 \neq 0$. Therefore the system has a unique solution.

Again using Matlab $K = A^{-1}B = \begin{bmatrix} 1 \\ 2 \\ -3 \\ -2 \end{bmatrix}$

$$V_0 = V_{s1} + 2V_{s2} - 3V_{s3} - 2V_{s4}$$

Q7.

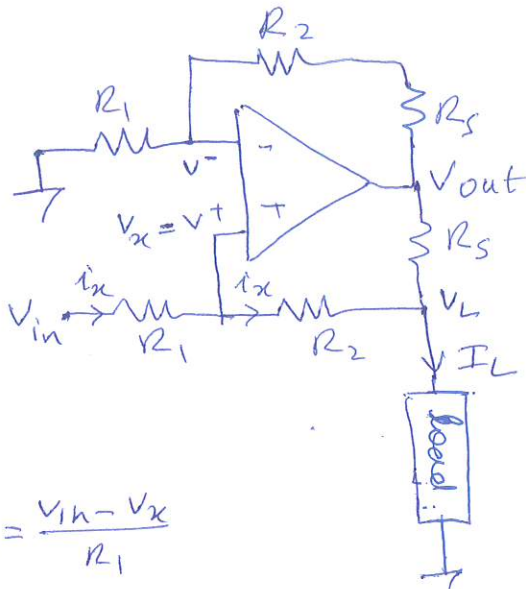

Assuming that the OpAmp is in the linear region (i.e. not saturated)
 $V^+ = V^-$. Define $V_x \triangleq V^+ = V^-$

$$\frac{V_{out} - V_x}{R_2 + R_5} = \frac{V_x}{R_1}$$

$$\frac{V_{out}}{R_2 + R_5} = V_x \left(\frac{1}{R_2 + R_5} + \frac{1}{R_1} \right)$$

$$V_{out} = V_x \left(1 + \frac{R_2 + R_5}{R_1} \right)$$

$$i_x = \frac{V_{in} - V_x}{R_1}$$

$$V_L = V_{in} - R_1 i_x - R_2 i_x$$

$$V_L = V_{in} - (R_1 + R_2) \frac{V_{in} - V_x}{R_1}$$

$$V_L = V_{in} \left(1 - \frac{R_1 + R_2}{R_1} \right) + \frac{R_1 + R_2}{R_1} V_x = -\frac{R_2}{R_1} V_{in} + \left(1 + \frac{R_2}{R_1} \right) V_x$$

$$i_L = i_x + \frac{V_{out} - V_L}{R_5} = \frac{V_{in} - V_x}{R_1} + \frac{1}{R_5} \left[V_x \left(1 + \frac{R_2 + R_5}{R_1} \right) + \frac{R_2}{R_1} V_{in} - \left(1 + \frac{R_2}{R_1} \right) V_x \right]$$

$$= \frac{V_{in} - V_x}{R_1} + \frac{1}{R_5} \left[V_x \frac{R_5}{R_1} + \frac{R_2}{R_1} V_{in} \right] = \frac{V_{in}}{R_1} - \frac{V_x}{R_1} + \frac{V_x}{R_1} + \frac{R_2}{R_5 R_1} V_{in}$$

$$i_L = V_{in} \left(\frac{1}{R_1} + \frac{R_2}{R_5 R_1} \right) = V_{in} \times \frac{R_5 + R_2}{R_5 R_1}$$