

CHAPTER 2 : BASIC CIRCUIT ANALYSIS

Connection Constraints : KCL, KVL

M elements $\rightarrow M$ currents and M voltages $\Rightarrow 2M$ unknowns

\Rightarrow Solve for constraints that relate these parameters.


Kirchhoff's current Law (KCL) based on Nodes

Algebraic sum of currents entering any node is zero.

Alternatively, sum of currents leaving any node is zero.

OR, sum of entering currents = sum of leaving currents.

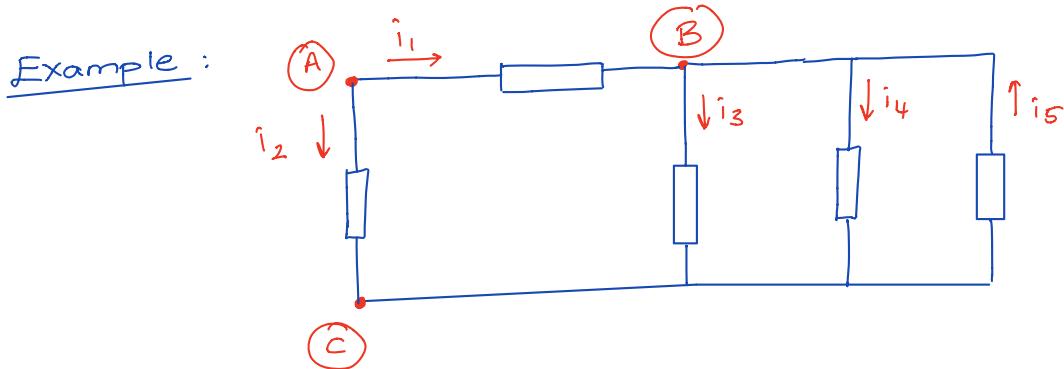Physical Reason: conservation of charge \Rightarrow rate of change of total charge at any node is zero.



entering

$$A: -i_1 - i_2 = 0$$

$$B: i_1 - i_3 - i_4 + i_5 = 0$$

$$C: i_2 + i_3 + i_4 - i_5 = 0$$

leaving

$$i_1 + i_2 = 0$$

$$-i_1 + i_3 + i_4 - i_5 = 0$$

$$-i_2 - i_3 - i_4 + i_5 = 0$$

Linear Dependence: A set of equations are linearly dependent if a linear combination of them is exactly zero \Rightarrow some equations can be derived from the others, and hence are unnecessary.


$$A + B + C = 0$$

* In the example above,

Conclusion: All node equations together are linearly dependent.

* Any $(n-1)$ of KCL node equations are linearly independent, where n is the # of nodes.

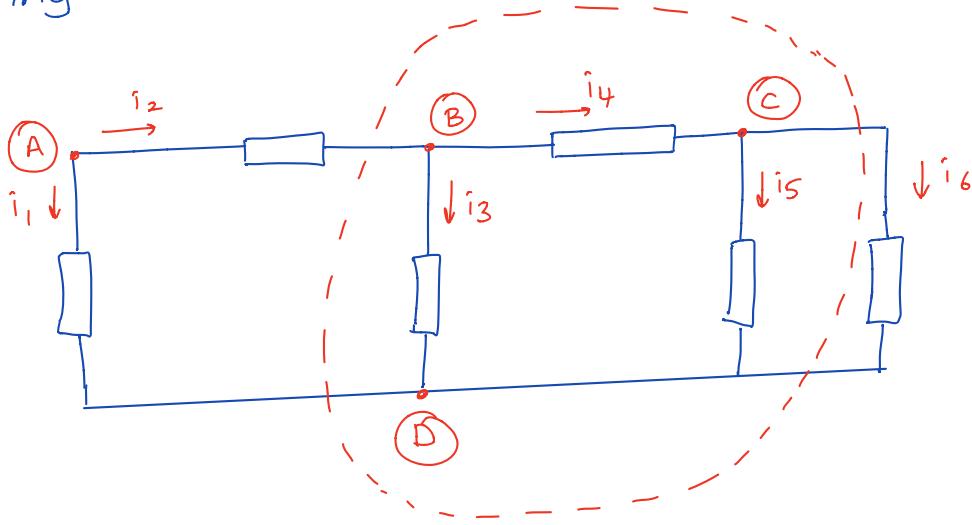* An alternative view of KCL: Take any spherical volume, place it inside the circuit. Algebraic sum of currents entering to the volume is zero.



$$\text{KCL} : i_1 + i_2 - i_5 + i_6 = 0$$

Physical Reason: conservation of charge in any volume.

* Place the volume around any node or shrink its size
 \Rightarrow KCL node equations.

Matrix Formulation of KCL equations.

$$A_i = 0$$

incidence matrix vector containing all currents

$$\left. \begin{array}{l} A: -i_1 - i_2 = 0 \\ B: i_1 - i_3 - i_4 + i_5 = 0 \\ C: i_2 + i_3 + i_4 - i_5 = 0 \end{array} \right\}$$

$$\underbrace{\begin{bmatrix} -1 & -1 & 0 & 0 & 0 \\ 1 & 0 & -1 & -1 & 1 \\ 0 & 1 & 1 & 1 & -1 \end{bmatrix}}_A \underbrace{\begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \\ i_5 \end{bmatrix}}_i = 0$$

* Due to redundancy, we may delete any one row of matrix A \Rightarrow equivalent to assigning one node as ground, and not writing KCL there.

Kirchhoff's Voltage Law (KVL) based on Loops

Loop : A closed path formed by tracing through an ordered sequence of nodes without passing any node more than once.


Closed path : starts and ends at the same node.

Closed node sequence : Same as loop, without the "passing any node more than once" requirement.
Union of loops.

KVL : Algebraic sum of voltages around any loop (or any closed node sequence) is zero.

Physical Reason : Due to conservative field, the potential difference between point A and A is zero.
The work done by moving a unit charge from point A to A is zero, no matter the path taken.

Example :

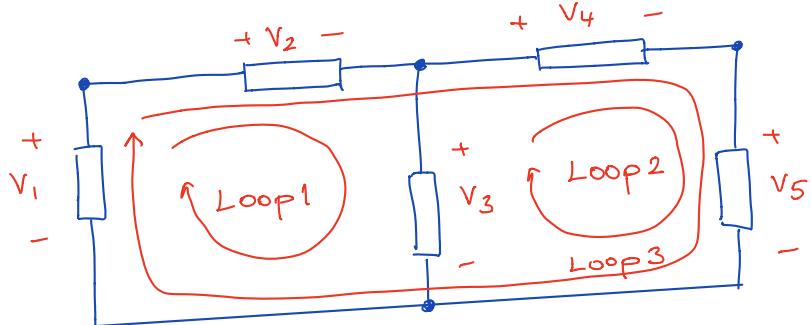

$$\text{Loop 1} : V_2 + V_3 - V_1 = 0$$

$$b = 5$$

$$n = 4$$

$$(b-n+1) = 2$$

$$\text{Loop 2} : V_4 + V_5 - V_3 = 0$$

$$\text{Loop 3} : V_2 + V_4 + V_5 - V_1 = 0$$

Question : Do we need all of these loop equations?
Are they linearly independent?


$$\text{Loop 1} + \text{Loop 2} - \text{Loop 3} = 0$$

* All loop equations together are linearly dependent.


- * b : number of two terminal elements
 n : number of nodes

There are $(b-n+1)$ linearly independent loop equations.
(# of meshes, as we will see later).

Examples :

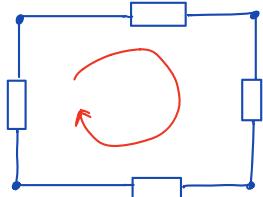

$$b=4 \\ n=4 \\ (b-n+1) = 1$$

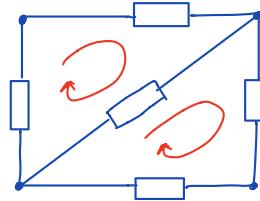

$$b=5 \\ n=4 \\ (b-n+1) = 2$$

Matrix Formulation of KVL equations :

$$Bv = 0$$

(→ vector containing all voltages
loop matrix)

Loop 1 : $v_2 + v_3 - v_1 = 0$

Loop 2 : $v_4 + v_5 - v_3 = 0$

Loop 3 : $v_2 + v_4 + v_5 - v_1 = 0$

$$\left\{ \begin{bmatrix} -1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & 1 \\ -1 & 1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \end{bmatrix} = 0 \right.$$

$\underbrace{\hspace{10em}}_{b-n+1 = 5-4+1=2}$
one row is redundant

Element Constraints :

- * Algebraic or differential relations between terminal voltage(s) and current(s) of a device.

* Resistors : algebraic relation between v and i .

* Linear resistors : algebraic relation is linear : $av + bi = 0$




* $v = Ri$
 $v - Ri = 0$

$\left\{ \begin{array}{l} R : \text{resistance in units of Ohm } (\Omega) \\ \text{Ohm} = V/A \end{array} \right.$

* $i = GV$ } G : conductance in units of Siemens (S)
 $GV - i = 0$ } Siemens = A/V



(6)

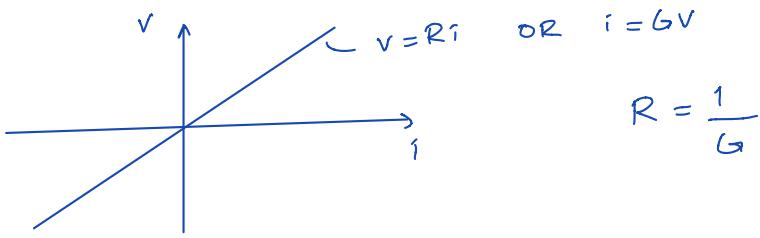



$$R = \frac{1}{G}$$

Special cases:

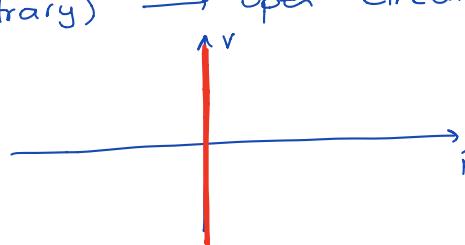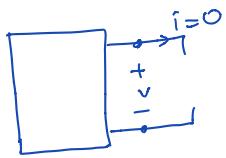
* $i = 0$ (V is arbitrary) \rightarrow open circuit



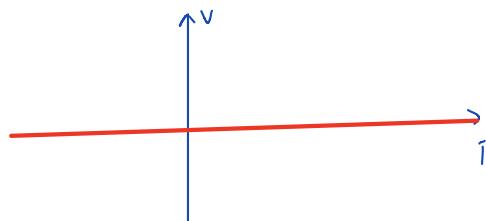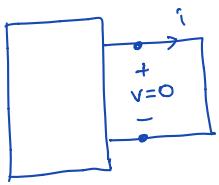* $v = 0$ (i is arbitrary) \rightarrow short circuit




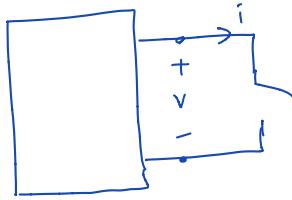* Ideal Switch: changes between open and short circuits



* Practical Switch: has a small resistance when short and large resistance when open

model:

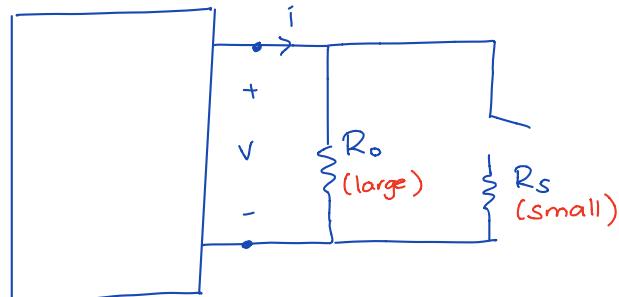


$$R_{\text{switch}} = \begin{cases} R_o & , \text{open} \\ R_s // R_o \approx R_s & , \text{short} \end{cases}$$


Sources: Generate power for the circuit

current source

ideal sources


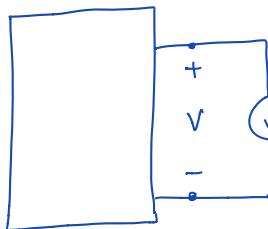


Practical sources

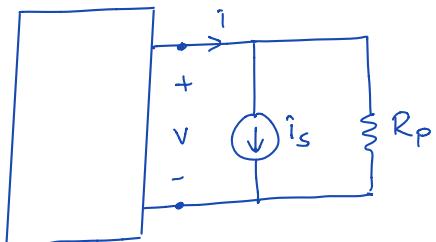

$$i = i_s + \frac{V}{R_p}$$

voltage source

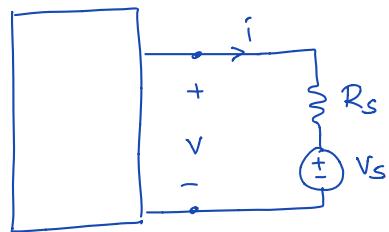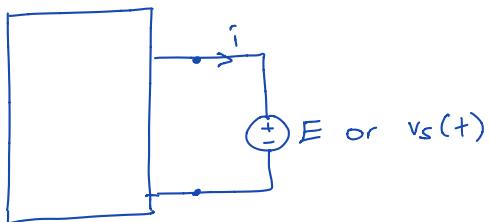

$$V = R_s \cdot i + V_s$$

Combined Constraints:

* When we write KCL + KVL + Element constraints \Rightarrow Combined constraints

* b : number of 2-terminal elements

n : number of nodes

* Each element has its v and i are unknowns

\Rightarrow $2b$ unknowns

\Rightarrow we need $2b$ linearly independent equations

How many equations do we have?

KCL equations : $n-1$

(# of nodes, except ground node)

KVL equations : $b-n+1$


(# of meshes)

+ Element Constraints : b

Total Equations : $2b$

* If all of these equations are linearly independent
 \Rightarrow circuit has a unique solution.

Example :

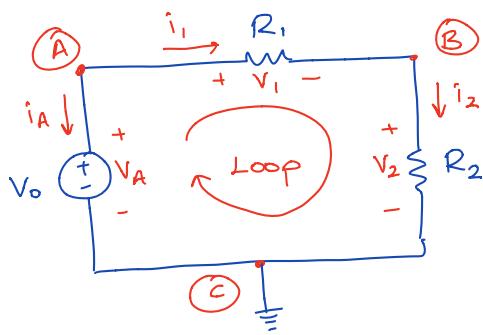

$$n = 3$$

$$b = 3$$

* Unknowns : $V_A, i_A, v_1, i_1, v_2, i_2 \Rightarrow 6$

* KCL equations : A : $i_A + i_1 = 0$ } $(n-1)$ equations
B : $-i_1 + i_2 = 0$

* KVL equations : Loop : $v_1 + v_2 - V_A = 0$ } $(b-n+1)$ equations

* Element Constraints : DA : $V_A = V_o$

$$D1 : v_1 = R_1 i_1 \Rightarrow v_1 - R_1 i_1 = 0$$

$$D2 : v_2 = R_2 i_2 \Rightarrow v_2 - R_2 i_2 = 0$$

Tableau Equations :

* Write KCL + KVL + Element Constraints in matrix form :

* KCL : $Ai = 0$

* KVL : $Bv = 0$

* Element constraints :

$$Mv + Ni = u$$

vector that depends
on sources

↑
depend on resistors

$$\begin{matrix} (b-n+1) \times b \\ \left[\begin{matrix} B & O \\ O & A \\ M & N \end{matrix} \right] \end{matrix} \begin{matrix} b \times 1 \\ \left[\begin{matrix} v \\ i \end{matrix} \right] \end{matrix} = \begin{matrix} b \times 1 \\ \left[\begin{matrix} O \\ O \\ u \end{matrix} \right] \end{matrix} \Rightarrow \begin{matrix} 2b \times 2b \\ T \end{matrix} \begin{matrix} 2b \times 1 \\ x \end{matrix} = \begin{matrix} 2b \times 1 \\ u_s \end{matrix}$$

* If T is invertible $\Rightarrow x = T^{-1} u_s$

* If T is not invertible \Rightarrow circuit has either no solution or has infinitely many solutions.

Example: For the previous example:

$$\begin{array}{c}
 \text{B} \\
 \left[\begin{array}{ccc|cc|c}
 -1 & 1 & 1 & 0 & 0 & 0 \\
 0 & 0 & 0 & 1 & 1 & 0 \\
 0 & 0 & 0 & 0 & -1 & 1 \\
 \hline
 1 & 0 & 0 & 0 & 0 & 0 \\
 0 & 1 & 0 & 0 & -R_1 & 0 \\
 0 & 0 & 1 & 0 & 0 & -R_2
 \end{array} \right] \quad \text{A} \\
 \left[\begin{array}{c} V_A \\ V_1 \\ V_2 \\ i_A \\ i_1 \\ i_2 \end{array} \right] = \left[\begin{array}{c} 0 \\ 0 \\ 0 \\ V_o \\ 0 \\ 0 \end{array} \right] \quad \text{u}
 \end{array}$$

* KCL equations: A : $i_A + i_1 = 0$

B : $-i_1 + i_2 = 0$

* KVL equations : Loop: $V_1 + V_2 - V_A = 0$

* Element Constraints: DA : $V_A = V_o$

D1 : $V_1 = R_1 i_1 \Rightarrow V_1 - R_1 i_1 = 0$


D2 : $V_2 = R_2 i_2 \Rightarrow V_2 - R_2 i_2 = 0$

Equivalent Circuits :

* Two circuits are equivalent if they have identical i-v relation between a specified pair of terminals.

* Result : The electrical behaviour inside the rest of the circuit will not change if we replace two identical circuits connected to it.

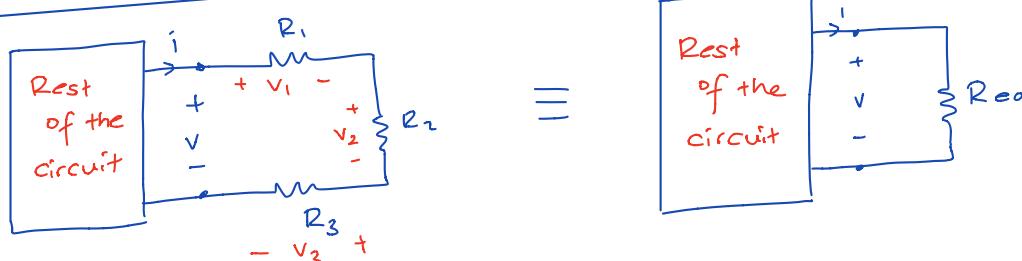
Equivalent Resistance : Series Combination



$$\left. \begin{array}{l} V = V_1 + V_2 + V_3 \\ V_j = R_j i_j = R_j i \end{array} \right\} \quad \left. \begin{array}{l} V = (R_1 + R_2 + R_3) i \\ V = R_{eq} i \end{array} \right\} \quad \begin{array}{l} \text{compare} \\ R_{eq} = R_1 + R_2 + R_3 \end{array}$$

Equivalent Resistance: Parallel Combination

(9)

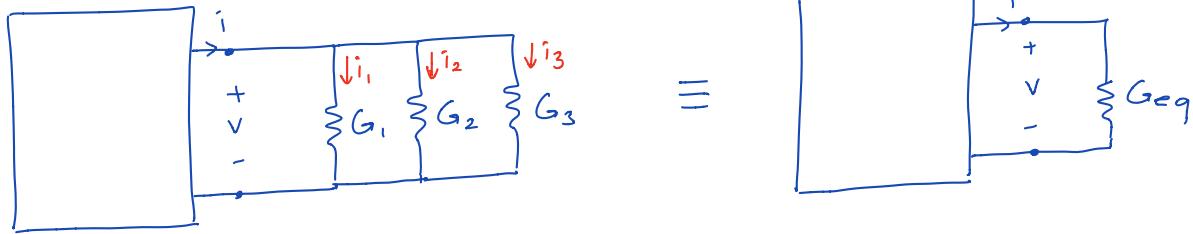


$$\left. \begin{array}{l} i = i_1 + i_2 + i_3 \\ i_j = G_j V_j = G_j V \end{array} \right\} \quad \left. \begin{array}{l} i = (G_1 + G_2 + G_3)V \\ i = G_{eq} \cdot V \end{array} \right\} \quad \text{compare: } G_{eq} = G_1 + G_2 + G_3$$


OR : $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

* 2 parallel resistors: $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$

Voltage Sources in series:

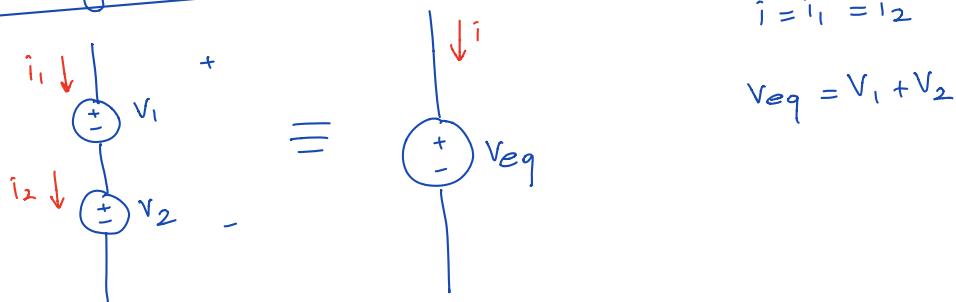


Current sources in parallel:

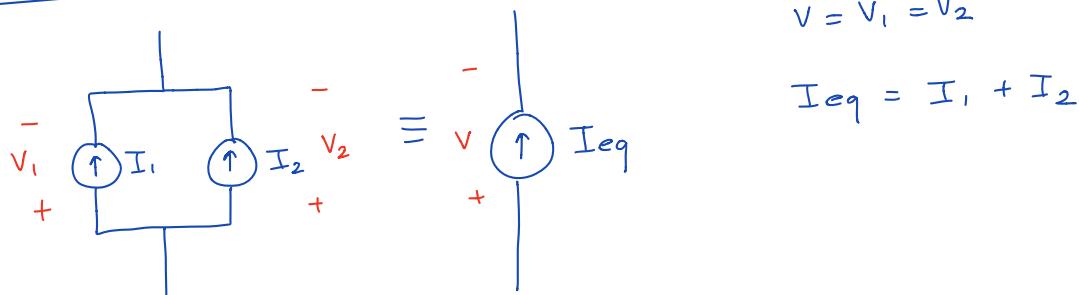


Equivalence of Practical Sources (Source Transformation)

Practical current source:

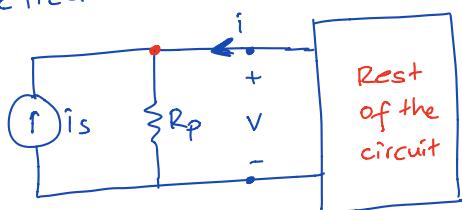

$$i = \frac{v}{R_p} - i_s \quad \xrightarrow{\text{compare}}$$

Practical voltage source:


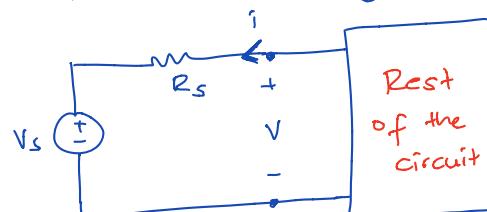


$$v = R_s \cdot i + v_s \quad i = \frac{v}{R_s} - \frac{v_s}{R_s}$$

* Equivalence when $R_p = R_s$ and $v_s = R_s \cdot i_s$
 (also, the relationship between Thevenin - Norton equivalent circuits)



more equivalent circuits:

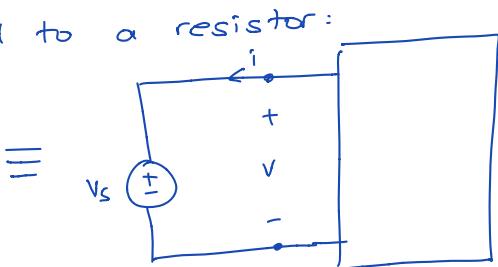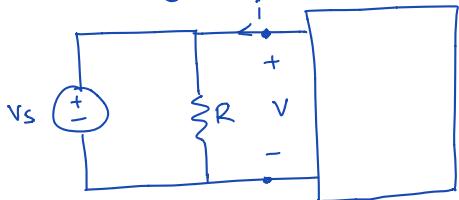* A voltage source in parallel to a resistor:




$v = v_s$ (independent of R)
 \Rightarrow Resistance can be omitted

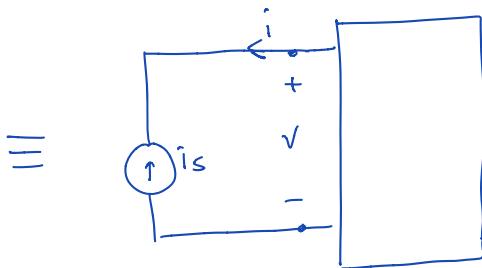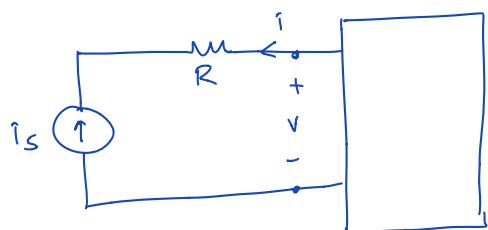* A current source in series with a resistor:



$i = -i_s$ (independent of R)
 \Rightarrow Resistance can be omitted

* Voltage Division:

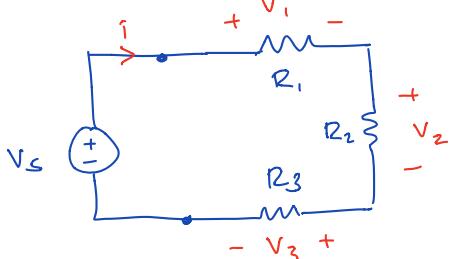


$$v_s = \text{Req. } i = (R_1 + R_2 + R_3) i$$

$$v_j = R_j \cdot i$$

} take ratio
 $v_j = \frac{R_j}{R_1 + R_2 + R_3} \cdot v_s$

* Current Division:

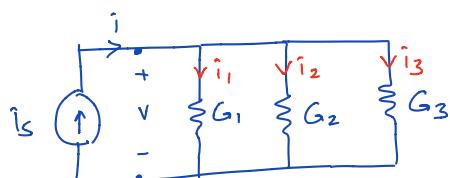


$$i_s = \text{Req. } v = (G_1 + G_2 + G_3) v$$

$$i_j = G_j \cdot v$$

} take ratio
 $i_j = \frac{G_j}{G_1 + G_2 + G_3} \cdot i_s$

* For 2 resistors:

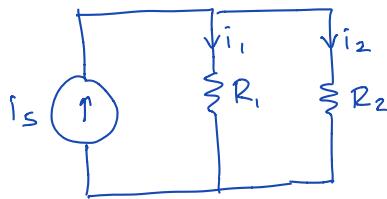


$$i_1 = \frac{G_1}{G_1 + G_2} \cdot i_s$$

$$i_2 = \frac{G_2}{G_1 + G_2} \cdot i_s$$




$$i_2 = \frac{R_2}{R_1 + R_2} \cdot i_s$$

Example

Circuit reduction

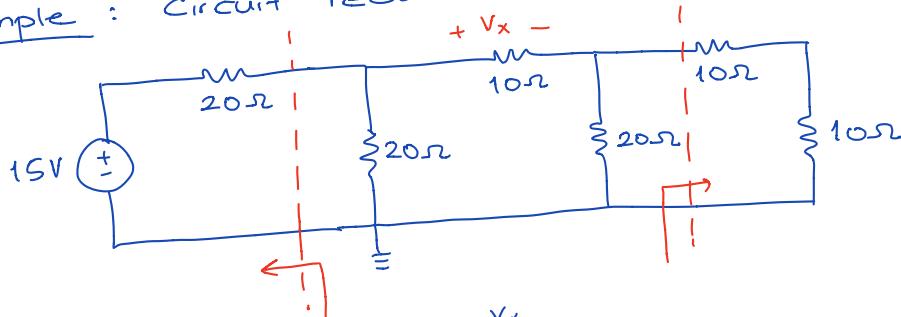

$$V_x = ?$$

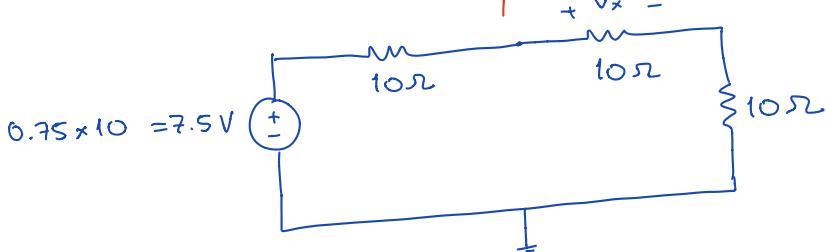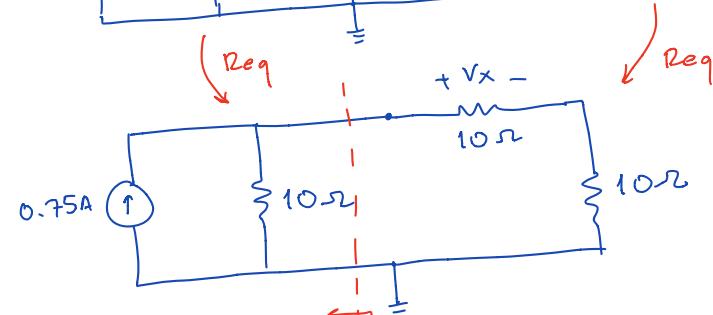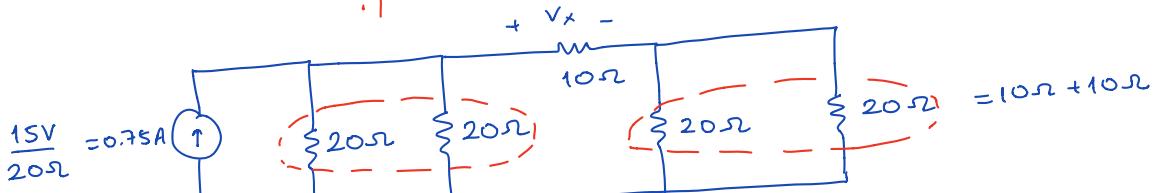

From voltage divider: $V_x = \frac{10}{10+10+10} \cdot 7.5V = 2.5V$

* Note that not all resistors are linear. A typical example is a diode, which is a non-linear resistor.
 $i = I_s(e^{v/v_T} - 1)$. This model can be simplified (piecewise linear switch).

- * A resistor is called passive if we have $p=vi \geq 0$ for all possible cases. Otherwise, it is called active.
- * A resistor is called time-varying, if its i-v behaviour changes with time.
- * A resistor is called bilateral if nothing changes when we replace the terminal connections
 \Rightarrow its i-v relation is symmetric with respect to the origin.