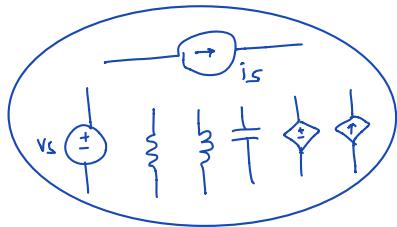


CHAPTER 8 - SINUSOIDAL STEADY STATE



All independent sources are sinusoidal.

$$v_s(t) = V_A \cdot \cos(\omega t + \phi)$$

- * Any variable (voltage or current) in the circuit satisfies an ODE of the form:

$$y^{(n)} + a_{n-1} y^{(n-1)} + \dots + a_1 y^{(1)} + a_0 y = u$$

nth order derivative

where u is sinusoidal and n is the order of the circuit.

- * Solution: $y(t) = \underbrace{y_N(t)}_{\text{natural response}} + \underbrace{y_F(t)}_{\text{forced response is also sinusoidal}}$

- * Natural Response: Assume $y_N(t) = e^{st}$

Insert into ODE: $s^n + a_{n-1}s^{n-1} + \dots + a_1 s + a_0 = 0$

characteristic polynomial with
n roots: s_1, \dots, s_n

$$y_N(t) = c_1 e^{s_1 t} + \dots + c_n e^{s_n t}$$

(if repeated roots exist)

$$\text{OR, } y_N(t) = c_1 e^{s_1 t} + c_2 t e^{s_1 t} + \dots$$

Assume that $\operatorname{Re} \{s_i\} < 0 \Rightarrow$ stable solution

- * So, $\lim_{t \rightarrow \infty} y_N(t) = 0$ for stable circuits \Rightarrow natural response decays down to zero.

i.e., $\lim_{t \rightarrow \infty} y(t) = y_F(t) \Rightarrow$ only forced response remains, which is sinusoidal.

This is called the sinusoidal steady state solution.
We will try to find this forced response when all sources are sinusoidal with the same frequency ω .

Phasor Representation :

We express sinusoids in cosine basis :

$$A_m \cdot \cos(\omega t + \phi)$$

where $A_m > 0$ by convention

$$\text{e.g., } -A_m \cos(\omega t + \phi) = A_m \cdot \cos(\omega t + \phi + \pi)$$

$$A_m \cdot \sin(\omega t + \phi) = A_m \cdot \cos(\omega t + \phi - \pi/2)$$

$$* A_m \cdot \cos(\omega t + \phi) = \operatorname{Re} \left\{ A_m \cdot e^{j(\omega t + \phi)} \right\} = \operatorname{Re} \left\{ \underbrace{A_m \cdot e^{j\phi}}_A \cdot e^{j\omega t} \right\}$$

$$A = \underbrace{A_m \cdot e^{j\phi}}_{\text{polar representation}} = \underbrace{A_m \cdot \cos \phi + j A_m \cdot \sin \phi}_{\text{Cartesian representation}} : \text{phasor of sinusoid}$$

$$\underbrace{A_m \cdot \cos(\omega t + \phi)}_{\substack{\text{signal waveform} \\ \text{in time domain}}} = \operatorname{Re} \left\{ \underbrace{A \cdot e^{j\omega t}}_{\substack{\text{phasor} \\ \text{in phasor domain}}} \right\} \quad \text{fixed } \omega$$

* ω should be a given, known frequency.

$$\text{Phasor: } A = \underbrace{A_m \cdot e^{j\phi}}_{\substack{\text{magnitude} \\ \text{phase}}} = A_m \angle \phi$$

Properties of Phasors

$$x(t) = X_m \cdot \cos(\omega t + \phi_x)$$

$$y(t) = Y_m \cdot \cos(\omega t + \phi_y)$$

$$\begin{array}{ccc} \longleftrightarrow & & \end{array} \begin{array}{l} X = X_m \cdot e^{j\phi_x} \\ Y = Y_m \cdot e^{j\phi_y} \end{array}$$

Uniqueness : iff $x(t) = y(t) \iff X = Y$ for fixed ω

$$\text{Linearity: } \alpha x(t) + \beta y(t) \iff \alpha X + \beta Y, \quad \alpha, \beta \in \mathbb{R}$$

$$\begin{aligned} \alpha x(t) + \beta y(t) &= \alpha \cdot \operatorname{Re} \{ X \cdot e^{j\omega t} \} + \beta \cdot \operatorname{Re} \{ Y \cdot e^{j\omega t} \} \\ &= \operatorname{Re} \{ \alpha X e^{j\omega t} + \beta Y e^{j\omega t} \} \\ &= \operatorname{Re} \{ \underbrace{(\alpha X + \beta Y)}_{\text{phasor}} e^{j\omega t} \} \quad \text{for fixed } \omega. \end{aligned}$$

(3)

Differentiation Rule :

$$x(t) = X_m \cos(\omega t + \phi) \iff X = X_m e^{j\phi}$$

$$\frac{dx(t)}{dt} = -\omega X_m \sin(\omega t + \phi)$$


$$= \omega X_m \sin(\omega t + \phi + \pi)$$

$$= \omega X_m \cos(\omega t + \phi + \pi - \pi/2)$$

$$= \omega X_m \cos(\omega t + \phi + \pi/2)$$

$$= \text{Re} \left\{ \underbrace{\omega X_m e^{j(\phi + \pi/2)}}_{\text{phasor of } \dot{x}(t)} \cdot e^{j\omega t} \right\}$$
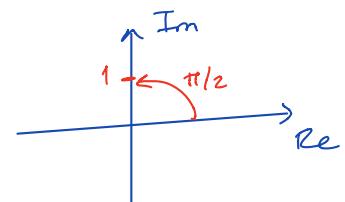
$$\begin{aligned} \text{Phasor of } \dot{x}(t) &= \omega X_m e^{j\phi} \cdot \underbrace{e^{j\pi/2}}_j \\ &= j\omega X_m \underbrace{e^{j\phi}}_X = j\omega X \end{aligned}$$



$$\boxed{\begin{array}{l} x(t) \iff X \\ \frac{dx(t)}{dt} \iff j\omega X \end{array}}$$

{ same ω ,
 $\omega = 1 \text{ rps}$

$$\text{Example : } x(t) = 3 \cos(t) - 4 \cos(t + \pi/4) + 2 \sin(t + \pi/6)$$

$$\text{write as } x(t) = A_m \cos(\omega t + \phi)$$

$$x(t) = 3 \cos(t) + 4 \cos(t + \pi/4 + \pi) + 2 \cos(t + \pi/6 - \pi/2)$$

$$X = 3 \cdot e^{j0^\circ} + 4 \cdot e^{j(\pi/4 + \pi)} + 2 \cdot e^{j(\pi/6 - \pi/2)}$$


$$= 3 + 4 e^{j5\pi/4} + 2 e^{-j\pi/3}$$

using scientific calculator

$$= 1.17 - j4.56$$

$$= 4.71 e^{-j75.61^\circ}$$

$$= 4.71 e^{-j1.32}$$

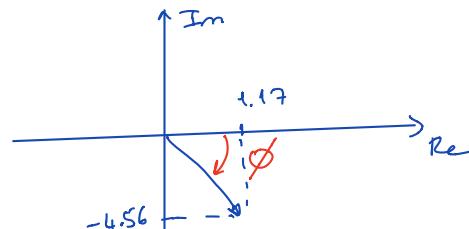

$$x(t) = 4.71 \cos(t - 1.32)$$

Example : $\ddot{x} + 3\dot{x} + 2x = \sin(3t)$ w=3 rps
 $x(0) = 1, \dot{x}(0) = 1$. Find $x(t)$ for $t \geq 0$.

$$x(t) = x_N(t) + x_F(t)$$

* Natural response : $\ddot{x} + 3\dot{x} + 2x = 0$
 $s^2 + 3s + 2 = 0$
 $(s+1)(s+2) = 0 \Rightarrow s_1 = -1, s_2 = -2$


$$x_N(t) = C_1 e^{-t} + C_2 e^{-2t}$$

* Forced response : $x_F(t) = \operatorname{Re} \{ X e^{j3t} \}$
 $\ddot{x} + 3\dot{x} + 2x = \cos(3t - \pi/2)$ convert to phasor domain

$$(j^3)^2 X + 3(j^3)X + 2X = e^{-j\pi/2}$$

$$(-9 + 9j + 2)X = e^{-j\pi/2}$$
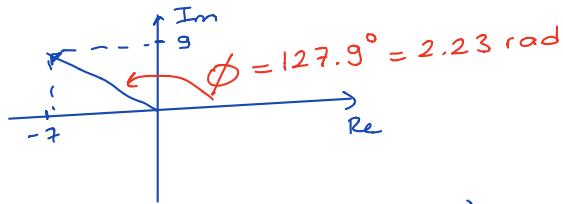
$$X = \frac{e^{-j\pi/2}}{-7 + 9j} = \frac{e^{-j\pi/2}}{\sqrt{7^2 + 9^2} \angle 2.23} = \frac{1}{\sqrt{130}} \angle (-\pi/2 - 2.23)$$



$$x_F(t) = \frac{1}{\sqrt{130}} \cos(3t - \pi/2 - 2.23)$$


* Then,

$$\begin{aligned} x(t) &= x_N(t) + x_F(t) \\ &= C_1 e^{-t} + C_2 e^{-2t} + \frac{1}{\sqrt{130}} \cos(3t - \pi/2 - 2.23) \end{aligned}$$

* Now, use initial conditions to find C_1 and C_2 .

Circuit Equations in Phasor Form

KCL :

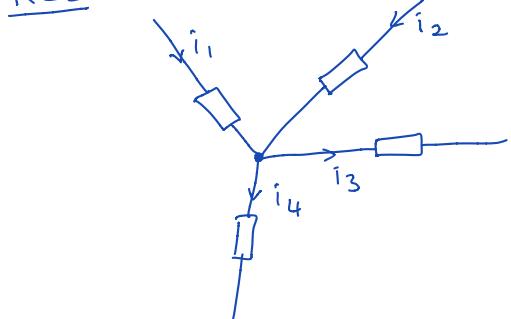


$$i_n(t) = \operatorname{Re} \left\{ \underbrace{I_n}_{\text{phasor}} e^{j\omega t} \right\}$$

$$\text{typical KCL : } -i_1(t) - i_2(t) + i_3(t) + i_4(t) = 0$$

uniqueness & linearity
of phasors

$$-I_1 - I_2 + I_3 + I_4 = 0$$

KVL :

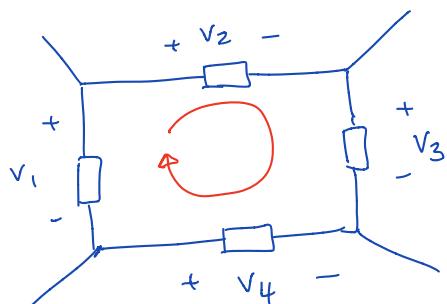

$$v_n(t) = \operatorname{Re} \left\{ \underbrace{V_n}_{\text{phasor}} e^{j\omega t} \right\}$$

$$\text{typical KVL : } -v_1(t) + v_2(t) + v_3(t) - v_4(t) = 0$$


uniqueness & linearity

$$-V_1 + V_2 + V_3 - V_4 = 0$$

Result : KCL and KVL retain their form in phasor domain.

Element Relations :

Resistors :

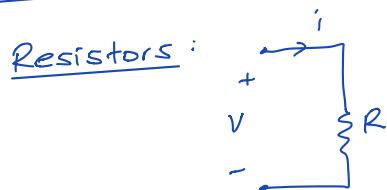

in time-domain :

$$v(t) = R \cdot i(t)$$

$$i(t) = G \cdot v(t)$$

in phasor-domain :

$$V = R \cdot I$$

$$I = G \cdot V$$


$$Z_R = \frac{V}{I} = R$$

impedance
of resistor

$$Y_R = \frac{I}{V} = G = \frac{1}{R}$$

admittance
of resistor

Capacitor :

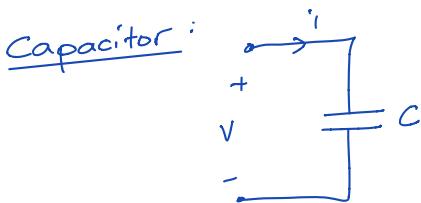

in time-domain :

$$i(t) = C \frac{dV(t)}{dt}$$

in phasor-domain :

$$I = C \cdot j\omega V$$

$$I = j\omega C \cdot V$$


$$Z_C = \frac{V}{I} = \frac{1}{j\omega C}$$

impedance
of capacitor

$$Y_C = \frac{I}{V} = j\omega C$$

admittance
of capacitor

(6)

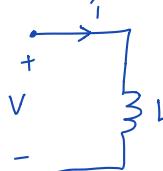Inductor: 

in time-domain: $v(t) = L \frac{di(t)}{dt}$

in phasor-domain: $V = L \cdot j\omega I$

$$V = j\omega L \cdot I$$


$$Z_L = \frac{V}{I} = j\omega L \quad , \quad Y_L = \frac{I}{V} = \frac{1}{j\omega L}$$

\nwarrow impedance of inductor \nwarrow admittance of inductor


Result: The whole circuit equations, KCL + KVL + branch equations, are now linear, algebraic, but with complex coefficients.

Result: All of our analysis techniques: node, mesh, Thévenin, Norton, etc. can still be applied in phasor domain. The only difference is now we have to deal with complex coefficients.

Concept of Impedance and Admittance

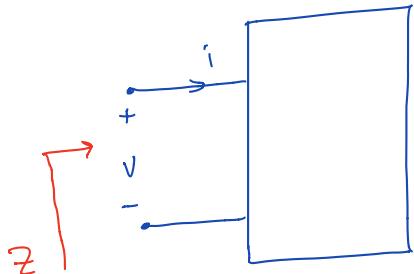

Impedance: $Z = \frac{V}{I} = \frac{|V| \cdot e^{j\angle V}}{|I| \cdot e^{j\angle I}} = \frac{|V|}{|I|} \cdot e^{j(\angle V - \angle I)}$

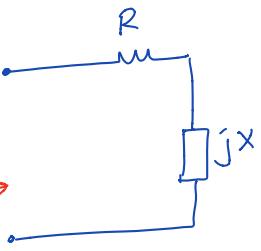


$= |Z| \cdot e^{j\angle Z}$ phase difference between voltage and current phasors
 magnitude ratio between voltage and current phasors


$Z = R + jX$ [in Ω]

\nwarrow resistance \nwarrow reactance

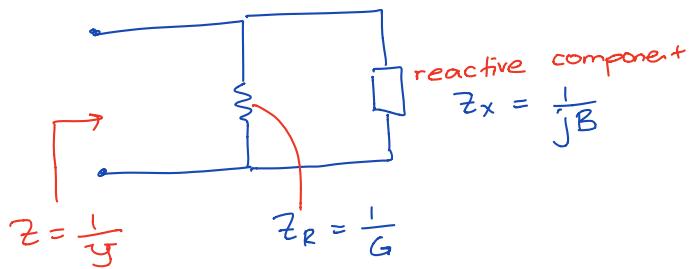
Admittance : $\text{Y} = \frac{\text{I}}{\text{V}} = \frac{1}{Z} = G + jB$ [in S] (7)



Example :

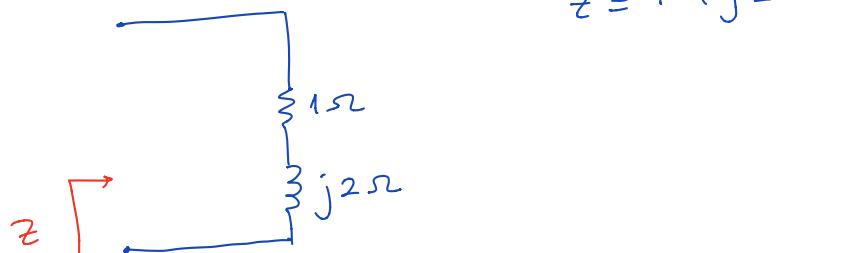

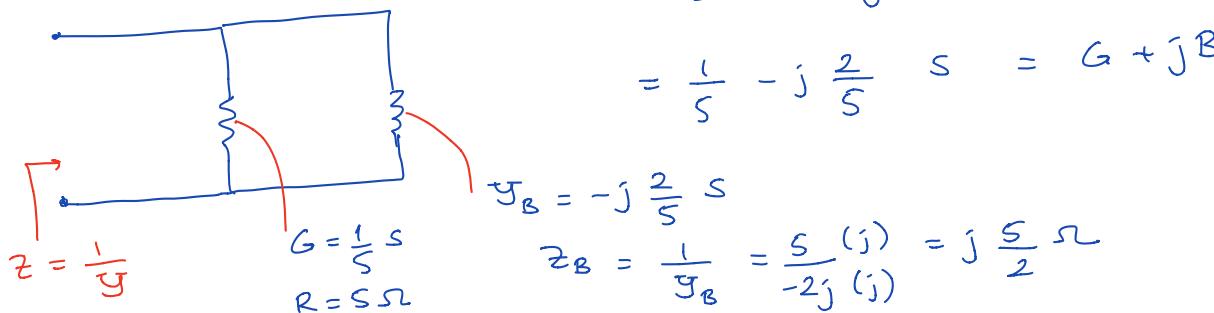
$$\begin{aligned} Y &= \frac{1}{Z} = \frac{1 - j2}{1 + j2} = \frac{1 - j2}{5} \\ &= \frac{1}{5} - j \frac{2}{5} \text{ S} = G + jB \end{aligned}$$



- * Series/parallel equivalences are the same as in resistive circuits.
- * Voltage/current division work the same as in resistive circuits.

Example : Node analysis

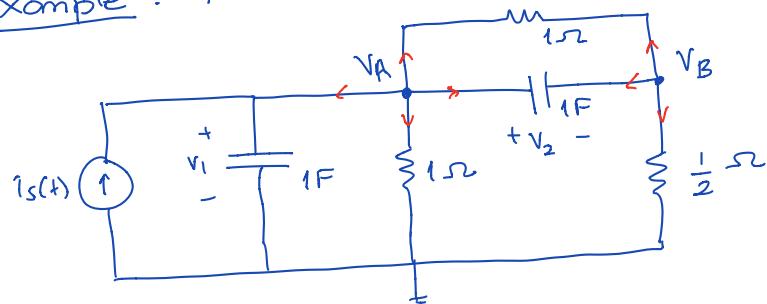

$i_s(t) = 2 \cos(t - 30^\circ) \text{ A}$

$v_1(t) = ?$

$v_2(t) = ?$

$i_s(t) = 2 \cos(t - \pi/6) \text{ A}$

w = 1 rps

 $\Rightarrow I_s = 2 e^{-j\pi/6} \text{ A}$

(8)

$$\text{KCL at A} : -I_s + \frac{V_A}{\frac{1}{j+1}} + \frac{V_A}{1} + \frac{V_A - V_B}{1} + \frac{V_A - V_B}{\frac{1}{j+1}} = 0$$

$$(2+2j)V_A - (1+j)V_B = I_s$$

$$\text{KCL at B} : \frac{V_B - V_A}{1} + \frac{V_B - V_A}{\frac{1}{j+1}} + \frac{V_B}{\frac{1}{2}} = 0$$

$$-(1+j)V_A + (3+j)V_B = 0 \Rightarrow V_B = \frac{1+j}{3+j} V_A$$

Insert into the first equation:

$$\left[2+2j - (1+j) \frac{(1+j)}{3+j} \right] V_A = I_s$$

$$\left[\frac{4+8j - 2j}{3+j} \right] \cdot V_A = I_s$$

$$V_A = \frac{3+j}{4+6j} I_s$$

$$V_B = \frac{1+j}{3+j} \cdot V_A = \frac{1+j}{3+j} \cdot \frac{3+j}{4+6j} \cdot I_s = \frac{1+j}{4+6j} I_s$$

$$\begin{aligned} * \text{ Then, } V_1 &= V_A = \frac{3+j}{4+6j} \cdot I_s = \frac{3+j}{4+6j} \cdot 2 \cdot e^{-j\pi/6} \\ &= \frac{\sqrt{10} \cdot e^{j\arctan(1/3)}}{\sqrt{52} \cdot e^{j\arctan(6/4)}} \cdot 2 \cdot e^{-j\pi/6} = 0.87 \cdot e^{-j1.17} \end{aligned}$$


$$V_1(t) = 0.87 \cos(t - 1.17) V$$

$$\begin{aligned} * \text{ Then, } V_2 &= V_A - V_B = \frac{3+j}{4+6j} I_s - \frac{1+j}{4+6j} I_s = \frac{2}{4+6j} I_s \end{aligned}$$

$$= \frac{2}{\sqrt{52}} \cdot e^{j\arctan(6/4)} \cdot 2 \cdot e^{-j\pi/6} = 0.55 e^{-j1.5}$$

$$V_2(t) = 0.55 \cos(t - 1.5) V$$

Concept of Network Function

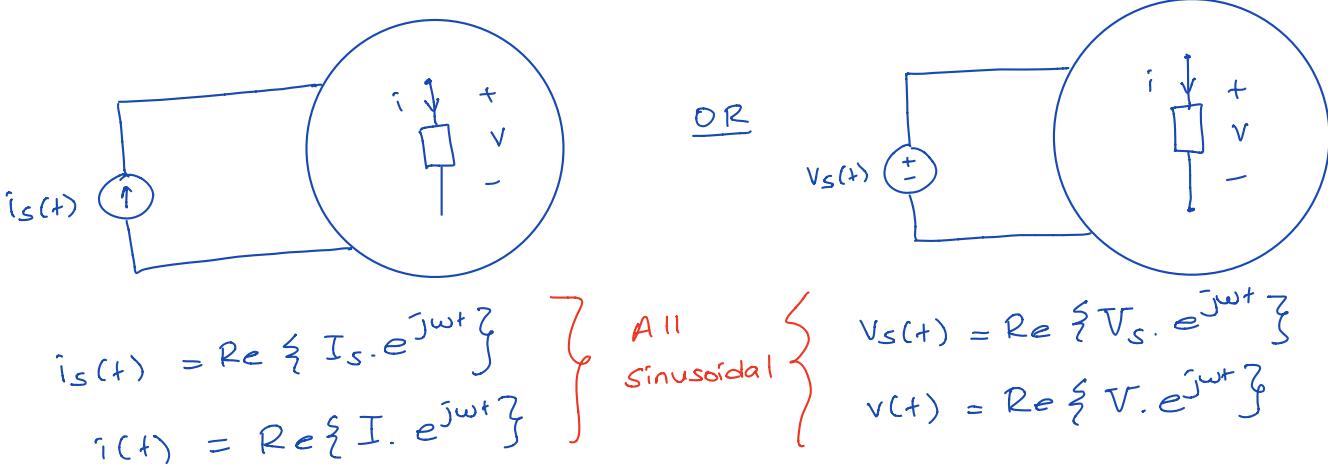

$H = \frac{\text{output phasor}}{\text{input phasor}}$: transfer function

e.g., $H_1 = \frac{V}{I_s}$, $H_2 = \frac{I}{I_s}$, $H_3 = \frac{V}{V_s}$, ...

Importance : (output phasor) = $H \times$ (input phasor)

e.g., $V = H_1 \cdot I_s$, let $I_s = I_{sm} e^{j\phi_s}$
 $H_1 = |H_1| \cdot e^{j\angle H_1}$

$$V = |H_1| \cdot I_{sm} \cdot e^{j(\angle H_1 + \phi_s)}$$

$$V(t) = \operatorname{Re} \{ V \cdot e^{j\omega t} \} = |H_1| \cdot I_{sm} \cos(\omega t + \underbrace{\angle H_1 + \phi_s}_{\text{in red}})$$

* output magnitude = (transfer fn. magnitude) \times (input magnitude)
* output phase = (transfer fn. phase) + (input phase)


$$H(j\omega) = \frac{\text{polynomial in } (j\omega)}{\text{polynomial in } (j\omega)}$$

$$= \frac{a_m (j\omega)^m + a_{m-1} (j\omega)^{m-1} + \dots + a_1 (j\omega) + a_0}{(j\omega)^n + b_{n-1} (j\omega)^{n-1} + \dots + b_1 (j\omega) + b_0}$$

$$H(j\omega) = \underbrace{|H(j\omega)|}_{\text{both magnitude and phase}} \cdot e^{j\angle H(j\omega)}$$

are functions of ω

Example :

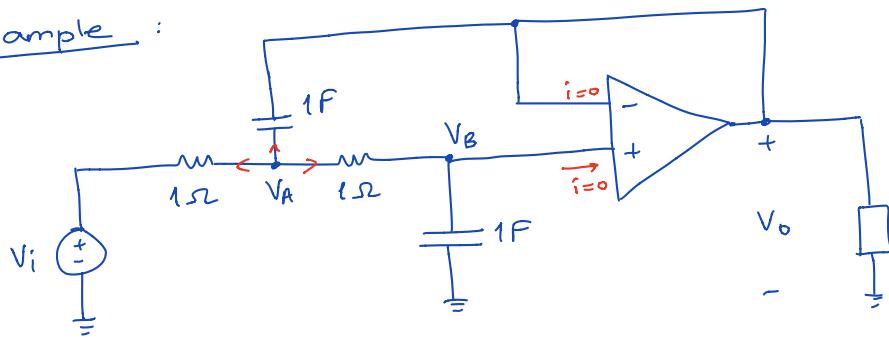

$$\text{Find } H(j\omega) = \frac{V_o}{V_i}$$

Assume OPAMP is in linear region. $\Rightarrow V_+ = V_-$
 $V_B = V_o$

$$\text{KCL at A} : \frac{V_A - V_i}{1} + \frac{V_A - V_B}{1} + \frac{V_A - V_o}{\frac{1}{j\omega \cdot 1}} = 0$$

$$(2 + j\omega)V_A - (1 + j\omega)V_o = V_i$$

$$\text{KCL at B} : V_B = \frac{\frac{1}{j\omega \cdot 1}}{1 + \frac{1}{j\omega \cdot 1}} \cdot V_A \quad (\text{voltage divider})$$

$$V_o = \frac{1}{1 + j\omega} \cdot V_A \Rightarrow V_A = (1 + j\omega) \cdot V_o$$

Insert into the first equation:

$$(2 + j\omega)(1 + j\omega)V_o - (1 + j\omega)V_o = V_i$$

$$[(j\omega)^2 + 3(j\omega) + 2 - 1 - (j\omega)]V_o = V_i$$

$$[(j\omega)^2 + 2(j\omega) + 1]V_o = V_i$$


$$H(j\omega) = \frac{V_o}{V_i} = \frac{1}{(j\omega)^2 + 2(j\omega) + 1} = \frac{1}{-\omega^2 + 2j\omega + 1}$$

* Then, if $v_i(+)=3 \cos(2t) \text{ V}$, $\omega = 2 \text{ rps}$

$$H(j2) = \frac{1}{-4 + j4 + 1} = \frac{1}{-3 + 4j} = \frac{1}{5 \cdot e^{j\arctan(\frac{4}{-3})}}$$

$$= \frac{1}{5 e^{j(\pi - \arctan(\frac{4}{3}))}}$$

$$= \frac{1}{5} e^{-j2.21}$$

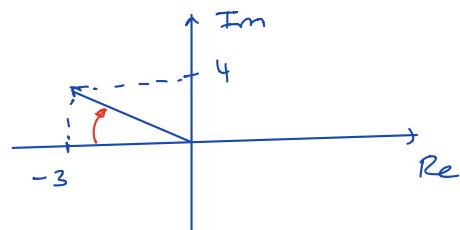


$$v_o(t) = 3 \cdot |H(j\omega)| \cdot \cos(\omega t + \angle H(j\omega)) \text{ V}$$

$$= \frac{3}{5} \cdot \cos(2t - 2.21) \text{ V}$$

Superposition:

Always applies in time domain.

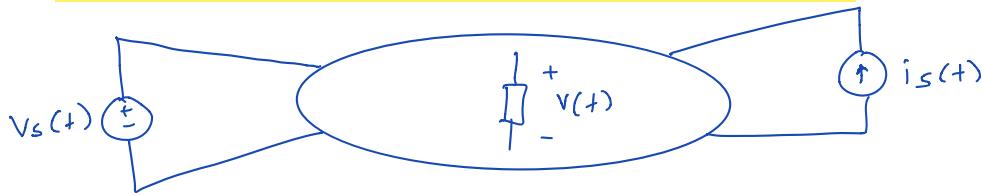

$$v_s(t) = V_m \cos(\omega_1 t + \phi_1)$$

$$i_s(t) = I_m \cos(\omega_2 t + \phi_2)$$

$$\left. \begin{array}{l} \\ \end{array} \right\} \omega_1 \neq \omega_2$$

* $v_s(t)$ acting alone \Rightarrow use phasor analysis with frequency ω_1

$$\Rightarrow \text{Find } V_1 \Rightarrow v_1(t) = \operatorname{Re} \{ V_1 e^{j\omega_1 t} \}$$

* $i_s(t)$ acting alone \Rightarrow use phasor analysis with frequency ω_2

$$\Rightarrow \text{Find } V_2 \Rightarrow v_2(t) = \operatorname{Re} \{ V_2 e^{j\omega_2 t} \}$$

Superposition:

$$v(t) = v_1(t) + v_2(t)$$


Added in time domain

* Note: If $\omega_1 = \omega_2$, then (and only then) we may also use superposition in phasor domain.

$$v(t) = v_1(t) + v_2(t) = \operatorname{Re} \{ V_1 e^{j\omega_1 t} \} + \operatorname{Re} \{ V_2 e^{j\omega_2 t} \}$$

$$= \operatorname{Re} \{ (V_1 + V_2) e^{j\omega t} \}, \quad \text{iff } \omega = \omega_1 = \omega_2$$

If $\omega_1 = \omega_2$, we may first add $V_1 + V_2$ in phasor domain, then find $v(t)$ in time domain.

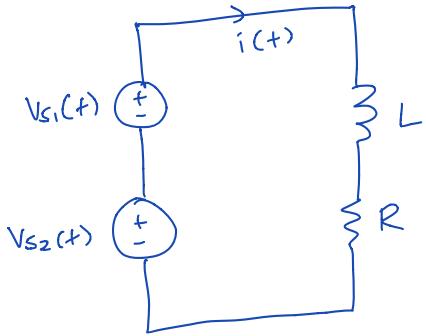
Simple Example :

$$R = 10 \text{ k}\Omega, \quad L = 200 \text{ mH}$$

$$V_{S1}(t) = 24 \cos(20000t) \text{ V}$$

$$V_{S2}(t) = 8 \cos(60000t + 30^\circ) \text{ V}$$

$$i(+) = ?$$

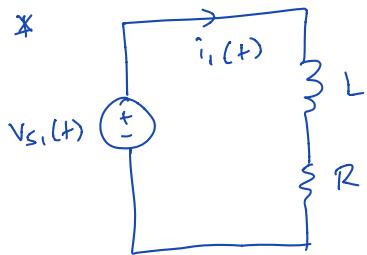


$$Z_R = 10 \text{ k}\Omega, \quad \omega_1 = 20000 \text{ rps}$$

$$Z_L = j\omega_1 L = j20 \cdot 10^3 \cdot 200 \cdot 10^{-3} = j4 \text{ k}\Omega$$

$$I_1 = \frac{V_{S1}}{Z_R + Z_L} = \frac{24 \cdot e^{j0}}{(10 + j4) \text{ k}\Omega} = 2.23 e^{-j0.38} \text{ mA}$$
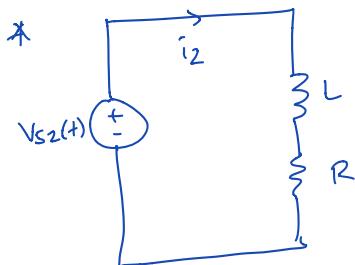
$$i_1(+) = 2.23 \cos(20000t - 0.38) \text{ mA}$$



$$Z_R = 10 \text{ k}\Omega, \quad \omega_2 = 60000 \text{ rps}$$

$$Z_L = j\omega_2 L = j60 \cdot 10^3 \cdot 200 \cdot 10^{-3} = j12 \text{ k}\Omega$$

$$I_2 = \frac{V_{S2}}{Z_R + Z_L} = \frac{8 \cdot e^{j\pi/6}}{(10 + j12) \text{ k}\Omega} = 0.51 e^{-j0.35} \text{ mA}$$

$$i_2(+) = 0.51 \cos(60000t - 0.35) \text{ mA}$$




* Finally,

$$i(+) = i_1(+) + i_2(+)$$

$$= 2.23 \cos(20000t - 0.38) + 0.51 \cos(60000t - 0.35) \text{ mA}$$

Thevenin - Norton Equivalent Circuits

13

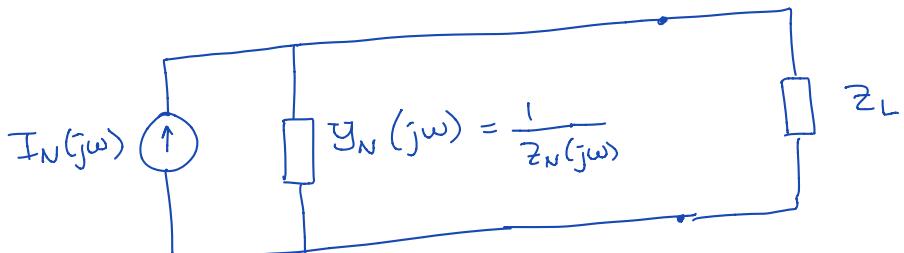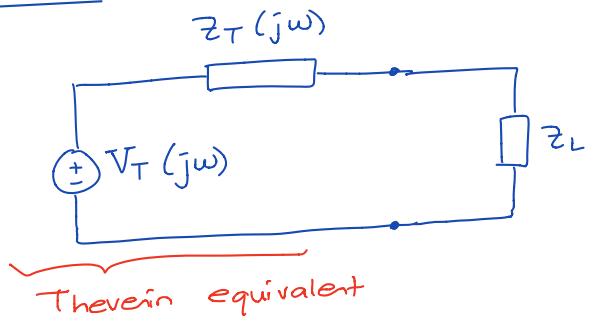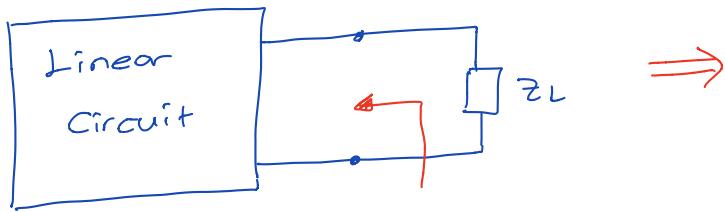


Norton equivalent

$$I_N = \frac{V_T}{Z_T}$$

$$Z_T = Z_N = \frac{1}{Y_N}$$

* Finding the equivalent circuit is the same as in resistive circuits, but with complex values in phasor domain.



Example:

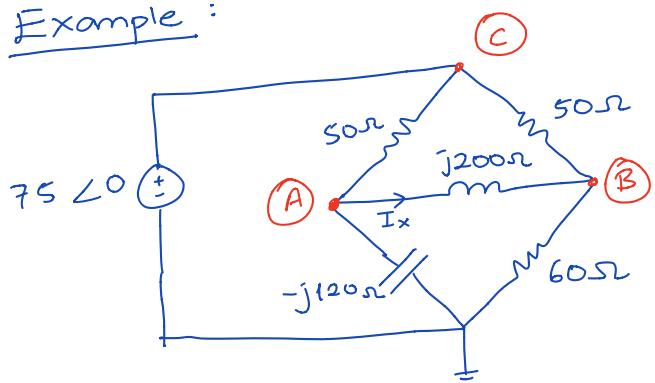

Find I_x in phasor domain by using Thevenin equivalent circuit.


So, first find Thevenin eq. seen by $j200\Omega$ inductor between A-B.

Z_T : Kill all independent sources

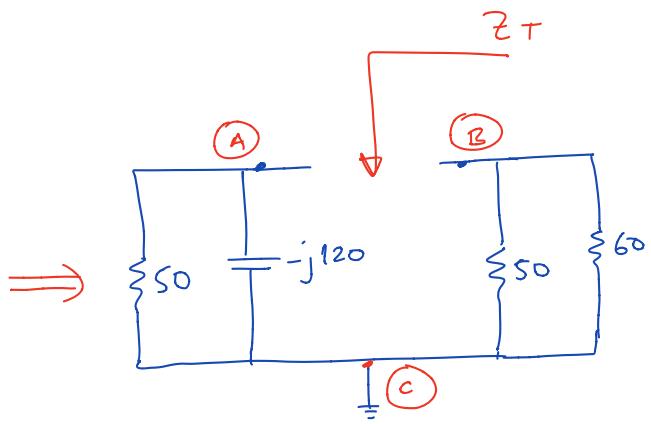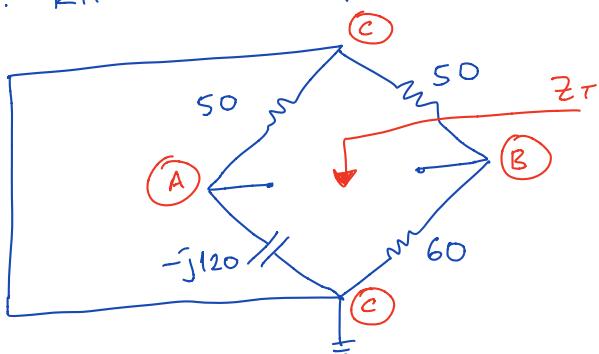

$$Z_T = [50 \parallel (-j120)] + [50 \parallel 60] \\ = \frac{50 \cdot (-j120)}{50 - j120} + \frac{50 \cdot 60}{50 + 60} = 69.9 - j17.8 \Omega$$

V_T : open circuit voltage between A-B.

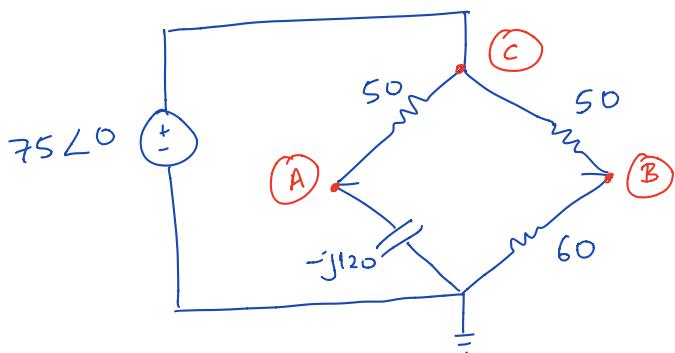

$$V_T = V_A - V_B$$


$$V_C = 75 \angle 0^\circ$$

$$V_A = \frac{-j120}{50 - j120} \cdot 75 \angle 0^\circ$$

$$V_B = \frac{60}{50 + 60} \cdot 75 \angle 0^\circ$$


$$V_T = V_A - V_B = 23 - j26.6 \text{ V}$$

* Finally,

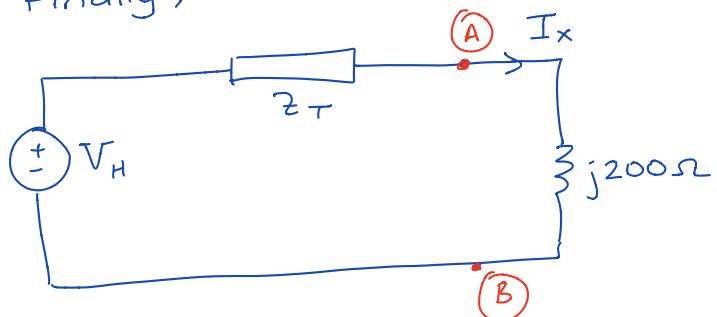

$$I_x = \frac{V_T}{Z_T + j200} = 0.18 \cdot e^{-j2.06} \text{ A} = 0.18 e^{-j118^\circ} \text{ A}$$

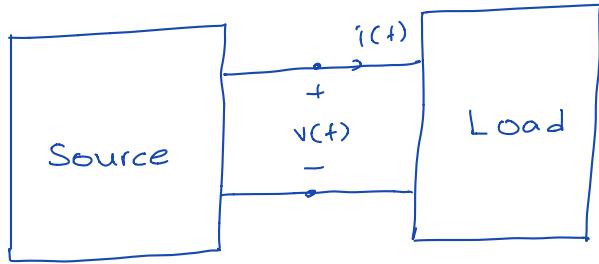Power and Energy in Sinusoidal Steady State



$$v(t) = V_m \cdot \cos(\omega t + \Delta V)$$

$$i(t) = I_m \cdot \cos(\omega t + \Delta I)$$

$p(t) = v(t) \cdot i(t) \Rightarrow$ instantaneous power delivered to the load

$$P_{\text{ave}} = \frac{1}{T} \int_0^T p(t) dt \Rightarrow \text{average power delivered to the load}$$

$$T = \frac{2\pi}{\omega}$$

$$p(t) = v(t) \cdot i(t) = V_m \cdot \cos(\omega t + \Delta V) \cdot I_m \cos(\omega t + \Delta I)$$

$$= \frac{1}{2} V_m \cdot I_m \left[\cos(2\omega t + \Delta V + \Delta I) + \cos(\Delta V - \Delta I) \right]$$

$$P_{\text{ave}} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \frac{1}{2} V_m \cdot I_m \cdot \cos(2\omega t + \Delta V + \Delta I) dt \quad \xrightarrow{\text{integrating over } 2 \text{ periods of } \cos(2\omega t + \dots)}$$

$$+ \frac{1}{T} \int_0^T \frac{1}{2} V_m \cdot I_m \cdot \cos(\Delta V - \Delta I) dt$$

constants

$$P_{\text{ave}} = \frac{1}{2} V_m \cdot I_m \cdot \cos(\Delta V - \Delta I)$$


called "power factor"

$$I_{\text{eff}} = \frac{I_m}{\sqrt{2}} = I_{\text{rms}} \quad , \quad V_{\text{eff}} = \frac{V_m}{\sqrt{2}} = V_{\text{rms}}$$

Then,

$$P_{\text{ave}} = I_{\text{eff}} \cdot V_{\text{eff}} \cdot \cos(\Delta V - \Delta I)$$

For resistive load :

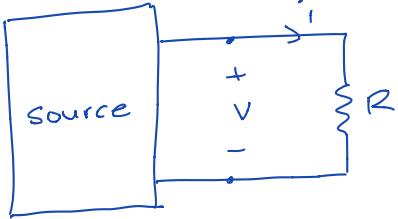

$$V = V_m \cdot e^{j\Delta V}$$

$$I = I_m \cdot e^{j\Delta I}$$


$$V = R I \Rightarrow V_m \cdot e^{j\Delta V} = R \cdot I_m \cdot e^{j\Delta I}$$

$$V_m = R \cdot I_m, \quad \Delta V = \Delta I$$

$$P_{ave} = \frac{1}{2} V_m \cdot I_m \cdot \cos(\Delta V - \Delta I) = \frac{1}{2} V_m \cdot I_m = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} I_m^2 \cdot R$$

$$= \frac{V_{eff}^2}{R} = I_{eff}^2 \cdot R$$

Capacitor :

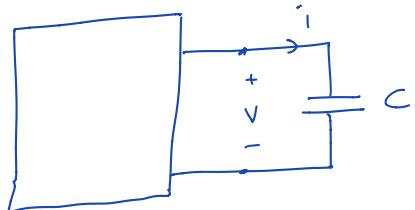

$$I = j\omega C \cdot V$$

$$I_m \cdot e^{j\Delta I} = j\omega C \cdot V_m \cdot e^{j\Delta V}$$


$\nwarrow j\pi/2$
 e

$$I_m = \omega C V_m, \quad \Delta I = \frac{\pi}{2} + \Delta V$$

$$P_{ave} = \frac{1}{2} V_m \cdot I_m \cdot \cos(\Delta V - \Delta I) = \frac{1}{2} \omega C V_m^2 \cdot \cos(-\pi/2) = 0$$

\Rightarrow capacitor does not dissipate power

Inductor :

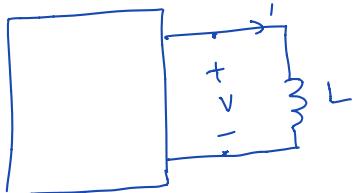

$$V = j\omega L \cdot I$$

$$V_m \cdot e^{j\Delta V} = j\omega L \cdot I_m \cdot e^{j\Delta I}$$


$\nwarrow j\pi/2$
 e

$$V_m = \omega L I_m, \quad \Delta V = \frac{\pi}{2} + \Delta I$$

$$P_{ave} = \frac{1}{2} V_m \cdot I_m \cdot \cos(\Delta V - \Delta I) = \frac{1}{2} \omega L I_m^2 \cos(\pi/2) = 0$$

\Rightarrow inductor does not dissipate power

In general

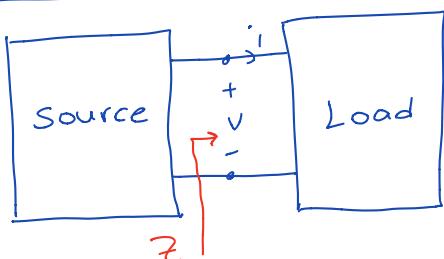

$$Z = \frac{V}{I} = \frac{V_m \cdot e^{j\Delta V}}{I_m \cdot e^{j\Delta I}} = \frac{V_m}{I_m} \cdot e^{j(\Delta V - \Delta I)}$$


$$\operatorname{Re}\{Z\} = \frac{V_m}{I_m} \cdot \cos(\Delta V - \Delta I)$$

power factor


$$y = \frac{1}{Z} = \frac{I}{V} = \frac{I_m}{V_m} \cdot e^{j(\Delta I - \Delta V)} \quad \text{cosine is an even function}$$

$$\operatorname{Re}\{y\} = \frac{I_m}{V_m} \cos(\Delta V - \Delta I) \quad \text{power factor}$$
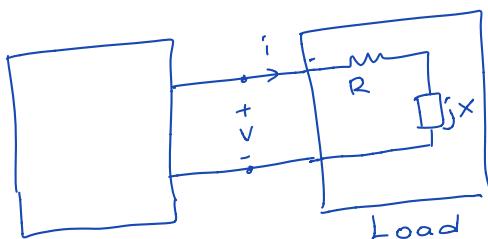
$$\begin{aligned} P_{\text{ave}} &= \frac{1}{2} V_m \cdot I_m \cdot \cos(\Delta V - \Delta I) \quad z = R + jX \\ &= \frac{1}{2} I_m^2 \cdot \operatorname{Re}\{z\} = I_{\text{eff}}^2 \cdot \operatorname{Re}\{z\} = I_{\text{eff}}^2 \cdot R \end{aligned}$$


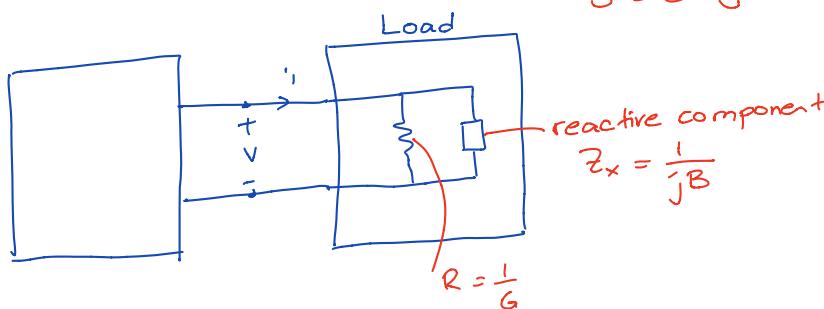
$$P_{\text{ave}} = \frac{1}{2} V_m^2 \cdot \operatorname{Re}\{y\} = V_{\text{eff}}^2 \cdot \operatorname{Re}\{y\} \quad y = G + jB$$



Alternative Way of Calculating Average Power


$$V = V_m \cdot e^{j\Delta V}, \quad I = I_m \cdot e^{j\Delta I}$$

$$S = \frac{1}{2} V \cdot I^* \Rightarrow \text{complex power}$$

$$\begin{aligned} P_{\text{ave}} &= \operatorname{Re}\{S\} = \operatorname{Re}\left\{\frac{1}{2} V \cdot I^*\right\} \\ &= \operatorname{Re}\left\{\frac{1}{2} V_m \cdot e^{j\Delta V} \cdot I_m \cdot e^{-j\Delta I}\right\} = \operatorname{Re}\left\{\frac{1}{2} V_m \cdot I_m \cdot e^{j(\Delta V - \Delta I)}\right\} \\ &= \frac{1}{2} V_m \cdot I_m \cdot \cos(\Delta V - \Delta I) \Rightarrow \text{same result as before} \end{aligned}$$

$$\begin{aligned}
 S &= \frac{1}{2} V_m \cdot I_m e^{j(\Delta V - \Delta I)} = V_{rms} \cdot I_{rms} \cdot e^{j\theta} \\
 &= \underbrace{\frac{1}{2} V_m \cdot I_m \cos(\theta)}_{P_{ave} : \text{actual}} + j \cdot \underbrace{\frac{1}{2} V_m \cdot I_m \sin(\theta)}_{Q : \text{"reactive power"} \text{ (in units of Volt-Amperes Reactive (VAR))}}
 \end{aligned}$$

Beer Analogy

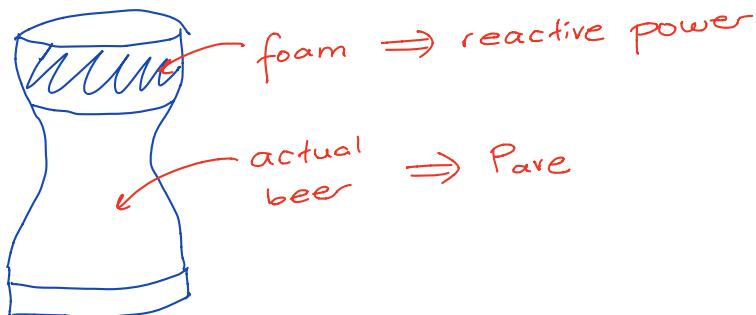


$|S| = \frac{1}{2} V_m \cdot I_m$: called "apparent power" in units of Volt-Ampere (VA)

Then, power factor = $\cos(\Delta V - \Delta I) = \frac{P_{ave}}{\text{Apparent Power}}$


* We want Q (reactive power) to be close to zero
 \Rightarrow make $(\Delta V - \Delta I)$ as small as possible.

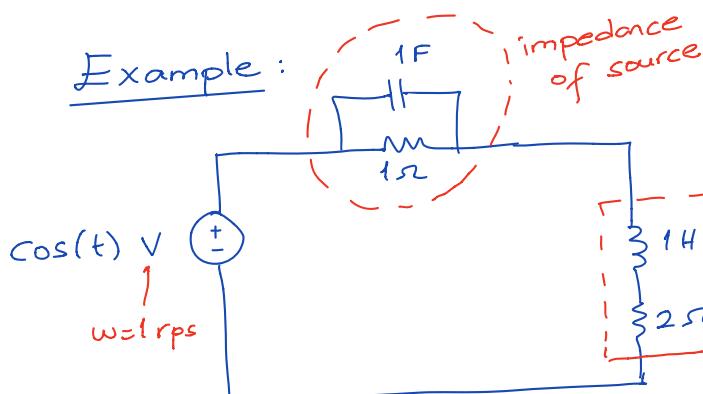Typically, Q is positive, because most loads are inductive overall.



Find power dissipated in Z_L .



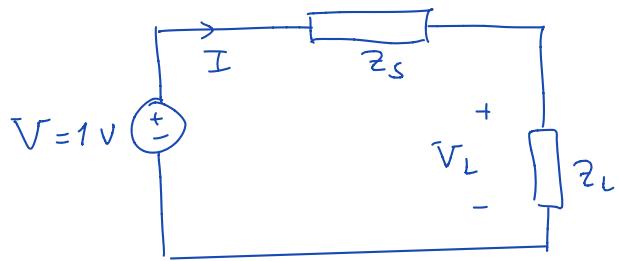

$$Y_S = 1 + j\omega C = 1 + j \quad (\text{s})$$

$$Z_S = \frac{1}{Y_S} = \frac{1}{1+j} = \frac{1-j}{2} \quad (\Omega)$$

$$Z_L = 2 + j\omega L = 2 + j \quad (\Omega)$$

$$Z_T = Z_S + Z_L = \frac{1-j}{2} + 2 + j = \frac{5+j}{2} \quad \Omega$$

$$I = \frac{V}{Z_T} = \frac{1}{\frac{5+j}{2}} = \frac{2}{5+j} \quad A$$

$$V_L = I \cdot Z_L = \frac{2(2+j)}{5+j} \quad V$$

$$* S = \frac{1}{2} V_L \cdot I^* = \frac{1}{2} \cancel{\frac{2(2+j)}{5+j}} \cdot \frac{2}{5-j} = \frac{2(2+j)}{26}$$

$$= \frac{2+j}{13} = \frac{2}{13} + j \frac{1}{13}$$


$$\operatorname{Re}\{S\} = P_{ave} = \frac{2}{13} \quad W$$

* Looking at 2Ω resistor only:


$$P_{ave} = \frac{1}{2} I_m^2 \cdot R = \frac{1}{2} \left| \frac{2}{5+j} \right|^2 \cdot 2 = \frac{4}{26} = \frac{2}{13} \quad W$$

same result

Maximum Power Transfer

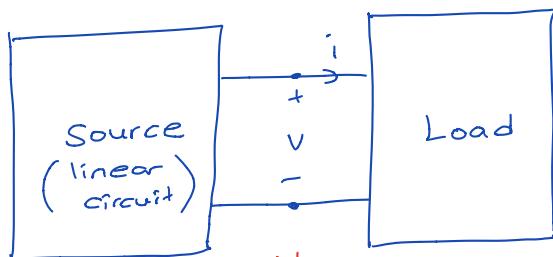

source : fixed
Load : variable

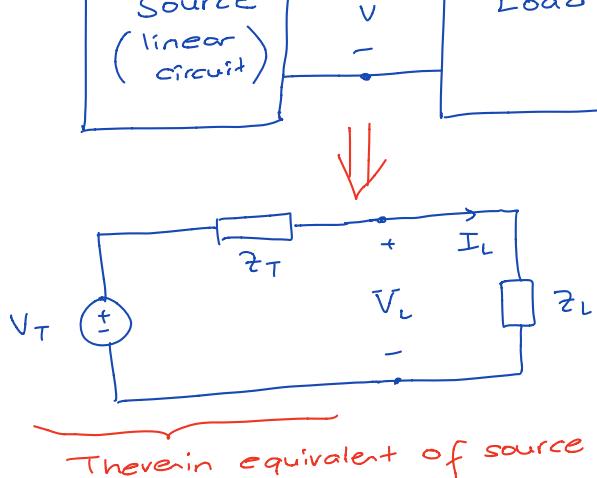

$$Z_T = R_T + j X_T$$

$$Z_L = R_L + j X_L$$

Thevenin equivalent of source

* maximum power is transferred to the load when

$$Z_L = Z_T^*$$

* Then, $I_L = \frac{V_T}{Z_T + Z_L} = \frac{V_T}{2R_T}$

$$P_{ave} = \frac{1}{2} |I_L|^2 \cdot R_T = \frac{1}{2} \frac{|V_T|^2}{4R_T^2} \cdot R_T = \boxed{\underline{\frac{|V_T|^2}{8R_T}} = P_{max}}$$