

"It ain't what you don't know that gets you into trouble.  
It is what you know for sure that just ain't so."

mark Twain

①

## CHAPTER 1 : INTRODUCTION

Circuit : An interconnection of electrical devices

Theory : A set of axioms, definitions, rules, techniques to understand a subject.


Our Aim : to predict the electrical behaviour of electrical systems.

To determine the electrical variables  $\rightarrow$  current, voltage, electrical power, and less importantly charge and flux.
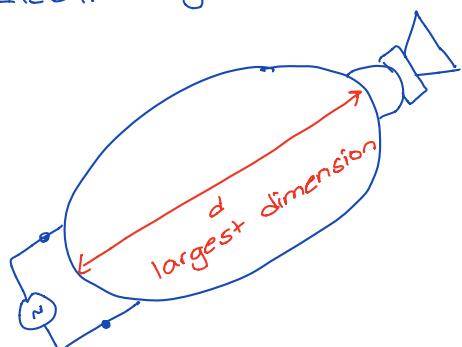
### What type of circuits?

Lumped-circuits

Electromagnetic waves travel at the speed of light




$\Delta t$  : maximum tolerable delay

$$d \ll c \cdot \Delta t$$

Lumped-circuits : propagation delays are not important

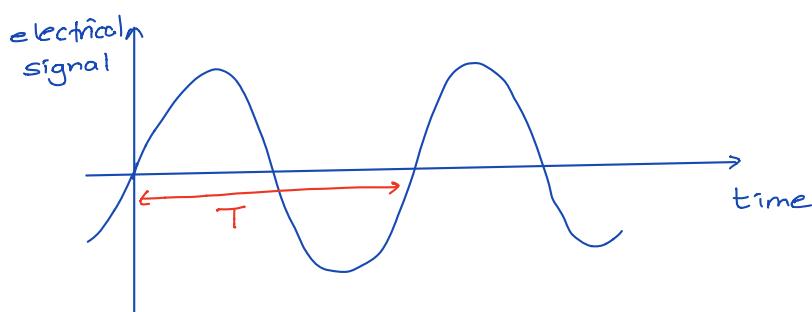$\Rightarrow$  electromagnetic effects occur instantaneously!



$$f = \frac{1}{T}$$

$$\Delta t \ll T$$

$$d \ll c T = \frac{c}{f} = \lambda \quad (\text{wavelength})$$

$$d \ll \lambda$$

In case signal contain many frequencies, choose the largest frequency  $\Rightarrow$  smallest wavelength:

$$d \ll \frac{c}{f_{\max}} = \lambda_{\min}$$

\* For audio circuits:

$$f_{\max} = 20 \text{ kHz} \Rightarrow \lambda = \frac{c}{f} \approx 15 \text{ km}$$

\* Other cases:

$$f_{\max} = 20 \text{ MHz} \Rightarrow \lambda = 15 \text{ m}$$

$$f_{\max} = 20 \text{ GHz} \Rightarrow \lambda = 15 \text{ mm}$$

Current: rate of change of the electrical charge passing through a cross-section in a part of circuit.

$$i = \frac{dq}{dt} \text{ in Amperes (A)} \Rightarrow A = \frac{\text{Charge}}{\text{Time}} = \frac{C}{sec}$$

Note: current can be positive or negative

Voltage: potential difference between two points A and B.

This is equivalent to the electrical work done against the electrical field to move a unit charge from B to A.

$$V = \frac{dw}{dq} \text{ in Volts (V)} \Rightarrow V = \frac{\text{Joule}}{\text{Coulomb}} = \frac{J}{C}$$

Note: voltage can be positive or negative

Electrical Power: the rate of change of electrical energy with respect to time


$$P = \frac{dw}{dt} = \frac{dw}{dq} \cdot \frac{dq}{dt} = V \cdot i \text{ in Watts (W)}$$

$$\Rightarrow W = \text{Volt} \times \text{Amp}$$

Note: power can be positive or negative
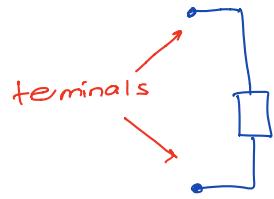
## Basic Terminology


Terminals: The joints where devices are accessible from outside.



We apply electrical excitations to terminals and measure electrical variables at terminals.


Electrical Circuits: Arbitrary interconnections of electrical devices through their terminals.

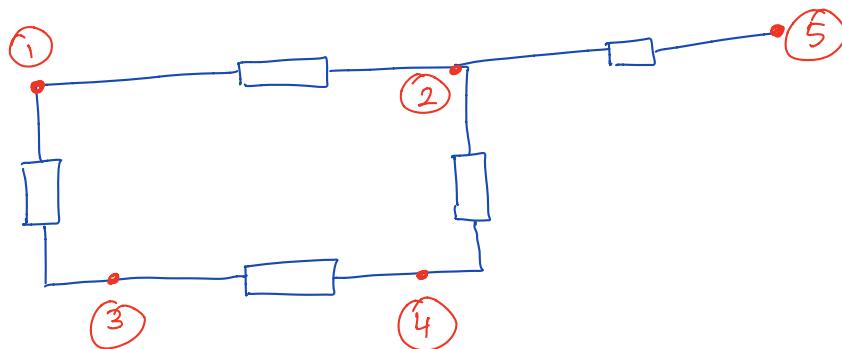\* Nodes: A junction in the circuit where the terminals are connected together, or any isolated terminal. If two terminals are connected by an electrical wire only, they form a single node.



Connected circuit: Any node can be reached from any other node by traversing a path through circuit elements.

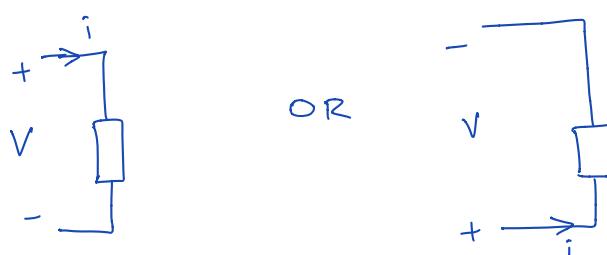\* Reference Directions: we will use passive sign convention.  
 $\Rightarrow$  the current flowing from (+) terminal to the (-) terminal of the device.



\*  $P = V \cdot i > 0$ , means the device is receiving power from the rest of the circuit.

$P = V \cdot i < 0$ , means the device is giving power to the rest of the circuit.

Voltage: defined as potential difference between two points.  
 Choose an arbitrary point as the reference point to measure voltages  $\Rightarrow$  called ground point


This can be done in any conservative field which has a potential (e.g., gravitation  $\rightarrow$  measure height  $\rightarrow$  reference point  $\rightarrow$  sea level)

We declare the potential of ground point as zero.

Node voltage: the voltage between any node and ground.

Then, we have:


$$V_{AB} = V_{AG} - V_{BG} = V_A - V_B$$

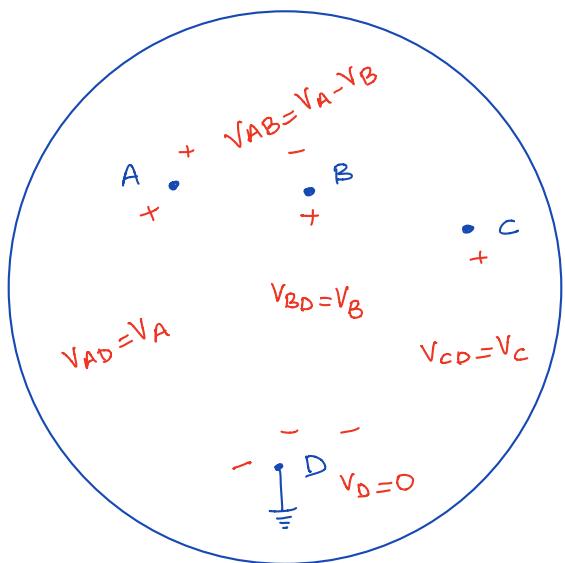

e.g.,  $V_{AB} = 50 \text{ V}$   $\Rightarrow$  point A has 50V more electrical potential than point B

$V_{AB} = -20 \text{ V}$   $\Rightarrow$  point A has 20V less " " than point B

Example :

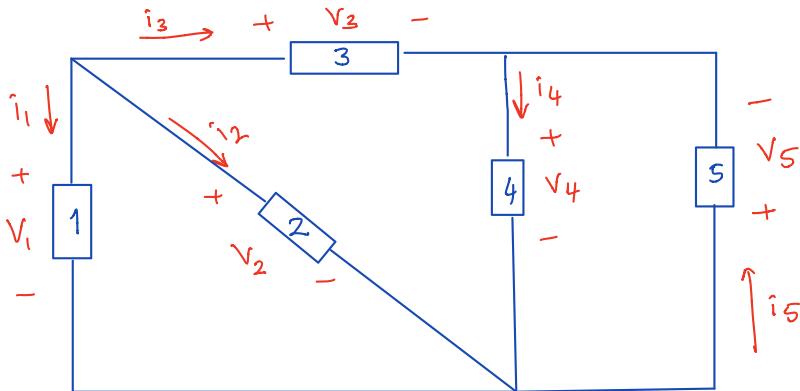

$$D_1 : V_1 = 100V, P_1 = -1W$$

$$D_2 : i_2 = 5mA, P_2 = 0.5W$$

$$D_3 : V_3 = 25V, i_3 = 5mA$$

$$D_4 : V_4 = 75V, P_4 = 0.75W$$

$$D_5 : V_5 = -75V, i_5 = 5mA$$

Are these devices giving or receiving power?

Find the missing variable ( $i, V, P$ ) for the devices.

\*  $D_1 : P_1 < 0 \Rightarrow D_1$  is giving power  
 $i_1 = \frac{P_1}{V_1} = -10mA$

\*  $D_2 : P_2 > 0 \Rightarrow D_2$  is receiving power  
 $V_2 = \frac{P_2}{i_2} = 100V$


\*  $D_3 : P_3 = i_3 \cdot V_3 = 0.125W > 0 \Rightarrow D_3$  is receiving power

\*  $D_4 : P_4 > 0 \Rightarrow D_4$  is receiving power  
 $i_4 = \frac{P_4}{V_4} = 10mA$


\*  $D_5 : P_5 = V_5 \cdot i_5 = -375mW < 0 \Rightarrow D_5$  is giving power

\* Note that  $P_1 + P_2 + \dots + P_5 = 0 \Rightarrow$  conservation of power  
 $\Rightarrow$  Tellegen's Theorem

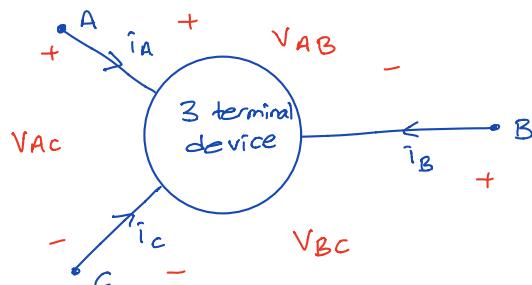\* Note : not all devices have 2 terminals.  
 we have 3 terminal (e.g., transistor), or  
 many terminal (OPAMP, integrated circuits, etc.).



## Devices and Models

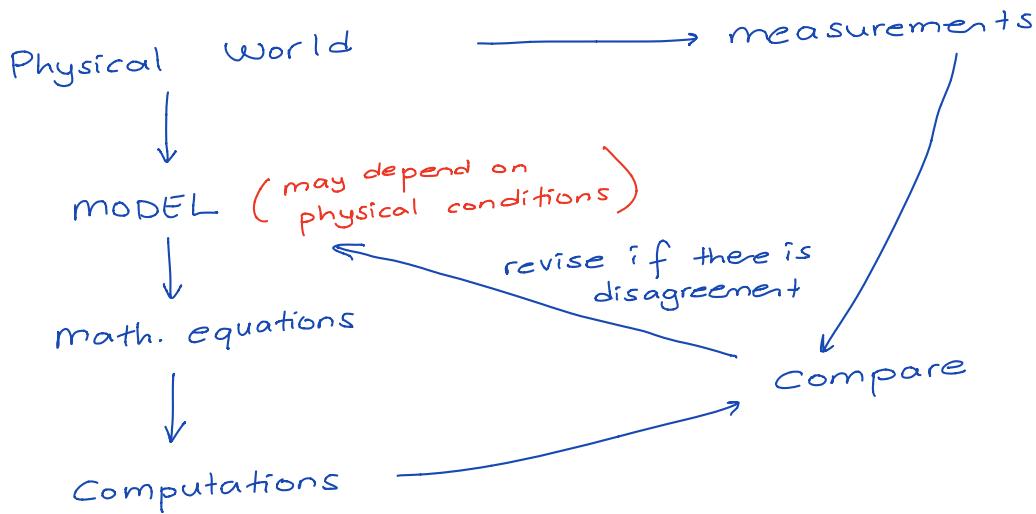

In Circuit Theory, we are interested in:

- the electrical behaviour of circuits, i.e., voltages, currents, electrical power
- external behaviour of devices (i.e., measured through terminals)
- not the internal behaviour of the device