

Ömer Morgül, F. Ömer İlday

NAME

FAMILYNAME

SECTION

## EEE 202 CIRCUIT THEORY


Final, Spring 2014-15

No credits will be given for unjustified answers. Good luck.


Problem 1	Problem 2	Problem 3	Problem 4	TOTAL

Prob. 1 : (20 pt.s)

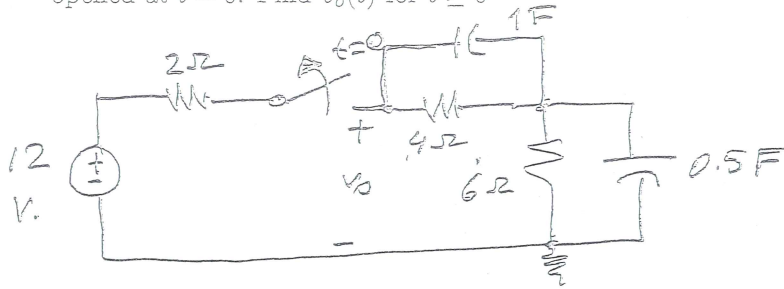i : (8 pt.s) Consider the following circuit. Switch is closed for a long time for  $t < 0$  and then is opened at  $t = 0$ . Find  $v_o(t)$  for  $t \geq 0$




$t < 0 \Rightarrow$  capacitors open

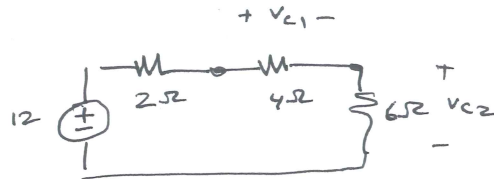

$$v_{c1} = \frac{4}{12} \cdot 12 = 4V$$

$$v_{c2} = \frac{6}{12} \cdot 12 = 6V$$

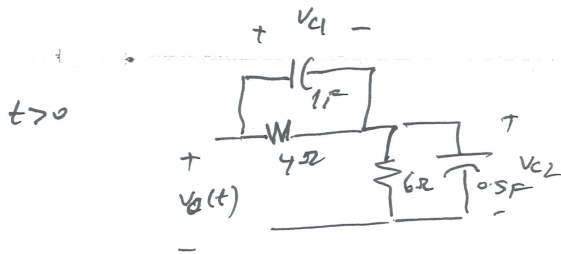

$$v_o(t) = v_{c1}(t) + v_{c2}(t)$$

$$v_{c1}(t) = 4 \cdot e^{-t/4} = 4e^{-t/4}$$


$$v_{c2}(t) = 6 \cdot e^{-t/0.5 \cdot 6} = 6e^{-t/3}$$

$$v_o(t) = 4e^{-t/4} + 6e^{-t/3} \quad t > 0$$

ii : (12 pt.s) Consider the following circuit. Assume that op-amps are linear and operate in the linear region. The input voltage  $v_i(t)$  is unit-step function. For simplicity, assume that all initial conditions are zero.

ii-1 Is it possible to have a damped sinusoid term (i.e. a term  $e^{-\alpha t} \cos(\omega t + \phi)$ ) at the output voltage  $v_o(t)$ ?

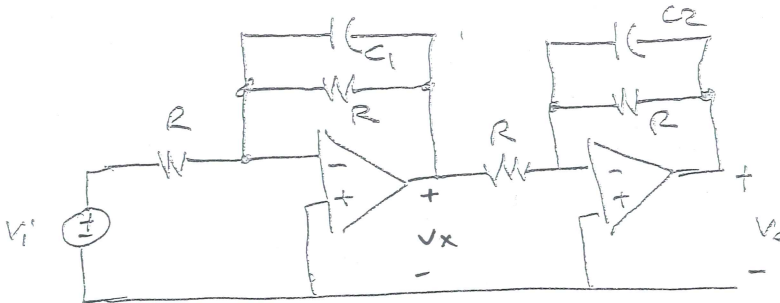ii-2 Let  $R = 1 \Omega$ ,  $C_1 = 1 F$ ,  $C_2 = 0.5 F$ . Find  $v_o(t)$ .



ii-1  $Y_1 = \frac{1}{R} + sC_1 = \frac{sCR + 1}{R}$   $Y_2 = \frac{1}{R} + sC_2 = \frac{sC_2R + 1}{R}$

$\frac{V_x}{V_i} = - \frac{Z_1}{R} = - \frac{1}{sCR + 1} = - \frac{1/CR}{s + 1/CR}$   $\frac{V_o}{V_x} = - \frac{Z_2}{R} = - \frac{1/C_2R}{s + 1/C_2R}$  (04)

$H(s) = \frac{V_o}{V_i} = \frac{1}{CR} \cdot \frac{1}{C_2R} \frac{1}{(s + 1/CR)(s + 1/C_2R)}$  (04)

$+V_i(s) = \frac{1}{s} \Rightarrow$  ALL POLES ARE REAL!  
NO COMPLEX POLES  
 $\Rightarrow$  DAMPED SINUSOIDS CANNOT EXIST!

ii-2

$V_o = \frac{2}{(s+1)(s+2)} \cdot \frac{1}{s} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+2}$  (04)

$k_1 = sV_o \Big|_{s=0} = \frac{2}{(s+1)(s+2)} \Big|_{s=0} = 1$  (01)

$k_2 = (s+1)V_o \Big|_{s=-1} = \frac{2}{s(s+2)} \Big|_{s=-1} = -2$  (01)

$k_3 = (s+2)V_o \Big|_{s=-2} = \frac{2}{s(s+1)} \Big|_{s=-2} = 1$  (01)


$\Rightarrow v_o(t) = 1 - 2e^{-t} + e^{-2t} \quad t \geq 0$

Prob. 2 : (25 pt.s) Consider the following circuit. Let  $v_C(0) = V_0$  and  $i_L(0) = I_0$  be given.

i : Find  $I_x(s)$  (in terms of  $V_i(s), V_0, I_0$ ).

ii : Let  $v_i(t)$  be a unit step function,  $V_0 = 0$  and  $I_0 = 0$ . Find  $i_x(t)$ .

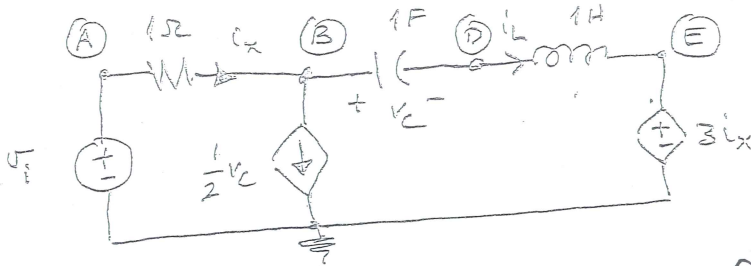iii : Find the node voltages of nodes B, D and E as  $t \rightarrow \infty$  (i.e. at the steady state).



i) (A)  $V_A = V_i$

(B)  $-V_A + (s+1)V_B - V_0 + \frac{1}{2}V_C = sV_B - 0$

(D)  $-sV_B + (s+\frac{1}{s})V_D - \frac{1}{s}V_E + V_0 + \frac{I_0}{s} = 0$

(E)  $V_E = 3I_x = 3(V_A - V_B)$

$V_C = V_B - V_D$

$$\Rightarrow \begin{cases} (s+\frac{3}{2})V_B - (s+\frac{1}{2})V_D = V_i + V_0 \\ (\frac{3}{s}-s)V_B + (s+\frac{1}{s})V_D = \frac{3}{s}V_i - V_0 - \frac{I_0}{s} \end{cases}$$

$$\Rightarrow \left[ \left( \frac{s^2+1}{s} \right) \frac{2s+3}{2} + \frac{2s+1}{2} \cdot \frac{3-s^2}{s} \right] V_B = \frac{s^2+1}{s} (V_i + V_0) + \frac{2s+1}{2} \left( \frac{3}{s}V_i - V_0 - \frac{I_0}{s} \right)$$

$$\Rightarrow \left( \frac{2s^2+8s+6}{2s} \right) V_B = \frac{2s^2+6s+5}{2s} V_i + \frac{2-s}{2s} V_0 - \frac{2s+1}{2s} I_0$$

$$\Rightarrow \left[ V_B = \frac{2s^2+6s+5}{2s^2+8s+6} V_i + \frac{2-s}{2s^2+8s+6} V_0 - \frac{2s+1}{2s^2+8s+6} I_0 \right]$$

$I_x = V_i - V_B$

$$\Rightarrow \left[ I_x = \frac{s+1/2}{s^2+4s+3} V_i + \frac{1/2s-1}{s^2+4s+3} V_0 + \frac{s+1/2}{s^2+4s+3} I_0 \right]$$

ii)  $I_x = \frac{s+1/2}{(s^2+4s+3)} \cdot \frac{1}{s} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+3}$


$k_1 = s I_x \Big|_{s=0} = \frac{s+1/2}{(s+1)(s+3)} \Big|_{s=0} = 1/6$

$k_2 = (s+1) I_x \Big|_{s=-1} = \frac{s+1/2}{s(s+3)} \Big|_{s=-1} = 1/4$

$k_3 = (s+3) I_x \Big|_{s=-3} = \frac{s+1/2}{s(s+1)} \Big|_{s=-3} = -5/12$

$$i_x(t) = \frac{1}{6} + \frac{1}{4}e^{-t} - \frac{5}{12}e^{-3t} \quad t \geq 0$$

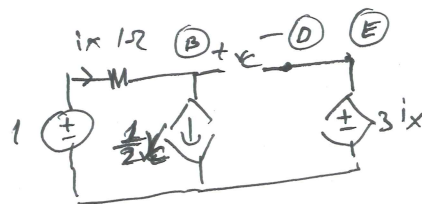iii) Capacitor  $\rightarrow$  open  
inductor  $\rightarrow$  short



$V_C = V_B - V_E \Rightarrow$

$$V_B = V_C + V_E = \frac{2}{6} + \frac{3}{6} = \frac{5}{6}$$

$I_x(\infty) = \frac{1}{6}$  (from above)

$i_x = \frac{1}{2}V_C \Rightarrow V_C = 2i_x = \frac{2}{6}$

$V_E = 3i_x = \frac{3}{6}$


$V_D = V_E = \frac{3}{6}$

Prob. 3 : (25 pt.s) Consider the following circuit. Assume that the op-amp is ideal and operates in the linear region. Assume zero initial conditions.

i : Find the transfer function  $H(s) = \frac{V_o(s)}{V_i(s)}$  in terms of  $R$  and  $C$ .

ii : Find and sketch  $|H(j\omega)|$ . If this circuit acts as a filter, determine its type.

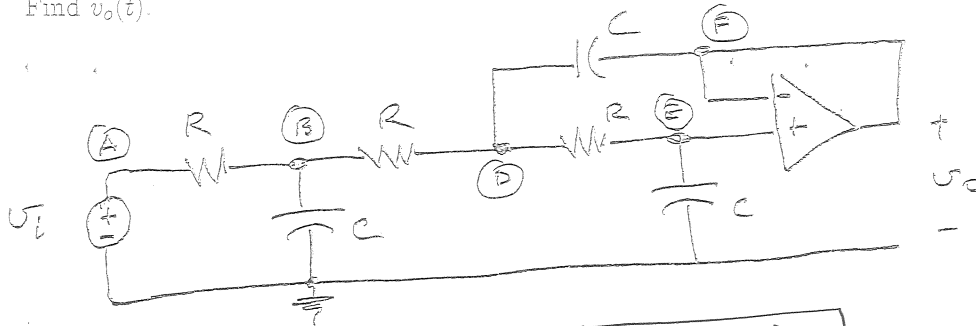iii : Let  $R = 1 \Omega$ ,  $C = 1 F$  and  $v_i(t) = \sin t V$ . Assume that the circuit is in sinusoidal steady-state. Find  $v_o(t)$ .



$$i) \begin{cases} V_E = V_F = V_o \\ V_A = V_i \end{cases}$$

$$\textcircled{E} \Rightarrow -\frac{V_D}{R} + \left(\frac{1}{R} + sC\right)V_o = 0 \Rightarrow \boxed{V_D = (sCR + 1)V_o}$$

$$\textcircled{D} \Rightarrow -\frac{V_B}{R} + \left(\frac{2}{R} + sC\right)V_D - \frac{V_o}{R} = 0 \Rightarrow V_B = (2 + sCR)V_D - V_o(1 + sCR)$$

$$V_B = [(2 + sCR)(sCR + 1) - (1 + sCR)]V_o = (1 + sCR)^2 V_o$$

$$\textcircled{B} \Rightarrow -\frac{V_i}{R} + \left(\frac{2}{R} + sC\right)V_B - \frac{V_D}{R} = 0 \Rightarrow V_i = (2 + sCR)V_B - V_D = [(2 + sCR)(1 + sCR)^2 - (1 + sCR)]V_o$$


$$\Rightarrow H(s) = \frac{V_o}{V_i} = \frac{1}{(sCR)^3 + 4(sCR)^2 + 4sCR + 1} = \frac{\frac{1}{(CR)^3}}{s^3 + \frac{4}{(CR)^2}s^2 + \frac{4}{CR}s + \frac{1}{(CR)^3}}$$

$$ii) |H(j\omega)| = \frac{\frac{1}{(CR)^3}}{\left| \frac{1}{(CR)^3} - \frac{4}{(CR)^2}\omega^2 + j\omega\left(\frac{4}{CR} - \omega^2\right) \right|} = \frac{\frac{1}{(CR)^3}}{\sqrt{\left(\frac{1}{(CR)^4} - \frac{4}{(CR)^2}\omega^2 + \omega^2\left(\frac{4}{CR} - \omega^2\right)^2\right)}}$$

$$|H(j0)| = 1$$

$$|H(j\infty)| = 0$$

$\Rightarrow$

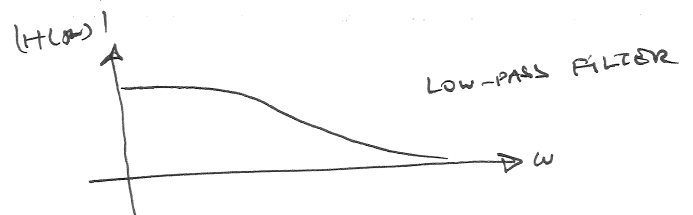

$$iii) RC=1 \Rightarrow H(s) = \frac{1}{s^3 + 4s^2 + 4s + 1} \quad V_i = 1 \cdot e^{-j\pi/2} \text{ (phase)}$$

$$\omega=1 \quad H(j1) = \frac{1}{-j + 4 + 4j + 1} = \frac{1}{-3 + 3j} = \frac{1}{3\sqrt{2}} e^{j135^\circ}$$

$$V_o = \frac{1}{3\sqrt{2}} e^{-j135^\circ} \cdot e^{-j90^\circ} = \frac{1}{3\sqrt{2}} e^{-j225^\circ}$$

$$\boxed{v_o(t) = \frac{1}{3\sqrt{2}} \cos(t - 225^\circ)}$$

Prob. 4 : (30 pt.s) A Wien bridge oscillator is a type of electronic oscillator that generates sine waves. The modern circuit is based on William Hewlett's 1939 Stanford University master's degree thesis. Hewlett eventually co-founded Hewlett-Packard, the first product of which was the HP200A, which is a precision Wien bridge oscillator. Note that there is no input signal (it is an oscillator, so not needed). Assume that the op-amp is ideal.

i : Let  $V_+$  and  $V_-$  denote the op-amp non-inverting and inverting terminal voltages, respectively. Find the transfer functions  $H_+(s) = \frac{V_+(s)}{V_o(s)}$  and  $H_-(s) = \frac{V_-(s)}{V_o(s)}$  in terms of resistor and capacitor values.

ii : Now assuming that the op-amp is in the linear region, by using the result obtained in i above, find a condition in terms of resistor and capacitor values such that this circuit shows a pure oscillation of the form  $v_o(t) = V_0 \cos \omega_0 t$ .

iii : For the case in ii, find the oscillation frequency  $\omega_0$  in terms of resistor and capacitor values.

iv : This circuit is a second order circuit. By using the results obtained in i and assuming that the op-amp operates in the linear region, obtain a second order ode for  $v_o$  in the form  $a\ddot{v}_o + b\dot{v}_o + cv_o = 0$ , where  $a, b, c$  depends on resistor and capacitor values.

