


CHAPTER 11 - NETWORK FUNCTION

$$\text{Network Function} = \frac{\{ \text{zero-state response of output} \}}{\{ \text{input} \}}$$

i.e., use zero-initial conditions.

$$H(s) = \frac{Y(s)}{X(s)} \Rightarrow \boxed{Y(s) = H(s) \cdot X(s)}$$

called "transfer function"

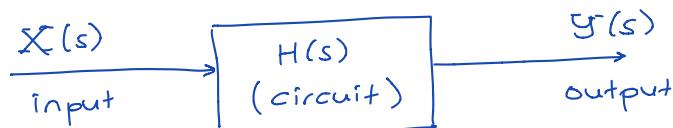

* If we know $H(s)$, we can find the output (zero-state response) when the input is specified.


$$\begin{aligned}
 Y(s) &= \underbrace{\frac{\text{poly. ins}}{\text{poly. ins}}}_{\substack{\text{N poles}}} \cdot \underbrace{\frac{\text{poly. ins}}{\text{poly. ins}}}_{\substack{\text{M poles}}} = \underbrace{\frac{\text{poly. ins}}{\text{poly. ins}}}_{\substack{\text{N+M poles}}} \\
 &= \sum_{i=1}^N \underbrace{\frac{k_i}{s-p_i}}_{\substack{\text{natural poles} \\ \text{from the circuit} \\ (H(s))}} + \sum_{l=1}^M \underbrace{\frac{k_l}{s-p_l}}_{\substack{\text{forced poles} \\ \text{from the input} \\ (X(s))}}
 \end{aligned}$$

partial fraction expansion

Then,

$$\begin{aligned}
 y(t) &= \sum_{i=1}^N k_i e^{p_i t} + \sum_{l=1}^M k_l e^{p_l t} \\
 &\quad \text{Natural response} \quad \text{forced response} \\
 &\quad (\text{decays to zero} \quad (\text{the part that may not decay}) \\
 &\quad \text{in a stable circuit}) \quad \Rightarrow \text{called steady-state response})
 \end{aligned}$$

Example :

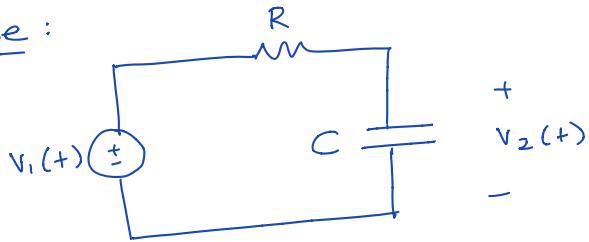

$$R = 10 \text{ k}\Omega$$

$$C = 10 \mu\text{F}$$

a) Find the transfer function $H(s) = \frac{V_2(s)}{V_1(s)}$

b) Find the zero-state response when

$$v_1(+) = 10 (1 - e^{-st}) u(t) \text{ V.}$$

$$\begin{aligned} a) H(s) &= \frac{V_2(s)}{V_1(s)} = \frac{\frac{1}{sc}}{\frac{1}{sc} + R} \quad (\text{voltage divider}) \\ &= \frac{1}{SRC+1} = \frac{1/RC}{s + 1/RC} = \frac{\frac{1}{10^4 \cdot 10^{-5}}}{s + \frac{1}{10^4 \cdot 10^{-5}}} = \boxed{\frac{10}{s+10}} \end{aligned}$$

$$b) v_1(+) = 10 u(t) - 10 \cdot e^{-st} u(t) \text{ V}$$

$$V_1(s) = \frac{10}{s} - \frac{10}{s+5} = \frac{50}{s(s+5)}$$

$$\text{So, } V_2(s) = H(s) \cdot V_1(s) = \frac{500}{s(s+5)(s+10)}$$

$$= \underbrace{\frac{k_1}{s}}_{\text{forced poles from } V_1(s)} + \underbrace{\frac{k_2}{s+5}}_{\text{natural pole from } H(s)} + \underbrace{\frac{k_3}{s+10}}$$

$$k_1 = s V_2(s) \Big|_{s=0} = \frac{500}{s \cdot 10} = 10$$

$$k_2 = (s+5) V_2(s) \Big|_{s=-5} = \frac{500}{-5 \cdot 5} = -20$$

$$k_3 = (s+10) V_2(s) \Big|_{s=-10} = \frac{500}{-10 \cdot (-5)} = 10$$


So,

$$V_2(t) = \left[10 - 20e^{-st} + 10 \cdot e^{-10t} \right] u(t) \text{ Volts}$$

forced response natural response

zero-state response

Example :

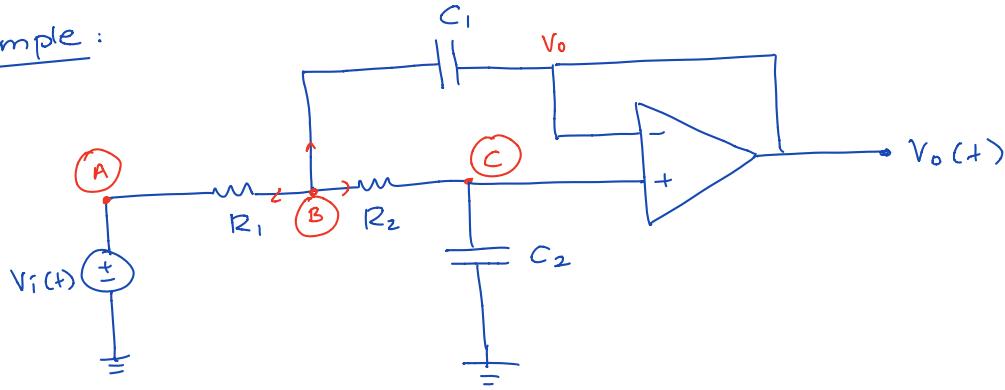

* Find $H(s) = \frac{V_o(s)}{V_i(s)}$

* If $R_1 = R_2 = 1\Omega$, $C_1 = 1F$, $C_2 = \frac{1}{2}F$

and $V_i(+)=u(t)$. Find $V_o(+)$, assuming zero initial conditions.

* Assume OPAMP is ideal and not saturated.

$$V_+ = V_- \Rightarrow V_c = V_o$$

KCL at B : $\frac{V_B - V_i}{R_1} + \frac{V_B - V_o}{R_2} + (V_B - V_o) \cdot sC_1 = 0$

$$V_B(R_1 + R_2 + sC_1 R_1 R_2) = R_2 V_i + (R_1 + sC_1 R_1 R_2) V_o$$

KCL at C : $V_c = V_o = \frac{\frac{1}{sC_2}}{\frac{1}{sC_2} + R_2} \cdot V_B = \frac{1}{sC_2 R_2 + 1} \cdot V_B$

$$V_B = (1 + sC_2 R_2) V_o$$

* Insert into the first equation:

$$(1 + sC_2 R_2)(R_1 + R_2 + sC_1 R_1 R_2) V_o = R_2 V_i + (R_1 + sC_1 R_1 R_2) V_o$$

$$\left[(R_1 + R_2) + sC_1 R_1 R_2 + sC_2 R_2 (R_1 + R_2) + s^2 C_1 C_2 R_1 R_2^2 - R_1 - sC_1 R_1 R_2 \right] V_o = R_2 V_i$$

$$\left[R_2 + sC_2 R_2 (R_1 + R_2) + s^2 C_1 C_2 R_1 R_2 \right] V_o = R_2 V_i$$

$$\left[1 + sC_2 (R_1 + R_2) + s^2 C_1 C_2 R_1 R_2 \right] V_o = V_i$$

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{1}{s^2 C_1 C_2 R_1 R_2 + s C_2 (R_1 + R_2) + 1}$$

$$H(s) = \frac{1}{s^2 + s \cdot \frac{1}{2} 2 + 1} = \boxed{\frac{2}{s^2 + 2s + 2}}$$

* $V_i(s) = \frac{1}{s}$

$$V_o(s) = H(s) \cdot V_i(s) = \frac{2}{s^2 + 2s + 2} \cdot \frac{1}{s}$$

$$s_{1,2} = \frac{-2 \pm \sqrt{4-8}}{2}$$

$$= -1 \pm j = -\alpha \pm j\beta$$


natural poles

$$= \frac{k_1}{s} + \frac{k}{s - (-1+j)} + \frac{k^*}{s - (-1-j)}$$

$$k_1 = s V_o(s) \Big|_{s=0} = \frac{2}{2} = 1$$

$$k = (s - (-1+j)) V_o(s) \Big|_{s=-1+j} = \frac{2}{(s - (-1-j))s} \Big|_{s=-1+j}$$

$$= \frac{2}{j(-1+j)} = \frac{1}{-1-j} = \frac{1}{\sqrt{2} \cdot e^{-j3\pi/4}} = \frac{1}{\sqrt{2}} e^{j3\pi/4} = |k| \cdot e^{j\theta}$$

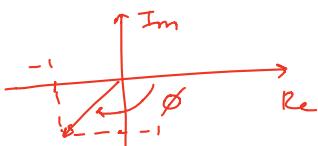

* So,

$$V_o(t) = \left[1 + \underbrace{\frac{2|k|}{\sqrt{2}} \cdot e^{-t} \cdot \cos(t + \frac{3\pi}{4})}_{\text{forced response}} \right] u(t) \quad V_o(t)$$

natural response

Network Function and Impulse Response

* Let input be an impulse. The zero-state response in this case is called "impulse response".

$$Y(s) = H(s) \cdot \underbrace{\mathcal{L}\{\delta(t)\}}_{=1} = H(s) \cdot 1 = H(s)$$

$$h(t) = \mathcal{L}^{-1}\{H(s)\} = \text{impulse response in time-domain}$$

$$\begin{aligned} * H(s) &= \frac{\text{poly. in } s}{\text{poly. in } s} = \frac{k_1}{s-p_1} + \frac{k_2}{s-p_2} + \dots + \frac{k_N}{s-p_N} \\ &= \sum_{i=1}^N \frac{k_i}{s-p_i} \quad \text{(natural poles)} \end{aligned}$$

(impulse does not introduce any forced poles)

Then,

$$h(t) = \left[\sum_{i=1}^N k_i e^{p_i t} \right] u(t)$$

natural response

If circuit is stable, $h(t)$ eventually decays to zero.

Important: $h(t)$ contains all the information needed to determine the circuit response to any other input.

$$y(t) = \mathcal{L}^{-1}\{H(s) \cdot X(s)\}$$

Step Response:

* The zero-state solution when the input is $u(t)$ is called "step response".

Remember: $U(s) = \frac{1}{s}$

* $Y(s) = H(s) \cdot U(s) = \frac{1}{s} H(s)$

$\downarrow \mathcal{L}^{-1}\{\cdot\}$

$$y(t) = \int_0^t h(\tau) d\tau$$

↑
step response = time integral of impulse response

$$\dot{y}(t) (= h(t)) = \frac{d}{dt} (\text{step response}) = \text{impulse response}$$

(except at discontinuities)


$$* Y(s) = \frac{1}{s} \cdot H(s) = \underbrace{\frac{k_0}{s}}_{\text{forced pole}} + \sum_{i=1}^N \underbrace{\frac{k_i}{s-p_i}}_{\text{natural poles}}$$

$$y(t) = k_0 \cdot u(t) + \left[\sum_{i=1}^N k_i \cdot e^{p_i t} \right] u(t)$$

forced response natural response

(called DC steady-state response)

Example :

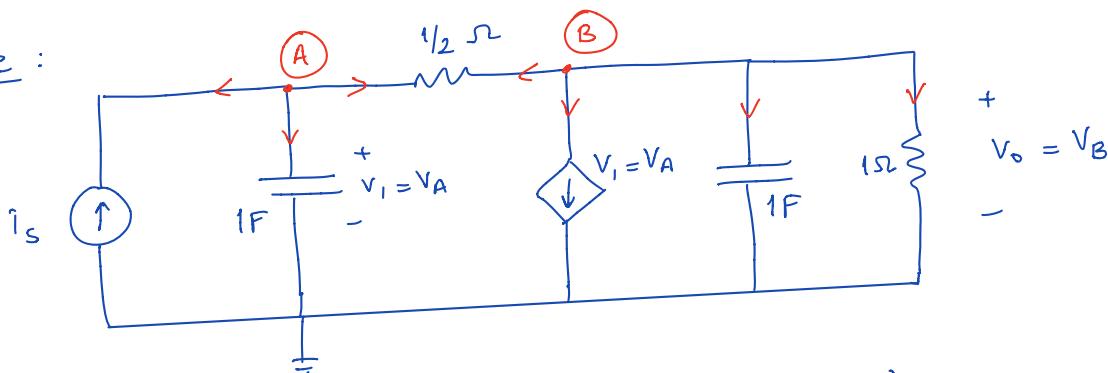

$$* \text{Find the transfer function : } H(s) = \frac{V_o(s)}{I_s(s)}$$

* Find the impulse response $h(t)$.

* Find the step response.

$$\text{KCL at A : } -I_s + \frac{V_A}{1 \cdot s} + \frac{V_A - V_B}{\frac{1}{2}} = 0$$

$$(s+2)V_A - 2V_B = I_s$$

$$\text{KCL at B : } \frac{V_B - V_A}{\frac{1}{2}} + V_A + \frac{V_B}{1 \cdot s} + \frac{V_B}{1} = 0$$

(7)

$$-\nabla_A + (s+3)\nabla_B = 0$$

$$\nabla_A = (s+3)\nabla_B$$

* Insert into first equation:

$$(s+2)(s+3)\nabla_B - 2\nabla_B = I_s$$

$$(s^2 + 5s + 4)\nabla_B = I_s$$

$$H(s) = \frac{V_o}{I_s} = \frac{\nabla_B}{I_s} = \boxed{\frac{1}{s^2 + 5s + 4}}$$

* $h(t) = \mathcal{L}^{-1}\{H(s)\}$

$$H(s) = \frac{1}{s^2 + 5s + 4} = \frac{1}{(s+1)(s+4)} = \frac{k_1}{s+1} + \frac{k_2}{s+4}$$

$$k_1 = (s+1)H(s) \Big|_{s=-1} = \frac{1}{3}$$


$$k_2 = (s+4)H(s) \Big|_{s=-4} = -\frac{1}{3}$$

Then,

$$h(t) = \left[\frac{1}{3} e^{-t} - \frac{1}{3} e^{-4t} \right] u(t)$$

↑
impulse response ↓
natural response

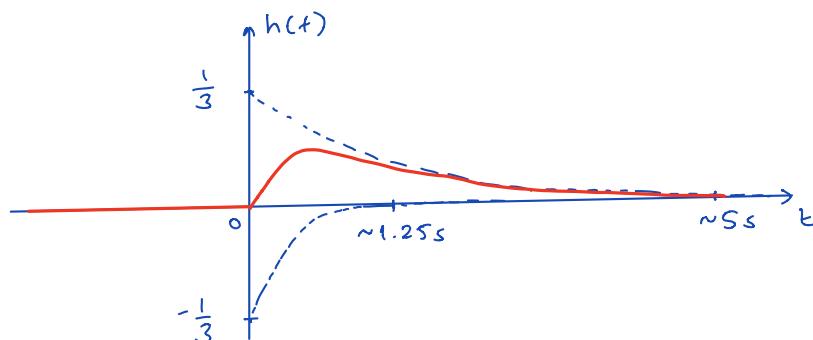$\tau_1 = \frac{1}{s} = 1 \text{ s}$ (dominant)
 $\tau_2 = \frac{1}{4} s = 0.25 \text{ s}$



$$* \quad i_s(t) = u(t)$$

$$I(s) = \frac{1}{s}$$

$$V_o(s) = H(s) \cdot I_s(s) = \frac{1}{s(s^2 + 5s + 4)} = \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+4}$$

$$k_1 = s V_o(s) \Big|_{s=0} = \frac{1}{4}$$


$$k_2 = (s+1) V_o(s) \Big|_{s=-1} = \frac{1}{-1 \cdot 3} = -\frac{1}{3}$$

$$k_3 = (s+4) V_o(s) \Big|_{s=-4} = \frac{1}{-4(-3)} = \frac{1}{12}$$

Then,

$$V_o(t) = \left[\frac{1}{4} - \frac{1}{3} e^{-t} + \frac{1}{12} e^{-4t} \right] u(t)$$

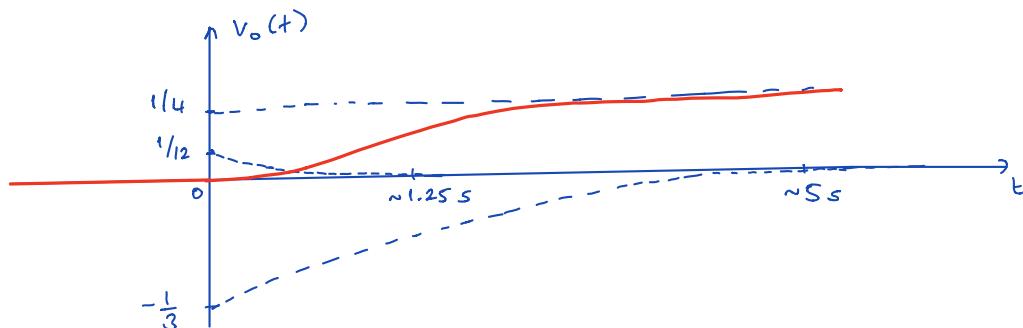↑
 step response forced resp. natural response



x Double check:

$$\begin{aligned} \frac{dV_o}{dt} &= \left[-(1) \cdot \left(-\frac{1}{3} \right) e^{-t} - \frac{4}{12} e^{-4t} \right] u(t) \\ &= \left[\frac{1}{3} e^{-t} - \frac{1}{3} e^{-4t} \right] u(t) = h(t) \quad \checkmark \end{aligned}$$

Impulse Response and Convolution

$$Y(s) = H(s)X(s)$$

$$y(t) = \mathcal{L}^{-1} \{ H(s) \cdot X(s) \}$$

(computed in s -domain,
followed by inverse Laplace transform)

* This corresponds to convolution in time-domain:

$$y(t) = \int_{0^-}^t h(t-\tau)x(\tau)d\tau = h(t) * x(t)$$

(computed
in time-domain)

Proof: $\mathcal{L} \{ y(t) \} = \mathcal{L} \left\{ \int_{0^-}^t h(t-\tau)x(\tau)d\tau \right\}$

zero if $\tau > t$

$\uparrow u(t-\tau)$

$$= \mathcal{L} \left\{ \int_{0^-}^{\infty} h(t-\tau)u(t-\tau)x(\tau)d\tau \right\}$$

$$= \int_{0^-}^{\infty} \left[\int_{0^-}^{\infty} h(t-\tau)u(t-\tau)x(\tau)d\tau \right] e^{-st} dt$$

$$= \int_{0^-}^{\infty} \left[\underbrace{\int_{0^-}^{\infty} h(t-\tau)u(t-\tau)e^{-st} dt}_{H(s) \cdot e^{-st}} \right] x(\tau)d\tau$$

(time-domain translation)

$$= \int_{0^-}^{\infty} H(s) e^{-st} x(\tau)d\tau$$

$$= H(s) \int_{0^-}^{\infty} x(\tau) e^{-s\tau} d\tau$$

$X(s)$

$$= H(s) \cdot X(s)$$

Example : $h(t) = 2e^{-t} u(t)$ \Rightarrow impulse response
 $x(t) = e^{-2t} u(t)$ \Rightarrow input

Find the zero-state response.

* $Y(s) = H(s) X(s)$

$$H(s) = \frac{2}{s+1}, \quad X(s) = \frac{1}{s+2}$$

$$Y(s) = \frac{2}{(s+1)(s+2)} = \underbrace{\frac{k_1}{s+1}}_{\text{natural pole}} + \underbrace{\frac{k_2}{s+2}}_{\text{forced pole}}$$

$$k_1 = (s+1) Y(s) \Big|_{s=-1} = \frac{2}{1} = 2$$

$$k_2 = (s+2) Y(s) \Big|_{s=-2} = \frac{2}{-1} = -2$$

$$y(t) = \mathcal{F}^{-1} \{ H(s) X(s) \} = \underbrace{2e^{-t}}_{\text{natural resp.}} - \underbrace{2e^{-2t}}_{\text{forced resp.}}, \quad t \geq 0$$

zero-state response

* Alternatively, we can use convolution:

$$y(t) = \int_0^t h(t-\tau) x(\tau) d\tau = \int_0^t 2e^{-(t-\tau)} u(t-\tau) e^{-2\tau} d\tau$$

always within the limits of the integral

$$= \int_0^t 2e^{-(t-\tau)} e^{-2\tau} d\tau = 2e^{-t} \int_0^t e^\tau \cdot e^{-2\tau} d\tau$$

$$= 2e^{-t} \int_0^t e^{-\tau} d\tau = 2e^{-t} \left[\frac{e^{-\tau}}{-1} \right] \Big|_0^t$$

$$= 2e^{-t} (-e^{-t} + 1) = -2e^{-2t} + 2e^{-t}$$

$$= 2e^{-t} - 2e^{-2t}, \quad \text{for } t \geq 0$$

\Rightarrow same result as before

Relation with Sinusoidal Steady State

$$H(s) = \frac{Y(s)}{X(s)} \Rightarrow Y(s) = H(s) \cdot X(s) \quad (\text{zero-state response})$$

* Assume that the input $x(t)$ is sinusoidal:

$$x(t) = X_m \cos(\omega t + \phi) = \operatorname{Re} \left\{ X_m e^{j\phi} e^{j\omega t} \right\} = \operatorname{Re} \left\{ \hat{X} e^{j\omega t} \right\}$$

$$= \frac{1}{2} \hat{X} e^{j\omega t} + \frac{1}{2} \underbrace{\hat{X}^* e^{-j\omega t}}_{\text{complex conjugate}}, \text{ where } \underbrace{\hat{X}}_{\text{phasor}} = X_m e^{j\phi}$$

$$\int \{x(t)\} = \frac{1}{2} \hat{X} \frac{1}{s-j\omega} + \frac{1}{2} \hat{X}^* \frac{1}{s+j\omega} = X(s)$$

$$Y(s) = H(s) \cdot X(s)$$

$$= H(s) \cdot \left\{ \underbrace{\frac{1}{2} \hat{X} \frac{1}{s-j\omega}}_{N \text{ natural poles}} + \underbrace{\frac{1}{2} \hat{X}^* \frac{1}{s+j\omega}}_{2 \text{ forced poles}} \right\}$$

partial fraction expansion

$$= \sum_{i=1}^N \underbrace{\frac{k_i}{s-p_i}}_{\text{natural poles from } H(s)} + \underbrace{\frac{k}{s-j\omega}}_{\text{forced poles from } X(s)} + \underbrace{\frac{k^*}{s+j\omega}}_{\text{forced poles from } X(s)}$$

$$k = (s-j\omega) Y(s) \Big|_{s=j\omega} = H(s) \cdot \left\{ \frac{1}{2} \hat{X} \frac{s-j\omega}{s+j\omega} + \frac{1}{2} \hat{X}^* \frac{s-j\omega}{s+j\omega} \right\} \Big|_{s=j\omega}$$

$$= H(j\omega) \cdot \left\{ \frac{1}{2} \hat{X} + \frac{1}{2} \hat{X}^* \cdot \frac{0}{2j\omega} \right\}$$

$$= \frac{1}{2} H(j\omega) \hat{X}$$

so,

$$y(t) = \sum_{i=1}^N k_i e^{p_i t} + \frac{1}{2} H(j\omega) \hat{X} \cdot e^{j\omega t} + \frac{1}{2} H^*(j\omega) \hat{X}^* \cdot e^{-j\omega t}$$

natural resp. forced resp.

$$= \sum_{i=1}^N k_i \cdot e^{p_i t} + \operatorname{Re} \left\{ \underbrace{H(j\omega) \hat{X}}_{\text{output phasor}} e^{j\omega t} \right\}$$

forced resp.
sinusoidal steady-state resp.

$$\text{where } H(j\omega) = |H(j\omega)| \cdot e^{j\angle H(j\omega)}$$

$$= \sum_{i=1}^N k_i \cdot e^{p_i t} + \operatorname{Re} \left\{ |H(j\omega)| e^{j\angle H(j\omega)} \cdot X_m \cdot e^{j\phi} \cdot e^{j\omega t} \right\}$$

$$= \quad " \quad + \operatorname{Re} \left\{ |H(j\omega)| X_m \cdot e^{j(\omega t + \phi + \angle H(j\omega))} \right\}$$

$$= \quad " \quad + |H(j\omega)| X_m \cdot \cos(\omega t + \phi + \angle H(j\omega))$$

natural resp.
(this will decay down to zero for stable case)

sinusoidal steady-state resp.
(same as in phasor analysis)

* Evaluate $H(s)$ at $j\omega$ to find the transfer function in phasor domain.

$$\text{Output phasor} = H(j\omega) \cdot \hat{X}$$

$$\text{Transfer function in phasor domain} = \frac{\text{output phasor}}{\text{input phasor}} = \frac{H(j\omega) \cdot \hat{X}}{\hat{X}}$$

$$= \boxed{H(j\omega) = H(s) \Big|_{s=j\omega}}$$

* So, phasor analysis reveals the steady-state (i.e., forced) response for the case of sinusoidal inputs.