

EE 202 - HW3 Solutions.

$$8.8) V_1 = 5 + j5 = 5\sqrt{2} \angle 45^\circ \Rightarrow v_1(t) = 5\sqrt{2} \cos(\omega t + 45^\circ) \text{ V}$$

$$V_2 = 3(8 - j6) = 30 \angle -36.8^\circ \Rightarrow v_2(t) = 30 \cos(\omega t - 36.8^\circ) \text{ V}$$

$$I_1 = 12 + j5 - 5j = 12 \angle 0^\circ \Rightarrow i_1(t) = 12 \cos(\omega t) \text{ mA}$$

$$I_2 = \frac{330 + j810}{2200 - j560} = \frac{874.6 \angle 67.8^\circ}{2270.1 \angle -14.3^\circ} = 0.385 \angle 82.1^\circ \Rightarrow i_2(t) = 0.385 \cos(\omega t + 82.1^\circ) \text{ A}$$

$$8.9) (a) V_1 = 10 \angle 90^\circ \Rightarrow V_2 = \frac{1}{100} j(100) V_1 + 20 V_1 = (20 + j) 10 \angle 90^\circ = 200.2 \angle 92.8^\circ$$

$$\Rightarrow v_2(t) = 200.2 \cos(100t + 92.8^\circ)$$

$$(b) I_1 = 4 \angle 180^\circ \Rightarrow I_2 = \frac{10}{j5} I_1 - 3 I_1 = (-j2 - 3) 4 \angle 180^\circ = 14.4 \angle 33.7^\circ$$


$$\Rightarrow v_2(t) = 14.4 \cos(5t + 33.7^\circ)$$

$$8.27) \omega = 10^3 \text{ rad/s}$$

Both Z & Y should be real values.


$$Y = \frac{1}{Z} = j\omega C + \frac{1}{100 + j\omega L} = j1000C + (0.0099 - 0.00099j)$$
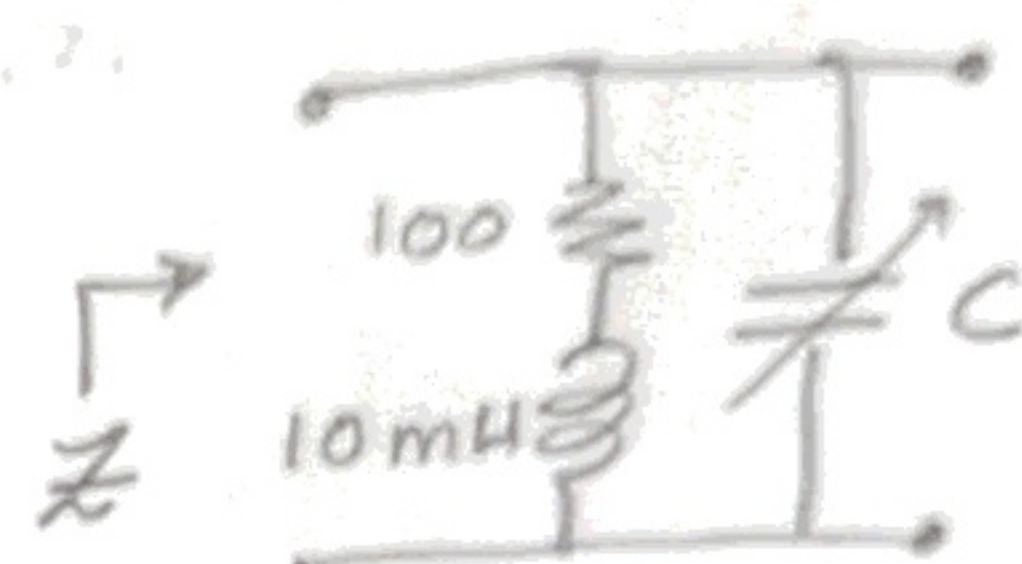
$$\text{imaginary} = 0 \Rightarrow C = 0.99 \times 10^{-6} \text{ F}$$



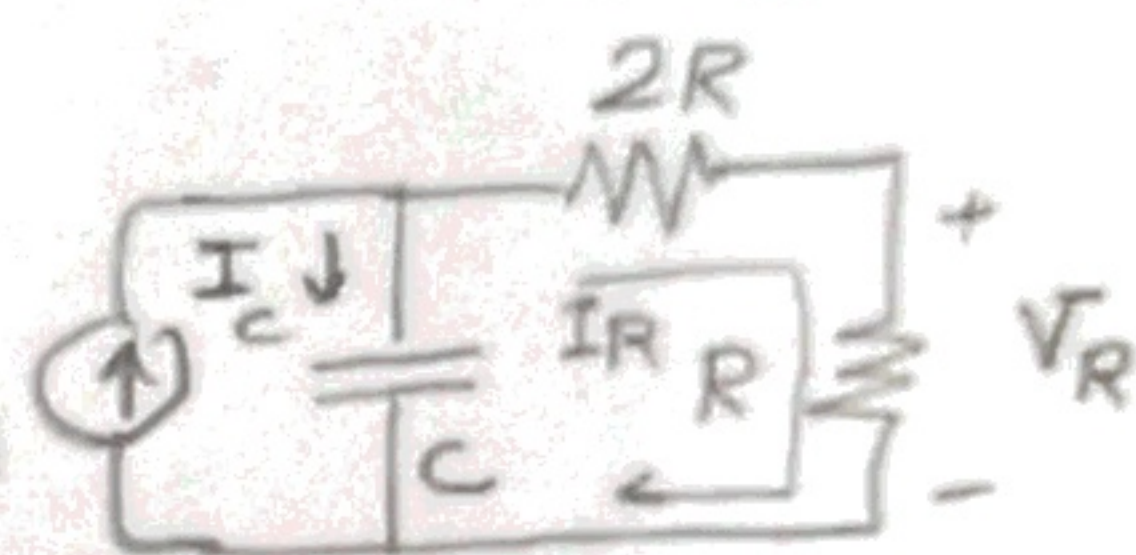8.37) We can use current division formula consisting of two branches, one C and another one 3R, to find branch currents.

$$I_C = I_A \frac{3R}{3R + 1/j\omega C} = \frac{jI_A 3R\omega C}{1 + j\omega 3RC} \quad \& \quad V_R = RI_R = R \frac{1/j\omega C}{3R + 1/j\omega C} I_A = \frac{RIA}{1 + j\omega 3RC} = I_A$$




8.46) (a) Using transfer function $H(j\omega) = \frac{V_x}{V_s} = \frac{1/j\omega C}{1/j\omega C + R}$, we can plug the element values and given frequencies to carry out v_x phasor:

$$1) \omega = 1500 \text{ \& } v_m = 5 \Rightarrow V_{x1} = 5 \angle 0^\circ \times \frac{1}{1 + j1500 \times 2 \times 10^{-6} \times 500} = 2.77 \angle -56.3^\circ$$

$$2) \omega = 500 \text{ \& } v_m = 10 \Rightarrow V_{x2} = 10 \angle 0^\circ \times \frac{1}{1 + j500 \times 2 \times 10^{-6} \times 500} = 8.94 \angle -26.5^\circ$$
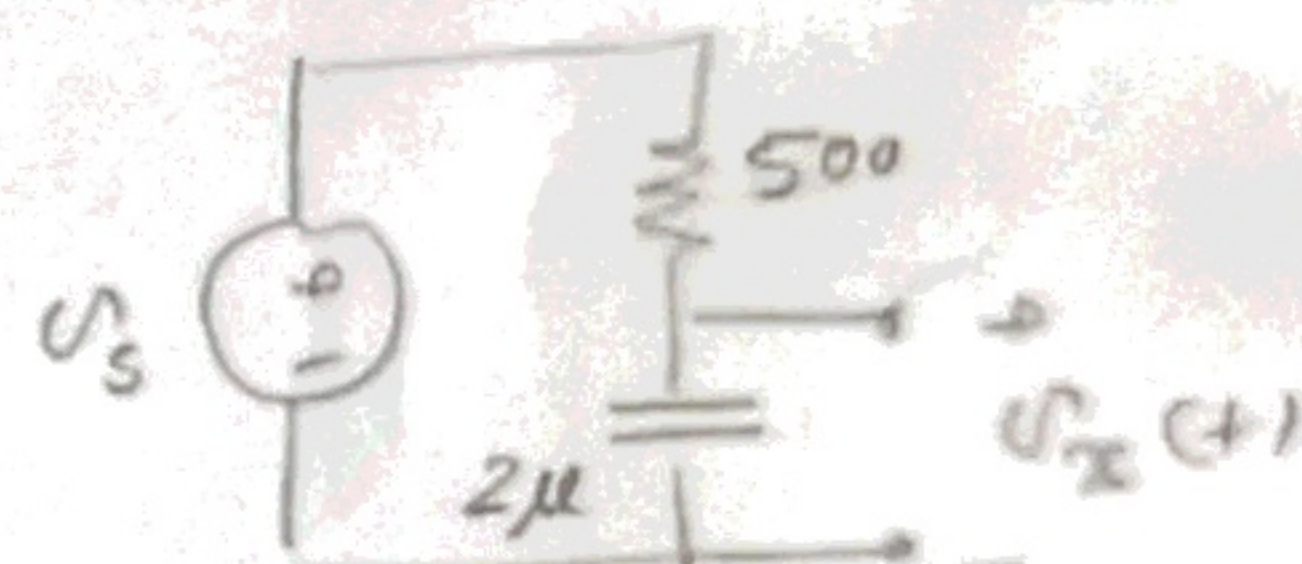
$$\Rightarrow v_x(t) = 2.77 \cos(1500t - 56.3^\circ) + 8.94 \cos(500t - 26.5^\circ)$$



$$8.68) v_s(t) = 100 \sin(10^4 t) \Rightarrow V_s = 100 e^{-j\pi/2} = 100 \angle -90^\circ$$


Using mesh analysis: $V_s = 1K(I_A - I_C) + j\omega L(I_A - I_B)$

$$I_C = -2I_2$$

$$\begin{cases} -j\omega L(I_A - I_B) + 1/j\omega C(I_B - I_C) + 2K I_B = 0 \\ I_C = -2(I_A - I_B) \end{cases}$$

$$\Rightarrow \begin{cases} -100j = (3000 + 100j) I_A - (2000 + 100j) I_B \\ -(2000 + 2600j) I_B - 5100j I_A = 0 \end{cases} \Rightarrow \begin{cases} I_A = 0.049 \angle -18.17^\circ \\ I_B = 0.077 \angle 19.39^\circ \end{cases} \Rightarrow I_C = 0.096 \angle 58.05^\circ$$
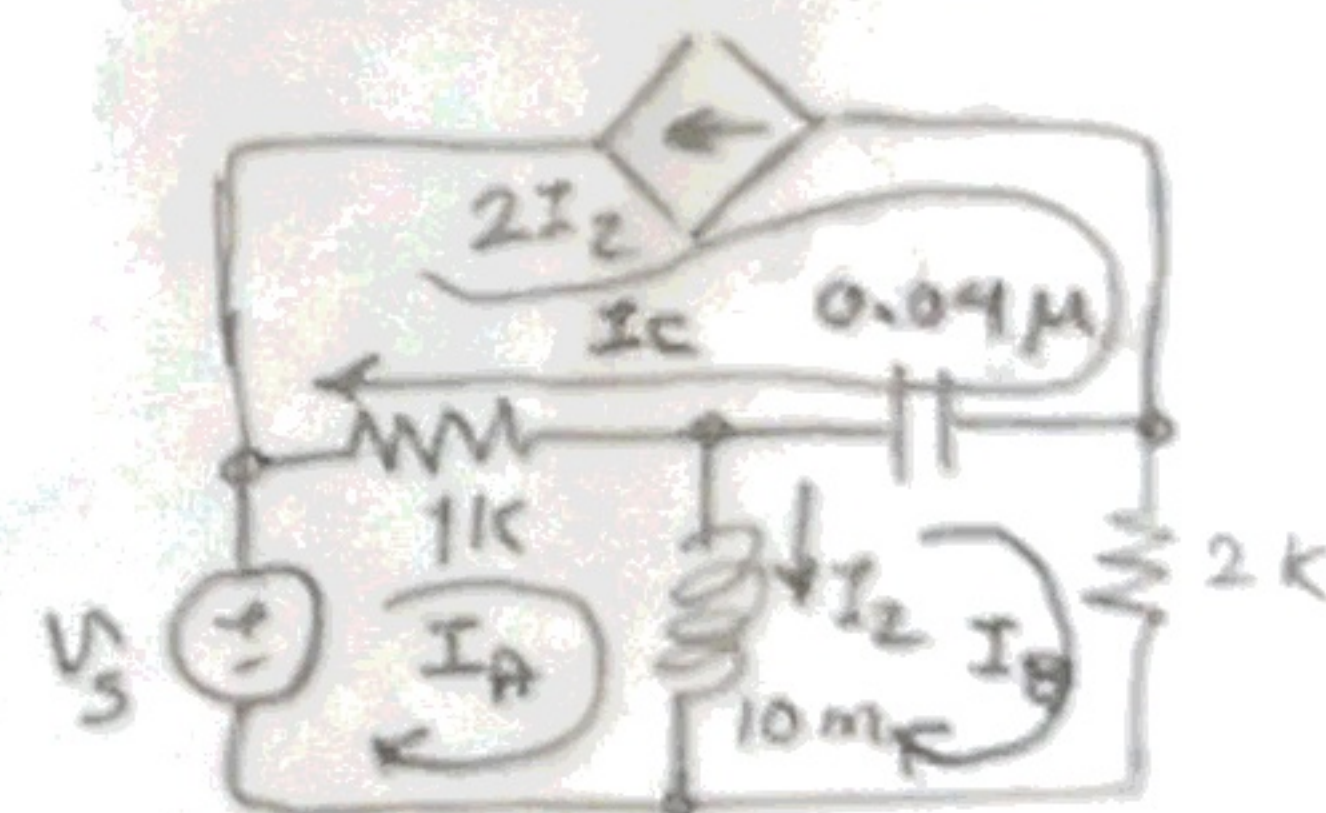
$$\Rightarrow I_1 = I_A - I_C = 0.097 \angle -92.4^\circ \quad \& \quad I_2 = I_A - I_B = 0.048 \angle -121.9^\circ \quad \& \quad I_3 = I_B$$



8.70) (a) KCL @ negative terminal assuming op-amp in linear mode: $V_s/Z = (V_o - V_s)/Z_F$


$$\Rightarrow \frac{V_o}{V_s} = \frac{(Z + Z_F)}{Z}, \text{ where } \begin{cases} Z_F = R_2 \\ Z = R_1 + 1/j\omega C \end{cases} \Rightarrow \frac{V_o}{V_s} = \frac{R_2 + R_1 + 1/j\omega C}{R_1 + 1/j\omega C} = \frac{(R_1 + R_2)j\omega C + 1}{R_1 j\omega C + 1} = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{j\omega + \frac{1}{C(R_1 + R_2)}}{j\omega + \frac{1}{R_1 C}} \right)$$

8.77) Attach a test source V_s and find related I_s . Writing KCL at input:

$$\frac{V_s - 10V_x}{1K} + \frac{V_s - 140}{2K + j2K} = I_s$$

$$\text{KCL @ } V_x: \frac{V_x - 140}{2K} = \frac{V_s - V_x}{j2K} \Rightarrow V_x = \frac{(1+j)}{2} (1 - jV_s)$$
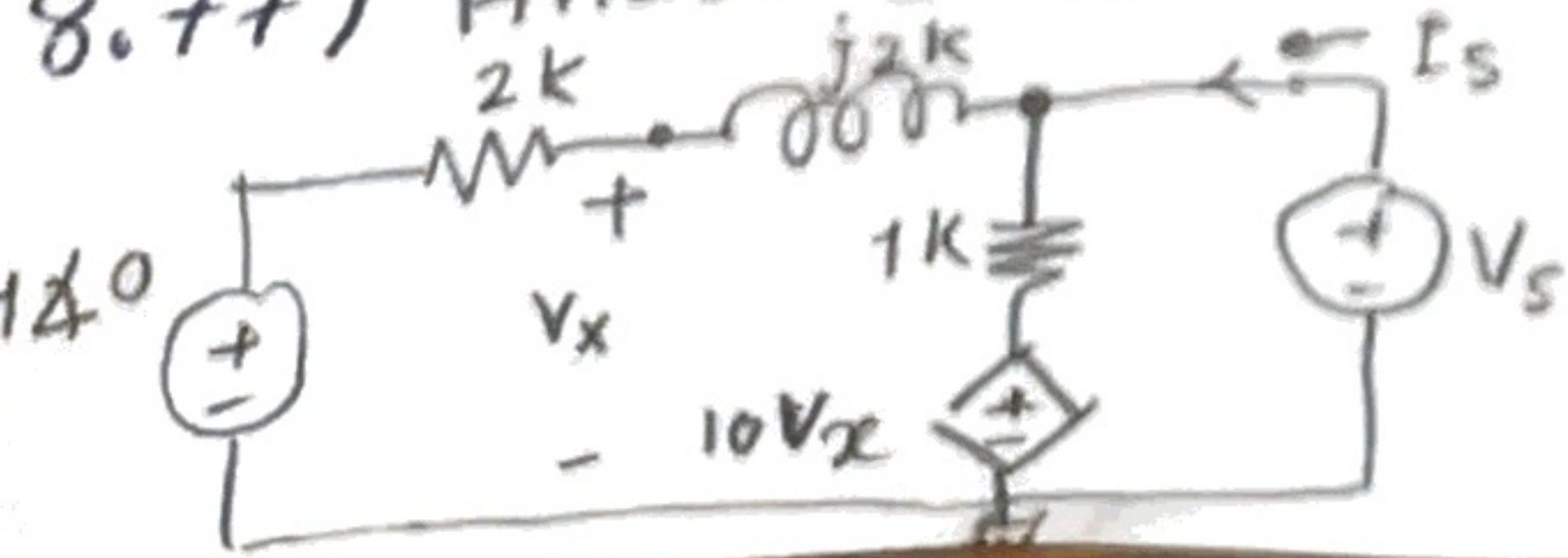
$$\Rightarrow V_s = \frac{(0.078 - j1.16)}{V_T} + \frac{(-0.102 - j0.13)}{Z_T (K\Omega)} I_s$$




$$8.93) V_s = 880 \angle 0$$

$$I_s = \frac{V_s}{0.4 \times 2 + j5 \times 2 + 50 + j150} = 5.24 \angle -72.38^\circ \text{ A}$$

$$P_{\text{wire}} = \frac{1}{2} |I_s|^2 \operatorname{Re}\{Z_{\text{wire}}\} = \frac{1}{2} \times 5.24^2 \times (0.4 \times 2) = 10.991$$

$$P_{\text{Load}} = \frac{1}{2} |I_s|^2 \operatorname{Re}\{Z_{\text{Load}}\} = \frac{1}{2} \times 5.24^2 \times 50 = 686.996$$
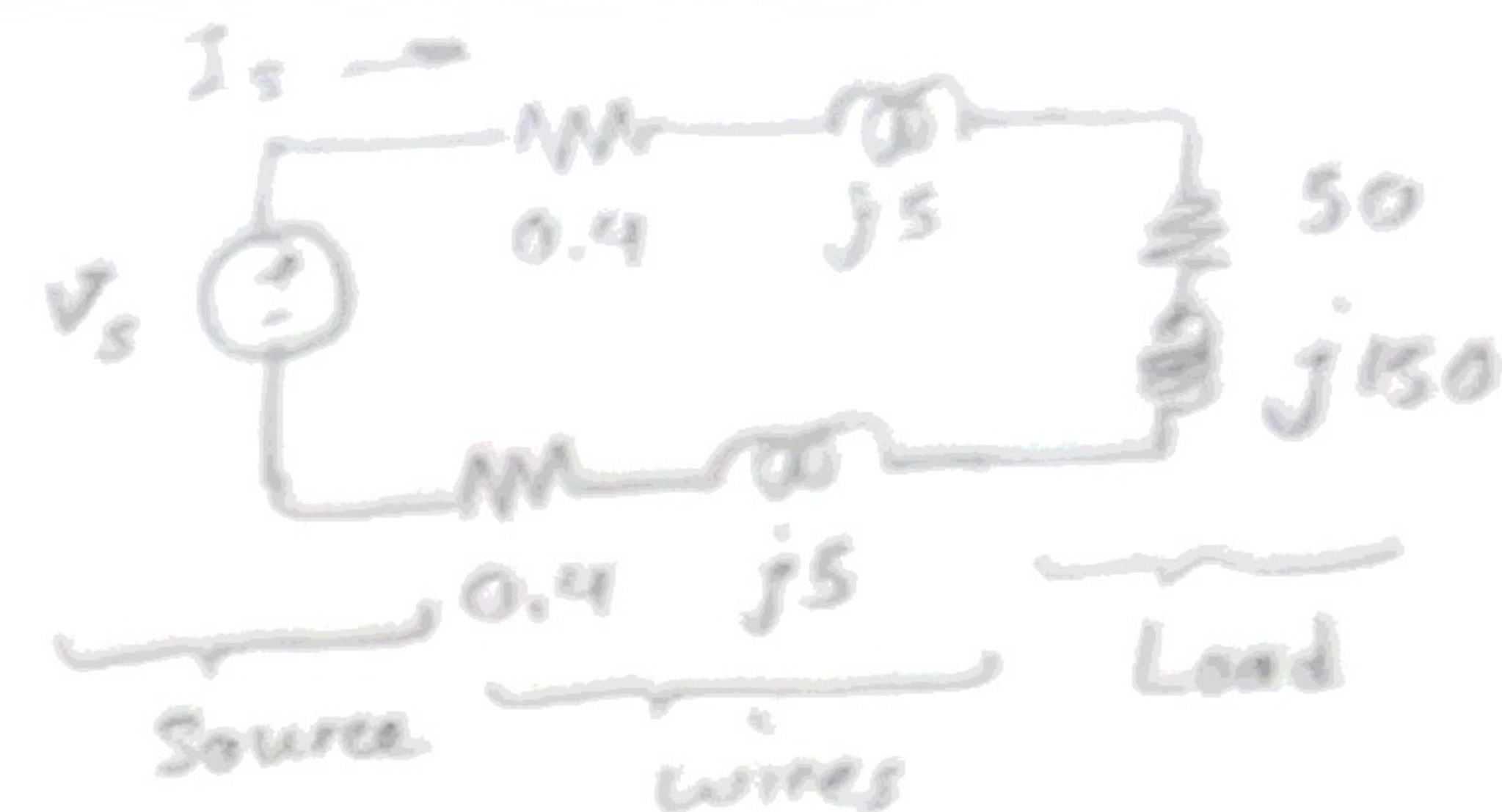
$$P_{\text{Source}} = \operatorname{Re}\left\{\frac{1}{2} V_s I_s^*\right\} = \operatorname{Re}\left\{\frac{1}{2} 880 \times 5.24 \angle 72.38^\circ\right\} = 697.988$$



$$\Rightarrow \eta = P_{\text{Load}} / P_{\text{Source}} = 98.4\%$$

* It is seen that: $P_{\text{Source}} = P_{\text{Wire}} + P_{\text{Load}}$