



EEE 202 CIRCUIT THEORY
Second Midterm, Spring 2012-13

No credits will be given for unjustified answers.


Prob. 1 : (20 pt.s) Consider the following circuit. Let $i_L(0) = 1$ Amps.

i : Find $i_L(t)$.

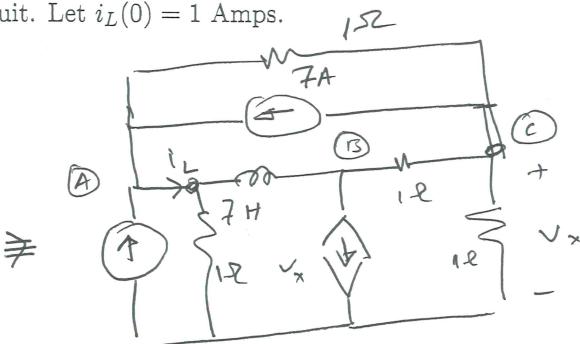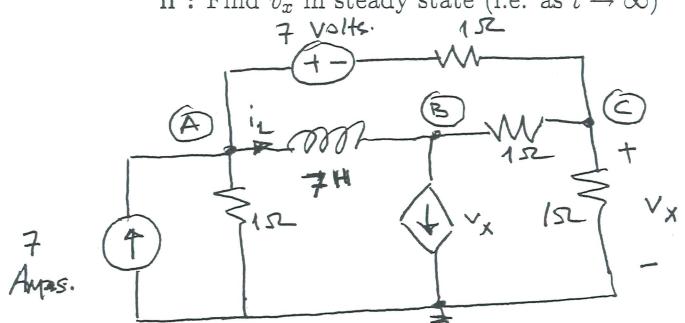ii : Find v_x in steady state (i.e. as $t \rightarrow \infty$)



Find i_{SC} (steady state)

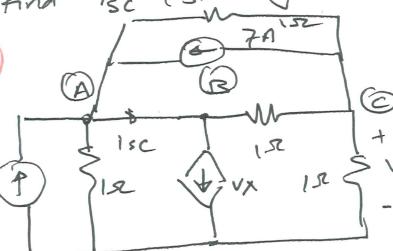


$$V_A = V_B$$

$$\begin{aligned} (A) & \rightarrow 2V_A - V_C + i_{SC} = 14 \\ (B) & \rightarrow -i_{SC} + V_X + V_B - V_C = 0 \\ (C) & \rightarrow 3V_C - V_B - V_A = -7 \end{aligned} \quad \Rightarrow \quad \boxed{i_{SC} = V_B} \quad (03)$$

$$V_X = V_C$$
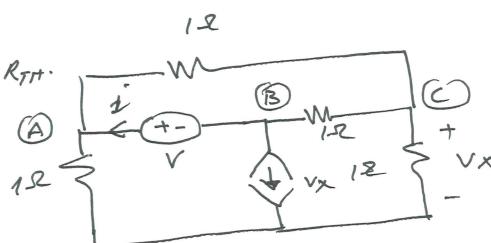
$$\Rightarrow \boxed{i_{SC} = V_B = 5A} \quad (02)$$



$$V = V_A - V_B = \frac{2}{5}i + i = \frac{7}{5}i \quad \Rightarrow \quad \boxed{R_{TH} = \frac{7}{5}\Omega} \quad (02)$$

$$\tau = \frac{L}{R} = \frac{7}{7/5} = 5 \text{ sec.} \quad (01)$$

$$\begin{aligned} (A) & : 2V_A - V_C = i \\ (B) & : V_X + V_B - V_C = -i \\ (C) & : 3V_C - V_B - V_A = -i \end{aligned} \quad \Rightarrow \quad \boxed{\begin{array}{l} V_B = -i \\ 2V_A - V_C = +i \\ 3V_C - V_A = -i \end{array}} \quad (03) \quad \Rightarrow \quad \boxed{V_A = \frac{2}{5}i} \quad (03)$$

$$\begin{aligned} V_X &= V_C \\ V &= V_A - V_B = \frac{2}{5}i + i = \frac{7}{5}i \end{aligned}$$

$$\Rightarrow \quad \boxed{\begin{array}{l} i_L(t) = 5 = [1 - 5] e^{-t/5} \\ i_L(t) = 5 - 4 e^{-t/5} \end{array}} \quad (04)$$


ii) $v_x(\infty) = V_C$ found above \Rightarrow (when inductor is short) (02)

$$\Rightarrow \quad \boxed{v_x(\infty) = 1V} \quad (05)$$

Prob. 2 : (20 pts) Consider the following circuit. Let $v_C(0) = 3$ Volts.

i : Find the value of α so that the time constant τ of the circuit is $\tau = 2$ sec. (If this is not possible, explain why).

ii : Let $\alpha = 4$. Find $v_C(t)$.

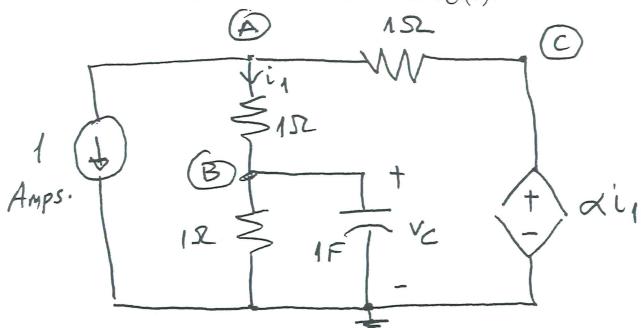

$$\text{i) Find } R_{TH}$$

$$v_B = v$$

$$v_C = \alpha i_1$$

$$= \alpha(v_A - v_B)$$

$$2v_B - v_A = i$$

$$2v_A - v_B - v_C = 0$$

(05)

$$\Rightarrow \begin{cases} 2v - v_A = i \\ (2-\alpha)v_A + (\alpha-1)v_B = 0 \end{cases}$$

$$v_A = \frac{\alpha-1}{\alpha-2} v_B \Rightarrow \left[2 - \frac{\alpha-1}{\alpha-2} \right] v = \frac{\alpha-3}{\alpha-2} v \Rightarrow R_{TH} = \frac{\alpha-2}{\alpha-3} \Omega$$

(03)

$$\Rightarrow \tau = R_{TH}C = \frac{\alpha-2}{\alpha-3} = 2 \quad \Rightarrow \alpha-2 = 2\alpha-6 \Rightarrow \alpha = 4$$

(02)

$$(c) \boxed{R_{TH} = 2 \Omega} \quad \text{For } v_{TH} \Rightarrow$$

$$i_1 = \frac{v_A}{2} \quad v_C = 4i_1 = \frac{4v_A}{2}$$

$$\textcircled{A} \rightarrow 1 + \frac{v_A}{2} + (v_A - 4 \cdot \frac{v_A}{2}) = 0$$

$$1 + \frac{v_A}{2} - v_A = 0 \Rightarrow \boxed{v_A = 2V}$$

(06)

$$\Rightarrow \boxed{v_B = v_{TH} = 1 V}$$


$$\tau = R_{TH}C = 2 \text{ sec.} \rightarrow v_C - 1 = [3-1] e^{-t/2}$$

$$\boxed{v_C(t) = 1 + 2 e^{-t/2} V} \quad (04)$$

Prob. 3 : (20 pt.s) Consider the following circuit. Let $v_C(0) = 1 \text{ V}$ and $i_L(0) = 2 \text{ A}$.

i : Find coupled ordinary differential equations for v_C and $i_L(t)$ in the form $\dot{v}_C = a_{11}v_C + a_{12}i_L$, $i_L = a_{21}v_C + a_{22}i_L$, here (\cdot) represents time derivative, a_{ij} are appropriate constants.

ii : Find $v_C(t)$.

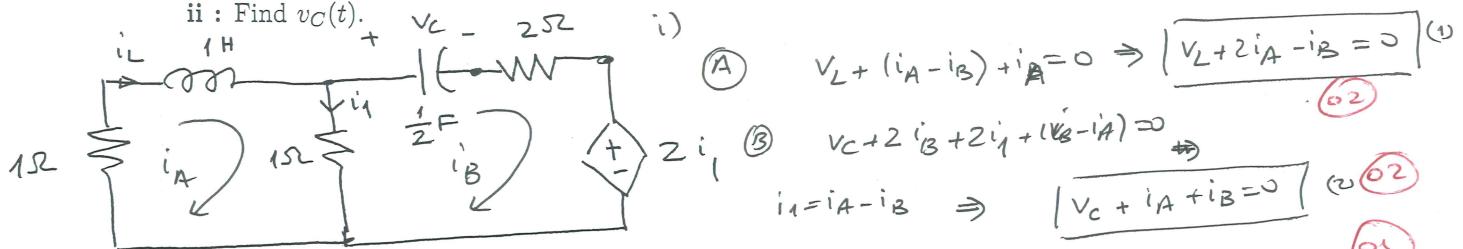

$$\begin{aligned} & \left| \begin{array}{l} i_A = i_L \\ i_B = i_C \end{array} \right. \Rightarrow \quad \left| \begin{array}{l} i_A = -i_L - v_C \end{array} \right. \Rightarrow \quad v_L = -2i_L + i_C \Rightarrow \left| \begin{array}{l} v_L = -3i_L - v_C \end{array} \right. \\ & \Rightarrow \frac{1}{2} \ddot{v}_C = -i_L - v_C \Rightarrow \left| \begin{array}{l} \ddot{v}_C = -2v_C - 2i_L \\ i_L = -v_C - 3i_L \end{array} \right. \quad \text{(04/04)} \end{aligned}$$

$$\begin{aligned} & \text{(i)} \quad \left| \begin{array}{l} \ddot{v}_C - T \cdot \dot{v}_C + \Delta v_C = 0 \\ T = -5 \\ \Delta = 6 - 2 = 4 \end{array} \right. \quad \left| \begin{array}{l} \ddot{v}_C + 5\dot{v}_C + 4v_C = 0 \end{array} \right. \quad \text{(02)} \\ & \Rightarrow s^2 + 5s + 4 = 0 \Rightarrow \left| \begin{array}{l} s_1 = -4 \\ s_2 = -1 \end{array} \right. \Rightarrow \left| \begin{array}{l} v_C(t) = C_1 e^{-t} + C_2 e^{-4t} \end{array} \right. \quad \text{(02)} \end{aligned}$$


$$\begin{aligned} & v_C(0) = 1, \quad \dot{v}_C(0) = -2v_C(0) - 2i_L(0) \\ & = -6 \quad \Rightarrow \quad \left| \begin{array}{l} 1 = C_1 + C_2 \\ -6 = -C_1 - 4C_2 \end{array} \right. \quad \left| \begin{array}{l} C_1 = -\frac{2}{3} \\ C_2 = \frac{5}{3} \end{array} \right. \quad \text{(02)} \end{aligned}$$

$$\Rightarrow \left| \begin{array}{l} v_C(t) = -\frac{2}{3} e^{-t} + \frac{5}{3} e^{-4t} \end{array} \right. \quad \text{(02)}$$

Prob. 4 : (20 pt.s) Consider the following circuit. Let $v_s(t) = 2 \cos(2t + 30^\circ)$ Volts. Assume that the circuit is in sinusoidal steady state.

i : Find the phasors V_1 and I_2 (corresponding to $v_1(t)$ and $i_2(t)$).

ii : Find $v_1(t)$.

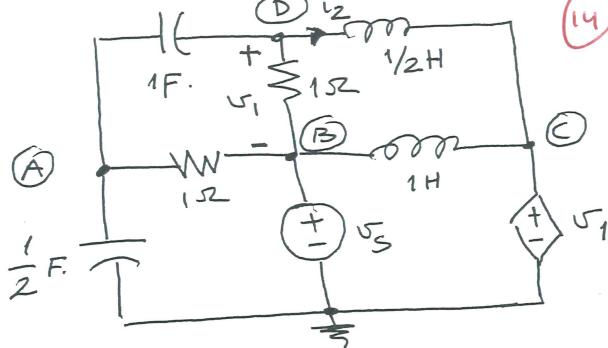

(14)

$$i) \quad V_B = V_s$$

$$V_C = V_1 = V_D - V_B$$

$$\omega = 2 \text{ rad/sec.}$$

$$(A) \quad ((1+3j)V_A - V_B - j2V_D = 0) \quad (02)$$

$$(B) \quad -j2V_A + (1+j2 + \frac{1}{j})V_D - \frac{1}{j}V_C - V_B = 0$$

$$\Rightarrow (-j2V_A + (1+j))V_D + jV_C = V_s \quad (02)$$

$$(1+3j)V_A - j2V_D = V_s$$

$$-j2V_A + (1+j)V_D + j(V_D - V_B) = V_s$$

$$((1+3j)V_A - j2V_D = V_s) \quad (02)$$

$$-j2V_A + (1+j)V_D = (1+j)V_s \quad (02)$$

$$\Rightarrow V_D = \frac{-2+6j}{-1+5j} V_s$$

$$\bar{V}_1 = V_D - V_B = \left(\frac{-2+6j}{-1+5j} - 1 \right) V_s = \frac{-1+j}{-1+5j} V_s \quad (03)$$

$$KVL \Rightarrow V_1 + V_s = jI_2 + V_1 \quad (03)$$

$$\Rightarrow jI_2 = V_s \Rightarrow I_2 = jV_s$$

$$ii) \quad V_1 = \frac{-1+j}{-1+5j} V_s = \frac{(-1+j)(-1-5j)}{(1+25)} V_s = \frac{3+2j}{13} V_s \quad (03)$$

$$V_s = 2 e^{j30^\circ}$$

(03)


$$V_1 = \frac{\sqrt{13}}{13} e^{j\tan^{-1}\frac{2}{3}} \cdot 2 e^{j30^\circ} = \frac{2\sqrt{13}}{13} e^{j(30^\circ + \tan^{-1}\frac{2}{3})} = \frac{2\sqrt{13}}{13} e^{j(63.69^\circ)}$$

$$= 0.554 e^{j(63.69^\circ)}$$

$$v_1(t) = 0.554 \cos(2t + 63.69^\circ) \quad (03)$$

Prob. 5 : (20 pt.s) Consider the following circuit. Let $i_s(t) = I_m \cos(\omega t + \phi)$ Amps. Assume that the circuit is in sinusoidal steady state.

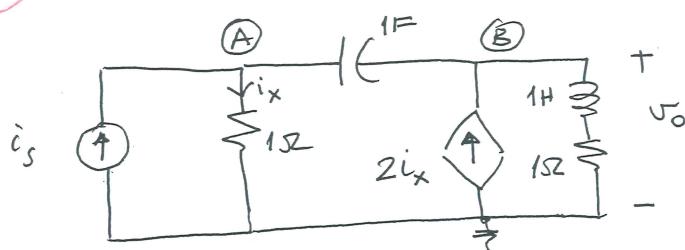- i : Find the transfer function $H = \frac{V_0}{I_s}$ in terms of ω . Here V_0 and I_s are phasors of $v_0(t)$ and $i_s(t)$.
- ii : Let $i_s(t) = 2 \cos(2t - 45^\circ)$ Amps. Find $v_0(t)$.



$$i) 1\Omega + 1H \Rightarrow Z_L = R + j\omega L = \frac{1+j\omega}{1-j\omega} \quad (02)$$

$$\textcircled{A} I_s = V_A + j\omega(V_A - V_B) = (1+j\omega)V_A - j\omega V_B \quad (02)$$

$$\textcircled{B} 2i_x = j\omega(V_B - V_A) + \frac{V_B}{1+j\omega} \quad (02)$$

$$\Rightarrow \begin{cases} (1+j\omega)V_A - j\omega V_B = I_s \\ -j\omega V_A + \left(j\omega + \frac{1}{1+j\omega}\right)V_B = 2i_x \end{cases} \Rightarrow i_x = V_A \quad (02)$$

$$(1+j\omega)V_A - j\omega V_B = I_s$$

$$-(2+j\omega)V_A + \frac{(j\omega)^2 + j\omega + 1}{1+j\omega}V_B = 0 \quad (02)$$

$$\Rightarrow \boxed{V_A = \frac{1-\omega^2 + j\omega}{(2+j\omega)(1+j\omega)} V_B} \Rightarrow \boxed{\left[\frac{1-\omega^2 + j\omega}{2+j\omega} \quad -j\omega \right] V_B = I_s} \Rightarrow V_B = \frac{2+j\omega}{1-\omega^2 - j\omega - 2j\omega + \omega^2} I_s \quad (02)$$

$$\Rightarrow \boxed{H(j\omega) = \frac{V_B}{I_s} = \frac{2+j\omega}{1-j\omega}} \quad (04)$$

$$ii) i_s(t) = 2 \cos(2t - 45^\circ) \Rightarrow \omega = 2 \text{ rad/sec.} \quad I_s = 2 e^{-j45^\circ}$$

$$V_B = \frac{2+j2}{1-j2} \cdot I_s = \frac{2(1+j)}{1-j^2} 2e^{-j45^\circ} = \frac{2\sqrt{2}e^{j45^\circ}}{\sqrt{5}e^{-j\tan^{-1}2}} 2e^{-j45^\circ} = \frac{4\sqrt{2}}{\sqrt{5}} e^{j\tan^{-1}2} \quad (04)$$

$$V_B(t) = V_0(t) = \frac{4\sqrt{2}}{\sqrt{5}} \cos(2t + \tan^{-1}2) = 2.53 \cos(2t + 63.44^\circ) \quad (04)$$