

Ömer Morgül

NAME

FAMILYNAME



SECTION

EEE 202 CIRCUIT THEORY
Final, Spring 2012-13

No credits will be given for unjustified answers.


Prob. 1 : (25 pt.s)

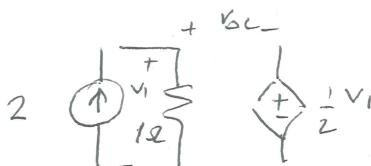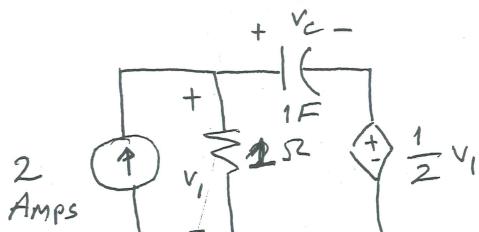i : (6 pt.s) In the following circuit, $v_C(0) = 0$ Volts. Find $v_C(t)$.



$$v_1 = 2V \quad \frac{1}{2} v_1 = 1V$$


$$v_{OC} = 2 - 1 = 1V$$
02

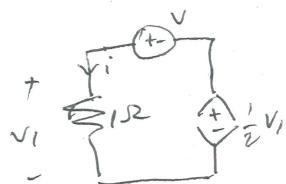

$$\begin{aligned} v &= v_1 - \frac{1}{2} v_1 = \frac{1}{2} v_1 \\ v_1 &= i \end{aligned} \quad \left. \begin{array}{l} v = \frac{1}{2} i \\ \Rightarrow R_{eq} = \frac{1}{2} \Omega \end{array} \right\} \quad \begin{aligned} \Rightarrow R_{eq} &= \frac{1}{2} \Omega \\ \Rightarrow \tau &= \frac{1}{2} \text{ sec.} \end{aligned}$$

$$v_C(t) - 1 = [0 - 1] e^{-t/\tau} \Rightarrow \boxed{v_C(t) = 1 - e^{-2t}}$$
02

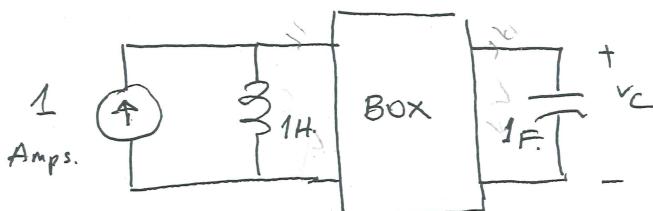ii : (4 pt.s) In the following circuit, the box contains only resistors and dependent sources. A student claims that $v_C(t) = 1 + 2e^{-t} \cos t + e^{-2t} \sin 3t$ Volts. Do you believe this result, and why.



$$v_C(t) = V_F + V_H$$


V_F : forced response \Rightarrow due to unit step 01
 \Rightarrow constant part

$V_H \Rightarrow$ homogeneous part \Rightarrow due to the roots of characteristic polynomial
 \Rightarrow poles of the system 01

$$\begin{aligned} e^{-t} \cos t &\rightarrow -1 + j \\ e^{-2t} \sin 3t &\rightarrow -2 + j3 \end{aligned} \quad \left. \begin{array}{l} 4 \text{ roots (4 poles)} \\ \text{are required.} \end{array} \right\}$$

But this is a SECOND ORDER SYSTEM 02
 \Rightarrow IMPOSSIBLE

iii : (5 pt.s) The following circuit is an equivalent of a piezoelectric crystal. Assume that the circuit is in sinusoidal steady state. Find a frequency ω_s such that $Z(j\omega_s) = 0$. (This is called the series resonance frequency). Find a frequency ω_p such that $Y(j\omega_p) = 0$. (This is called the parallel resonance frequency). Here Z and Y represent the impedance and admittance, as usual.

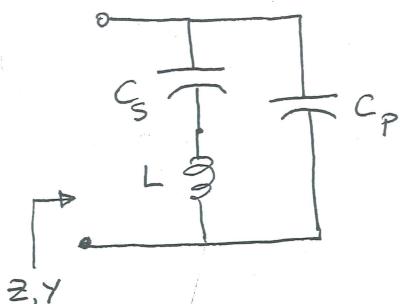


$$Y = j\omega C_p + \frac{1}{j\omega L + \frac{1}{j\omega C_s}} = j\omega C_p + \frac{j\omega C_s}{1 - \omega^2 L C_s} = \frac{j\omega [C_p(1 - \omega^2 L C_s) + C_s]}{1 - \omega^2 L C_s} \quad (01)$$

$$Z(j\omega_s) = 0 \Rightarrow 1 - \omega_s^2 L C_s = 0 \Rightarrow \omega_s = \sqrt{\frac{1}{L C_s}} \quad (02)$$

$$Y(j\omega_p) = 0 \Rightarrow C_p(1 - \omega^2 L C_s) + C_s = 0$$

$$C_p + C_s = \omega_p^2 L C_s C_p \Rightarrow \omega_p = \sqrt{\frac{1}{L \frac{C_s C_p}{C_s + C_p}}} \quad (02)$$

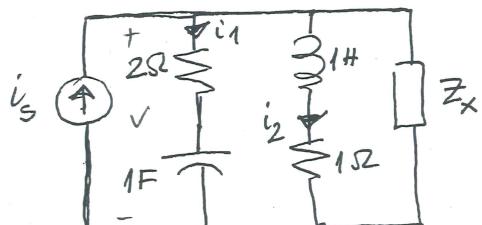iv : (5 pt.s) Consider the following circuit, which is in sinusoidal steady state. Here Z_x is an unknown impedance, which contains only linear elements. If $i_1(t) = \cos t$, find $i_2(t)$.



$$I_1 = 1 \text{ A}$$

$$\omega = 1 \text{ rad/sec.}$$

$$V = (2 + \frac{1}{j}) I_1 = (2 - j) \quad (01)$$

$$I_2 = \frac{V}{1+j} = \frac{2-j}{1+j} = \frac{\sqrt{5} e^{-j \tan^{-1} 1/2}}{\sqrt{2} e^{j 45^\circ}} \quad (02)$$

$$i_2(t) = \frac{\sqrt{5}}{\sqrt{2}} \cos(t - \tan^{-1} 1/2 + 45^\circ) \quad (02)$$

v : (5 pt.s) Consider the circuit shown above (problem iv). Let $i_s(t) = 3 \cos t$, $i_1(t) = \cos t$. Find the average power dissipated in Z_x .

$$I_S = I_1 + I_2 + I_x \Rightarrow I_x = 3 - 1 - \frac{2-j}{1+j} = 2 - \frac{2-j}{1+j} = \frac{3j}{1+j} \quad (01)$$

$$P_x = \frac{1}{2} V I_x^* = \frac{1}{2} (2-j) \frac{-3j}{1-j} = \frac{1}{2} \frac{-3-6j}{1-j} = \frac{1}{4} (-3-6j)(1+j) \quad (02)$$


$$= \frac{1}{4} (6-3-9j) = \frac{1}{4} (3-9j)$$

$$P_{ave} = \Re \{ P_x \} = \frac{3}{4} \text{ watts.} \quad (02)$$

Prob. 2 : (25 pt.s) Consider the following circuit. Assume that the initial conditions are given as $v_C(0) = \gamma$ Volts, and $i_L(0) = \beta$ Amps.

i : Find $I_A(s)$ in terms of $V_i(s)$, γ and β , i.e. like $I_A(s) = H_1(s)V_i(s) + H_2(s)\gamma + H_3(s)\beta$.
ii : Let $v_i(t) = 5u(t)$ (here $u(t)$ is the unit-step function). By choosing initial conditions γ and β appropriately, is it possible to have $i_A(t) = I_0 u(t)$, where I_0 is a constant and $u(t)$ is the unit step function? (i.e. i_A does not contain any transients). If possible, find such initial conditions γ and β . (If possible, this is called "to set up a mode")

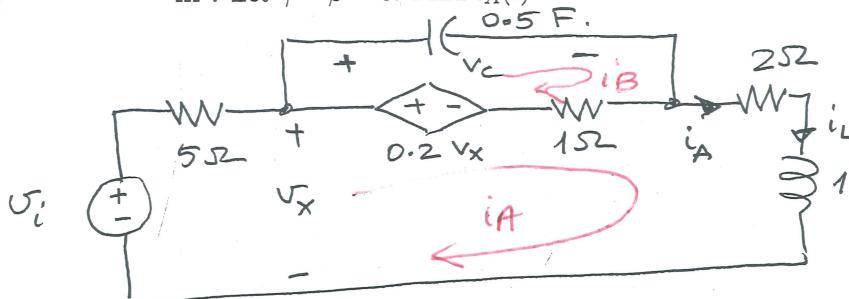iii : Let $\gamma = \beta = 0$. Find $i_A(t)$.



$$\begin{aligned} & \text{(10) i) Write mesh eqn s} \\ & 7I_A + (I_A - I_B) + sI_A - B = -0.2Vx + V_i \\ & \text{(2)} [(s+8)I_A - I_B = -0.2Vx + V_i + \beta] \\ & \frac{2}{s}I_B + \frac{1}{s}\gamma + (I_B - I_A) = 0.2Vx \\ & \text{(2)} [-I_A + (\frac{2}{s} + 1)I_B = 0.2Vx - \frac{1}{s}\gamma] \end{aligned}$$

$$V_x = V_i - 5I_A \Rightarrow (s+7)I_A - I_B = 0.8V_i + \beta \quad (1) \quad \left(\frac{2}{s} + 1 \right)I_B = 0.2V_i - \frac{1}{s}\gamma$$

$$\Rightarrow \left[I_B = \frac{0.2s}{s+2}V_i - \frac{1}{s+2}\gamma \right] \quad (2) \Rightarrow \left[I_A = \frac{s+1.6}{(s+2)(s+7)}V_i - \frac{1}{(s+2)(s+7)}\gamma + \frac{1}{s+7}\beta \right] \quad (2)$$

$$\text{ii) } v_i = 5u(t) \Rightarrow \left[I_A = \frac{5s+8}{s(s+2)(s+7)} - \frac{1}{(s+2)(s+7)}\gamma + \frac{1}{s+7}\beta \right]$$

$$\left[\begin{array}{l} I_A = \frac{K_1}{s} + \frac{K_2}{s+2} + \frac{K_3}{s+7} \\ \text{we need } \begin{cases} K_2 = 0 \\ K_3 = 0 \end{cases} \\ K_2 = (s+2)I_A \Big|_{s=-2} = \frac{1}{5} - \frac{\gamma}{5} \\ K_3 = (s+7)I_A \Big|_{s=-7} = \frac{27}{35} + \frac{\gamma}{5} + \beta \end{array} \right] \quad (2)$$

$$\Rightarrow \left[\begin{array}{l} \gamma = 1 \\ \beta = +\frac{27}{35} \end{array} \right] \Rightarrow \left[I_A = \frac{K_1}{s} \right] \rightarrow \left[i_A(t) = K_1 u(t) \right]$$

$$\text{iii) } \gamma = \beta = 0 \Rightarrow I_A = \frac{5s+8}{s(s+2)(s+7)} = \frac{k_1}{s} + \frac{k_2}{s+2} + \frac{k_3}{s+7} \quad (1)$$

$$\left[\begin{array}{l} k_1 = I_A \Big|_{s=0} = \frac{8}{14} \\ k_2 = (s+2)I_A \Big|_{s=-2} = \frac{1}{5} \\ k_3 = (s+7)I_A \Big|_{s=-7} = -\frac{27}{35} \end{array} \right] \quad (1)$$


$$i_A(t) = \frac{4}{7} + \frac{1}{5}e^{-2t} - \frac{27}{35}e^{7t} \quad (3)$$

Prob. 3 : (25 pt.s) Consider the following circuit. Assume that the initial conditions are zero.

i : Find the transfer function $H(s) = \frac{V_A}{I_s}$.

ii : Assume that the circuit is in sinusoidal steady state and that $i_s(t) = 2 \cos t$. Find $v_1(t)$.

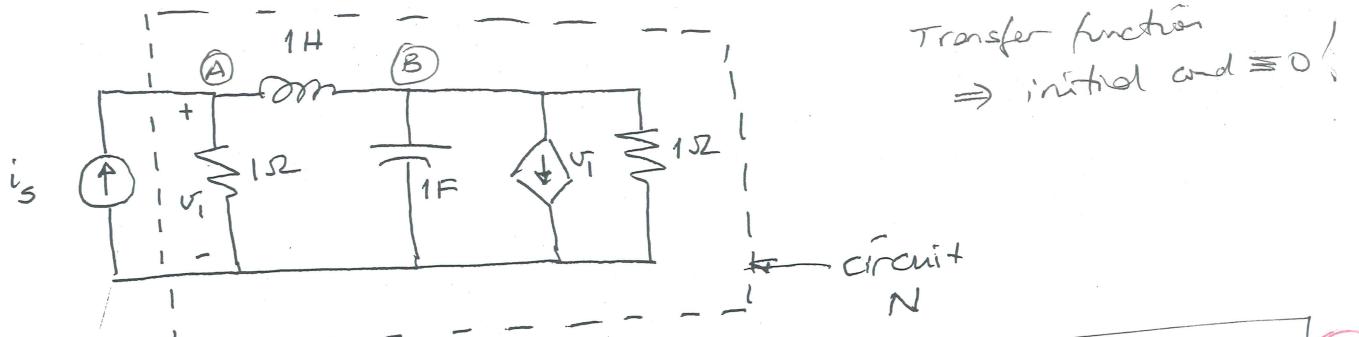iii : Assume that the circuit is in sinusoidal steady state and that $i_s(t) = 2 \cos t$. Find the average power dissipated in the circuit N .



13/13

i)

$$\left. \begin{array}{l} (03) \quad (A) \rightarrow (1 + \frac{1}{s}) V_A - \frac{1}{s} V_B = I_s \\ (03) \quad (B) \rightarrow -\frac{1}{s} V_A + (1 + \frac{1}{s} + s) V_B = -v_1 \\ \quad \quad \quad v_1 = V_A \end{array} \right\} \quad \left. \begin{array}{l} \frac{s+1}{s} V_A - \frac{1}{s} V_B = I_s \\ \frac{s^2+s+1}{s} V_B + \frac{s-1}{s} V_A = 0 \end{array} \right\} \quad \left. \begin{array}{l} V_B = \frac{1-s}{s^2+s+1} V_A \\ H(s) = \frac{V_A}{I_s} = \frac{s^2+s+1}{s^2+2s+3} \end{array} \right\} \quad (03) \quad (04)$$

$$(05) \quad ii) \omega = 1 \text{ rad/sec} \Rightarrow H(j\omega) = \frac{j}{2+2j} = \frac{1}{2\sqrt{2}} e^{j45^\circ} \quad I_s = 2$$

$$v_1(t) = \frac{1}{2\sqrt{2}} \cos(t+45^\circ) = \frac{1}{\sqrt{2}} \cos(t+45^\circ) \quad (04) \quad (02)$$

06/06

$$iii) \quad I_s = 2 \quad V_1 = \frac{1}{\sqrt{2}} e^{j45^\circ} \quad (02)$$

06/06

$$P_{ave} = \operatorname{Re} \left\{ \frac{1}{2} V_1 \cdot I_s^* \right\} = \frac{1}{2} \cdot \frac{1}{\sqrt{2}} \cdot \cos 45^\circ \cdot 2$$



$$\boxed{P_{ave} = \frac{1}{2} \text{ watts.}} \quad (02)$$

Prob. 4 : (25 pt.s) Consider the following circuit. Assume that the op-amp is ideal and operates in the linear region.

i : Find the transfer function $H(s) = \frac{V_0}{V_i}$. Show that it has the form $H(s) = \frac{K\beta s}{s^2 + \beta s + \omega_0^2}$. Find K , β , ω_0 in terms of the resistor and capacitor values.

ii : Evaluate and sketch $|H(j\omega)|$. Show that it has the band-pass characteristics given below. Find H_{max} , ω_m where $|H(j\omega_m)| = H_{max}$ and the bandwidth $BW = \omega_{c2} - \omega_{c1}$ in terms of K , β , ω_0 . (This is actually a practical realization of a high quality band-pass filter).

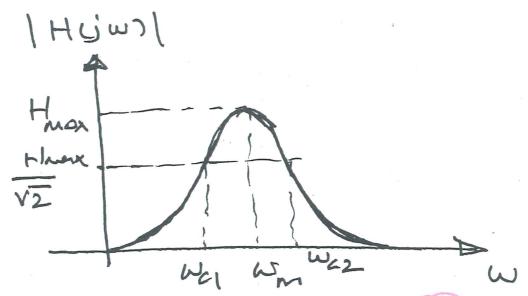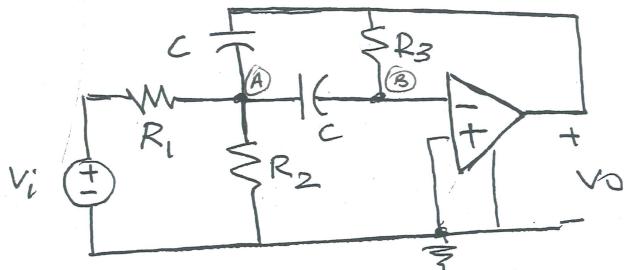iii : Let $R_1 = R_2 = R_3 = 1 \Omega$, $C = 1 F$. Assume that $v_i(t) = 3 \cos(2t - 30^\circ)$ and that the circuit is in sinusoidal steady state. Find $v_0(t)$.



$$i) \text{ (3)} \rightarrow V_A \cdot SC + \frac{V_O}{R_3} = 0 \Rightarrow V_A = -\frac{V_O}{SC R_3} \quad \text{(2)}$$

$$\Rightarrow -\frac{1}{R_1} V_i - \left[\left(\frac{R_1 + R_2}{R_1 R_2} + 2SC \right) \cdot \frac{1}{SR_3 C} + SC \right] V_o = 0 \quad \Rightarrow \quad H(s) = \frac{V_o}{V_i} = \frac{-\frac{1}{R_1 C} s}{s^2 + \frac{2}{R_3 C} + \frac{1}{R_3 R_2 C^2}}$$

$$\boxed{\beta = \frac{2}{R_3 C}} \quad \boxed{\omega_0^2 = \frac{1}{\frac{R_1 R_2}{R_1 + R_2} R_3 C^2}} \quad \boxed{K_B = -\frac{1}{R_1 C}} \Rightarrow \boxed{K = -\frac{R_3}{2R_1}}$$

$$\text{ii) } H(j\omega) = \frac{-K\beta j\omega}{\omega_0^2 - \omega^2 + j\beta\omega} \quad |H(j\omega)| = \frac{K}{\sqrt{1 + \left(\frac{\omega_0^2 - \omega^2}{\beta\omega}\right)^2}} \quad \begin{matrix} 02 \\ \text{Bend-Poss.} \end{matrix}$$

$$\text{For } \lambda x \rightarrow \text{derivative min} \Rightarrow \boxed{\text{ot}} \quad \boxed{w_m = w_0} \quad \Rightarrow \quad \boxed{|H(w_m)|}$$

$$\text{For } \omega_{c1}, \omega_{c2} \Rightarrow \frac{\omega_0^2 - \omega^2}{\beta N} = \mp 1 \quad \Rightarrow \quad \boxed{\omega^2 \mp \beta N - \omega_0^2 = 0} \quad \Rightarrow \quad \Delta = \beta^2 + 4\omega_0^2$$

$$w_{C1} = \frac{-\beta + \sqrt{\Delta}}{2} \quad w_{C2} = \frac{\beta + \sqrt{\Delta}}{2} \quad \Rightarrow \quad \boxed{BW = w_{C2} - w_{C1} = \beta} \quad (62)$$

$$iii) \quad \frac{V_o}{V_i} = \frac{-s}{s^2 + 2s + 2} \rightarrow w=2 \quad H(j2) = \frac{-2+j4}{-2+j4} \quad 20$$

$$V_i = 3 e^{-j30^\circ}$$