

Ömer Morgül, F. Ömer İlday

NAME

FAMILYNAME

SECTION

EEE 202 CIRCUIT THEORY
Second Midterm, Spring 2014-15

No credits will be given for unjustified answers. **Good luck.**


| Problem 1 | Problem 2 | Problem 3 | Problem 4 | TOTAL |
|-----------|-----------|-----------|-----------|-------|
| | | | | |

Prob. 1 : (28 pt.s)


i : (15 pt.s) Consider the following circuit. Assume that the circuit is stable.

i-1 Find the value of α so that $\lim_{t \rightarrow \infty} v_o(t) = 3 \text{ V}$.

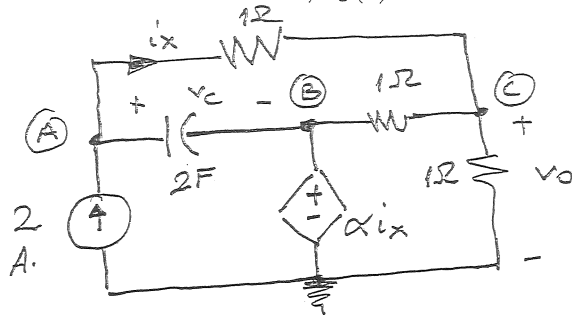i-2 Now let $\alpha = 2$, $v_C(0) = 3 \text{ V}$. Find $v_C(t)$ and $i_x(t)$.



ii : Consider the following circuit. Let $i_L(0) = 1$ A. Find $i_L(t)$ and $i_x(t)$.

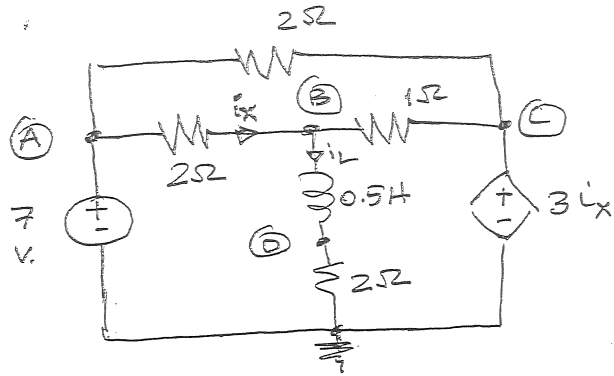


Prob. 2 : (22 pt.s) Consider the following circuit.

i : Find a second order ODE for v_C . (i.e. of the form $\ddot{v}_C + a\dot{v}_C + bv_C = u$. Note that some coefficients may depend on β).

ii : Find the range of β so that the solution $v_C(t)$ contains a damped sinusoid term (i.e. a term $e^{-\alpha t} \cos(\omega t + \phi)$).

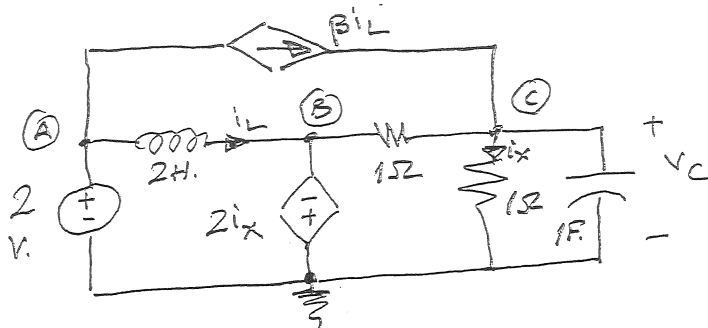iii : Let $\beta = 3$, $v_C(0) = 2$ V, $i_L(0) = 1$ A. Find $v_C(t)$ and $i_L(t)$.





Prob. 3 : (25 pt.s) Consider the following circuit. Assume that $v_i(t) = V_i \cos \omega t$ and that the circuit is in sinusoidal steady state. The load represents an arbitrary (nonzero and finite) impedance.

i : Assume that we measured $i_L(t) = 0$ A. Find R_x and L_x in terms of ω , R and C .

ii : Now assume that the load is as given below (in fig. 2). Let $v_i(t) = 4 \cos 1000t$ V, $C = 1 \mu\text{F}$, $L_x = 0.5$ H, $R_x = 2$ k Ω , $R = 1$ k Ω . Find $v_o(t)$.

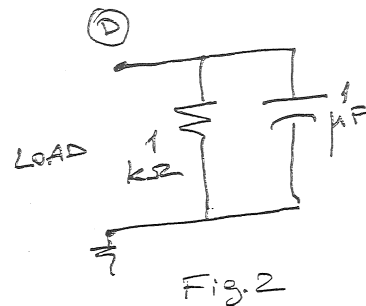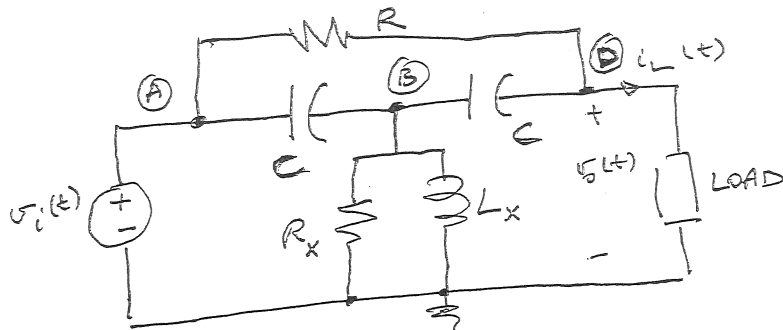iii : Find the average power dissipated in the load.



Prob. 4 : (25 pt.s) Consider the following circuit. Assume that $v_{in}(t) = V_i \cos \omega t$, the op-amps are linear, operate in linear region, and that the circuit is in sinusoidal steady state. Here Z_1, Z_2, Z_3, Z_4, Z_5 represent arbitrary impedances.

i : Find $Z_{eq} = \frac{V_{in}}{I_{in}}$ in terms of impedances Z_1, Z_2, Z_3, Z_4, Z_5 .

ii : Choose four of these impedances as resistors of equal value R , and the last impedance as a capacitance C such that this circuit is equivalent to the circuit shown below (fig.2). Find L_{eff} in terms of R and C . Which impedances can be chosen as the capacitor to obtain this result?

