

Q.1

a.)


Donor: Donates an e^- for current conduction.

If we are talking about Silicon which is from IV-A in periodic table, Donors come from VA. When they replace one of the Si atoms, they will have one extra free e^- that can be used for current conduction.


examples: Phosphorus (P), Arsenic (As)

Acceptor: Donates a hole, or equivalently accepts an e^- for current conduction, creates a space for neighbor e^- to jump into. Acceptors come from II-A. When replaced with a Si atom, there will be one missing e^- which can be used by e^- to jump into and contribute to current conduction.

examples: Boron (B)

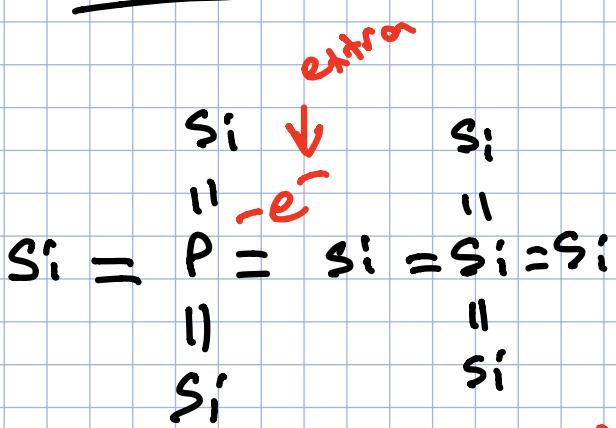


Donor atom (P)

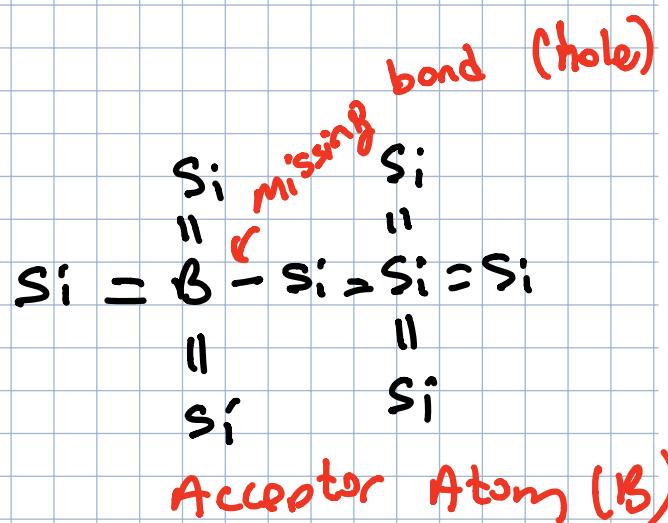

Acceptor Atom (B)

b)

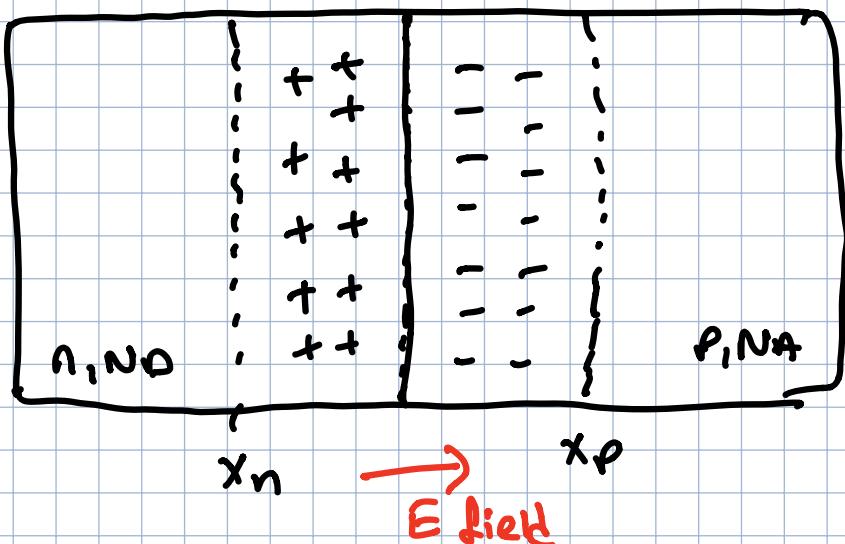

n-side has a lot of e^- from donor atoms, and p-side has a lot of holes from acceptor atoms. Once n and p-sides touch each other the diffusion process starts. e^- diffuse into the p-side and holes diffuse into the n-side. One e^- s leave donors on n-side a (+) charged region is created. Similarly a (-) charged region is created on the p-side. There are no mobile regions in this "depletion region".

The (+) and (-) charged regions created by diffusion creates an E field that opposes the diffusion of e^- from the n-side to p-side and "holes" from the p-side to n-side. The E field creates the drift current that balances the diffusion current. The charge flow stops when these drift and diffusion processes are equal to each other.

Energy band diagram

Fermi level

E_F

E_i

n_{side}



$$\text{Energy} = -q \cdot V$$

p_{side}

$p \text{ side.}$

* Note that

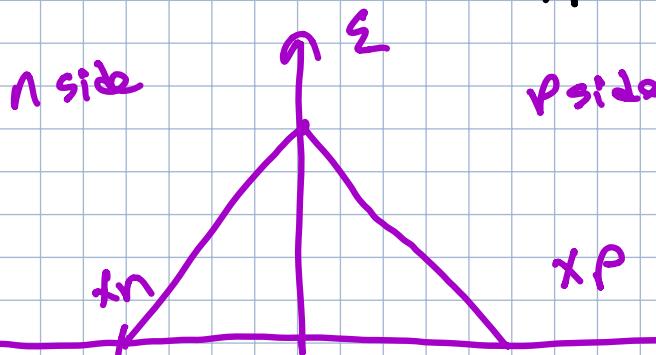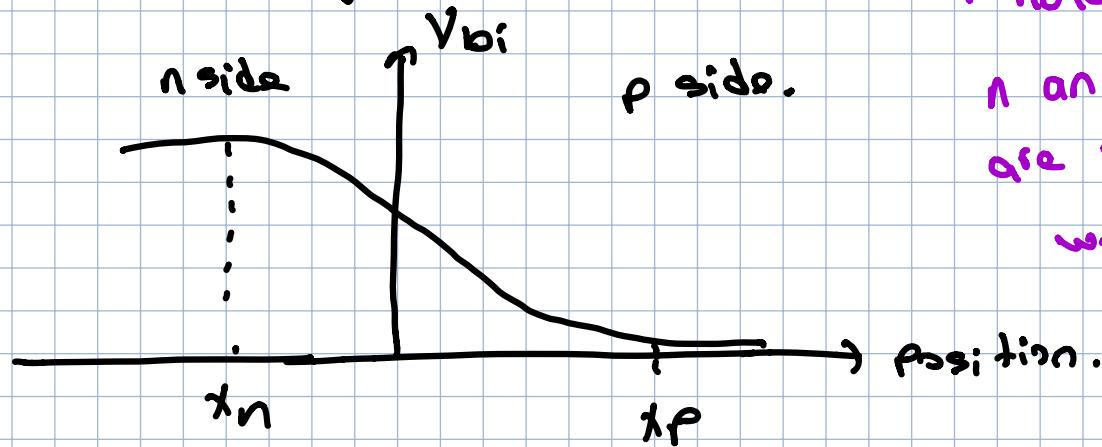n and p sides
are swapped here
w.r.t. class.




Σ : Electric field

$$\Sigma = -\frac{dV}{dx}$$


P : Charge density.

$$P: \frac{d\Sigma}{dx}$$

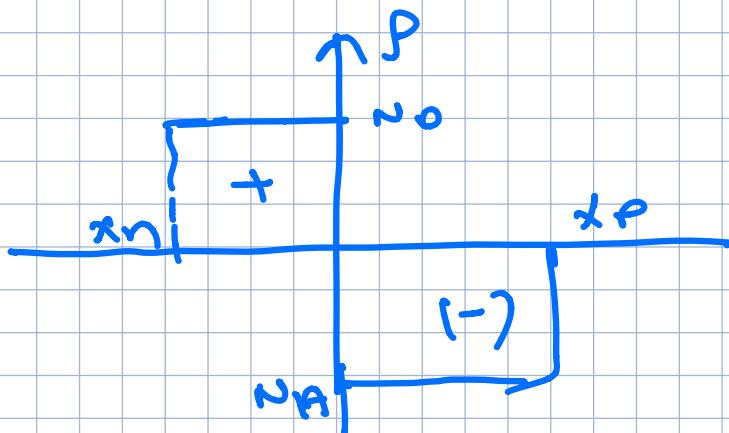


c)

forward bias ($V_D > V_{DN}$)

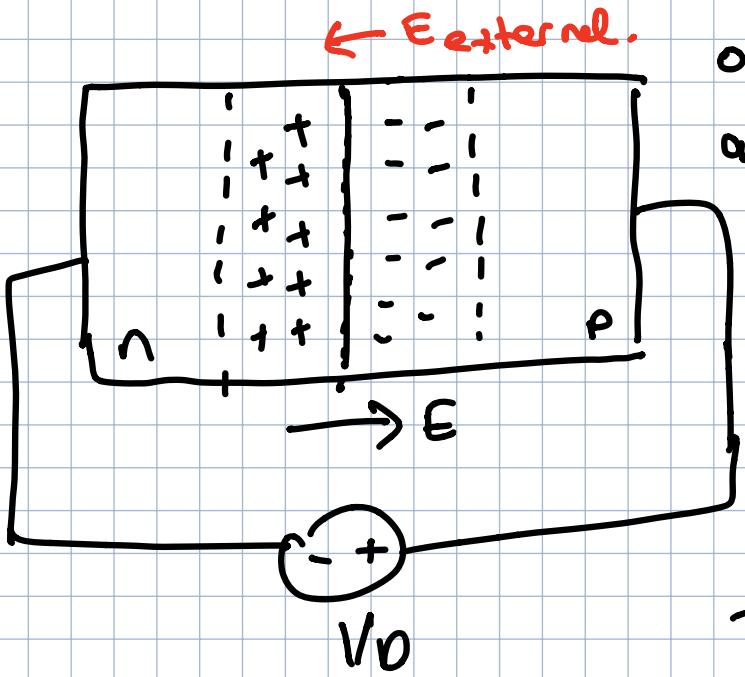

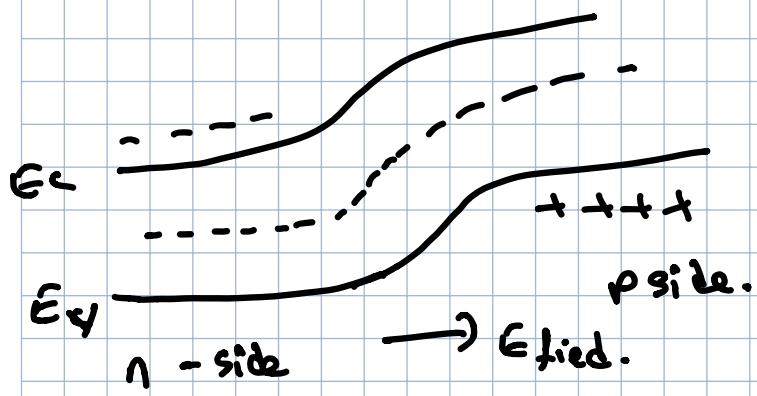* External formed by V_D opposes the internal E field and hence reduces the energy barrier between the sides.




The possibility of finding an e^- on n-side and a hole on p-side (majority carriers) that has the energy to pass the energy barrier is exponential. Reducing this energy height with forward bias with V_D leads to an exponential I-V relationship.


bias with V_D leads to an exponential I-V relationship.

reverse bias ($V_D < V_{DN}$)

\rightarrow External.

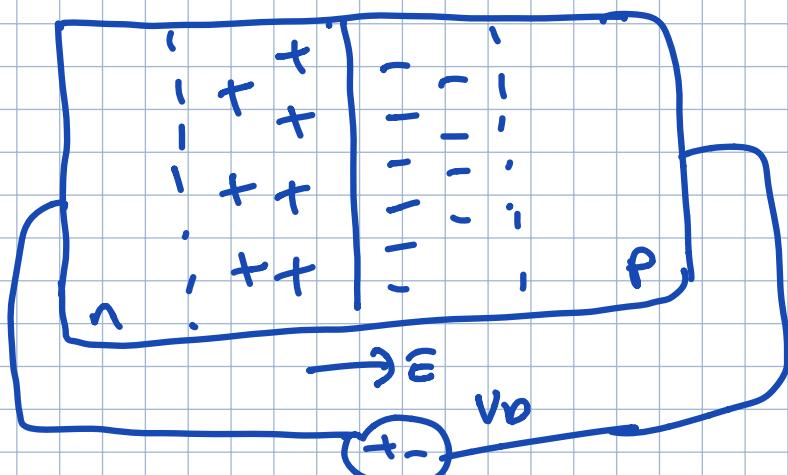

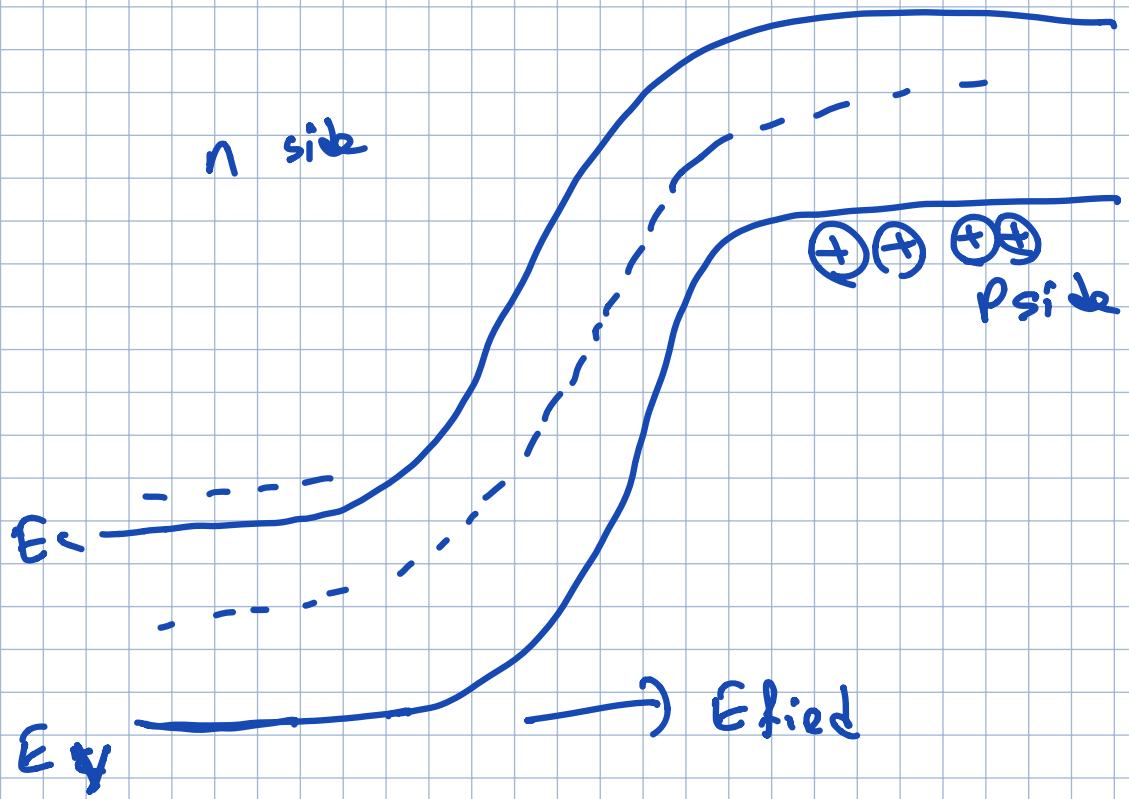
Applying a (+) voltage to the n side increases the potential barrier between the n and p sides.



The possibility of finding an e^- on n side and a hole on p-side that can pass the energy barrier is extremely low. (exponential relationship)


Instead minority carriers on n side, holes and " " " p side, e^- will form the reverse bias current. These carriers flow with the applied E field. Since the minority carriers form the reverse bias current, it is small and independent of reverse bias. (ignoring break down)

diode I-V:

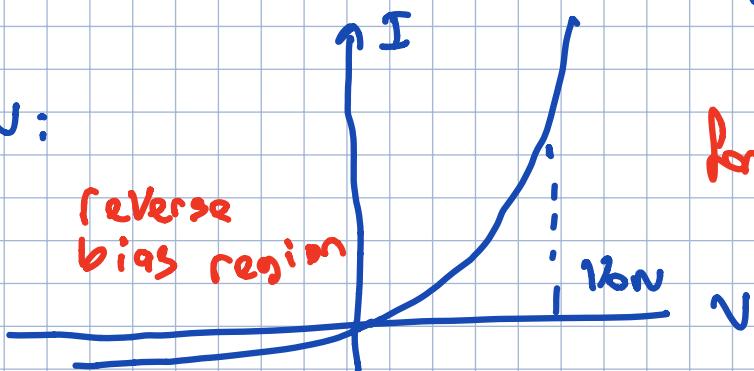


forward bias region.


Q2 solution

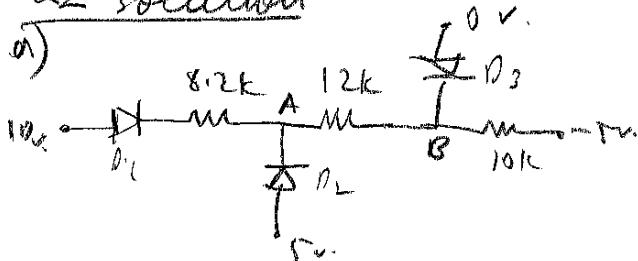

Assume all diodes are OFF

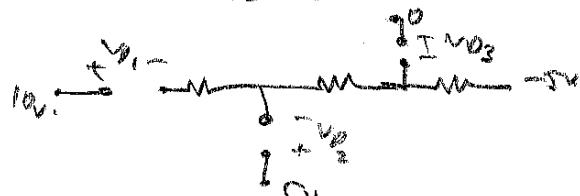

Assume D₁ ON, D₂ and D₃ OFF

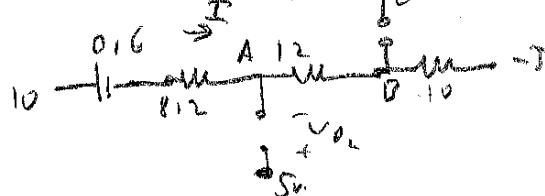

$$I = \frac{10 - 0.6 - (-r)}{8.2 + 12 + 10} = \frac{14.4}{30.2} = 0.477 \text{ mA}$$

$$V_A = 10 - 0.6 - 8.2 \times 0.477 = 5.49 \text{ V}$$

$$V_{D_1} = 5 - 5.49 = -0.69 \leq 0.6 \quad \checkmark$$

$$V_B = -5 + 10 \times 0.477 = -0.23 \text{ V}$$


$$V_{D_3} = 0 - (-0.23) = 0.23 \leq 0.6 \quad \checkmark$$

$$\begin{aligned} V_{D_1} &= 10 - (-r) = 10 < 0.6 \quad ? \\ V_{D_2} &= 5 < 0.6 \quad X \\ V_{D_3} &= 0 - (-r) = 5 \text{ V.} < 0.6 \quad X \end{aligned}$$


$$\begin{aligned} V_A &= 5.49 \text{ V} \\ V_B &= -0.23 \text{ V} \\ I_{D_1} &= 0.477 \text{ mA} \\ I_{D_2} &= I_{D_3} = 0 \end{aligned}$$

D₁ ON, D₂ OFF, D₃ OFF

b)

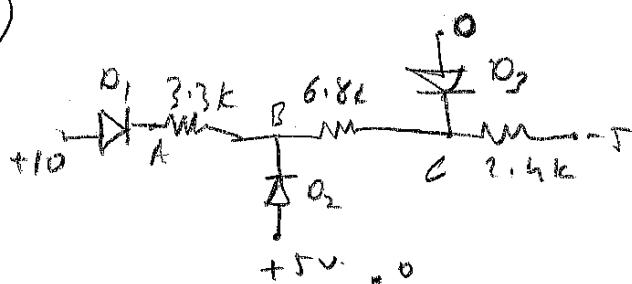

Assume D₂ ON, D₁ OFF, D₃ ON

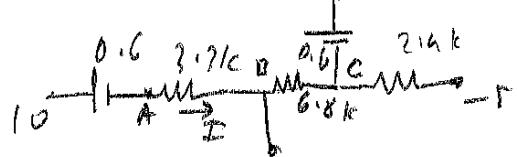

$$I = \frac{10 - 0.6 - (-0.6)}{3.3 + 6.8} = 0.99 \text{ mA} > 0 \quad \checkmark$$

$$V_A = 10 - 0.6 = 9.4 \text{ V}$$

$$V_B = 9.4 - 3.3 \times 0.99 = 6.1 \text{ V.}$$

$$V_C = -0.6 \text{ V.}$$

$$I_{D_1} = 0.99 \text{ mA} \quad I_{D_2} = 0$$


$$-I_{D_3} = 0.99 - \frac{-0.6 - (-r)}{2.4}$$

$$= 0.99 - \frac{5.4}{2.4} = -0.843 \text{ mA}$$


$$I_{D_3} = 0.843 \text{ mA} > \checkmark$$

$$\begin{aligned} V_{D_2} &= 5 - V_B = 5 - 6.1 \\ &= -1.1 \leq 0.6 \quad \checkmark \end{aligned}$$

$$+2 \text{ V}$$

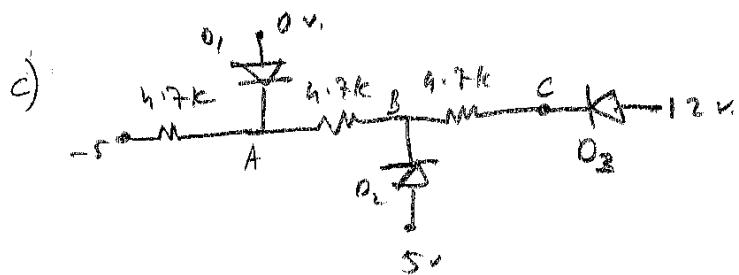

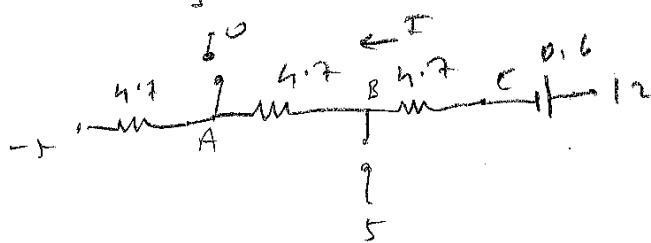Assume D_2 is ON and the other one is OFF.



$$I = \frac{12 - 0.6 - (-5)}{3 \times 4.7} = 1.163 \text{ mA}$$


$$V_C = 12 - 0.6 = 11.4 \text{ V}$$

$$V_B = 11.4 - 4.7 \times 1.163 = 5.937 \text{ V}$$


$$V_A = 5.937 - 4.7 \times 1.163 = 0.467 \text{ V}$$

$$V_{D2} = 5 - 11.4 < 0.6 \quad \checkmark$$
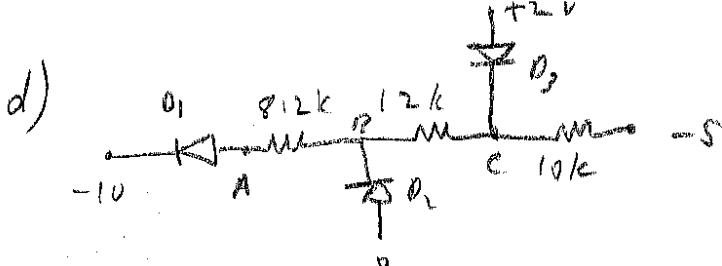
$$V_{D1} = 0 - V_A = -0.467 < 0.6 \quad \checkmark$$



Assume all diodes are ON

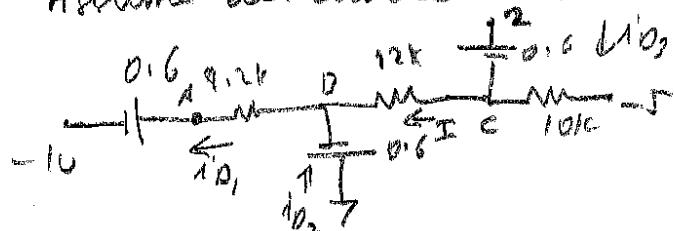

$$V_A = -10 + 0.6 = -9.4 \text{ V}$$

$$V_B = -0.6 \text{ V}$$

$$V_C = -0.6 + 2 = 1.4 \text{ V}$$

$$i_{D1} = \frac{V_D - V_A}{8.12} = \frac{-0.6 - (-9.4)}{8.12} = \frac{8.8}{8.12} = 1.073 \text{ mA} > 0 \quad \checkmark$$


$$I = \frac{V_C - V_B}{12} = \frac{1.4 - (-0.6)}{12} = \frac{2}{12} = 0.1667 \text{ mA}$$

$$i_{D2} = i_D - I = 1.073 - 0.1667 = 0.9063 \text{ mA} > 0 \quad \checkmark$$

$$i_{D3} = I + \frac{V_C - (-5)}{10} = 0.1667 + \frac{6.4}{10} = 0.8067 \text{ mA} > 0 \quad \checkmark$$

The same circuits are then solved using LTspice and very close results are obtained:


a)

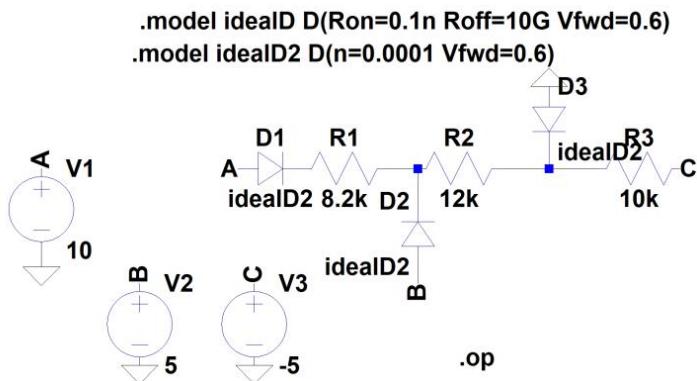

--- Operating Point ---

V(a) :	10	voltage
V(p001) :	9.4	voltage
V(n002) :	-0.231788	voltage
V(n001) :	5.49007	voltage
V(c) :	-5	voltage
V(b) :	5	voltage
I(D2) :	-9.80132e-013	device_current
I(D3) :	4.63576e-013	device_current
I(D1) :	0.000476821	device_current
I(R3) :	0.000476821	device_current
I(R2) :	0.000476821	device_current
I(R1) :	0.000476821	device_current
I(V3) :	0.000476821	device_current
I(V2) :	9.80132e-013	device_current
I(V1) :	-0.000476821	device_current

b)

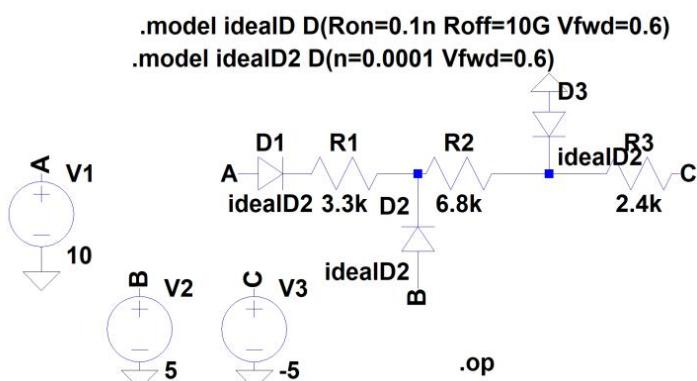

--- Operating Point ---


V(a) :	10	voltage
V(p001) :	9.4	voltage
V(n002) :	-0.600001	voltage
V(n001) :	6.13267	voltage
V(c) :	-5	voltage

```

V(b) : 5 voltage
I(D2) : -2.26534e-012 device_current
I(D3) : 0.000843234 device_current
I(D1) : 0.000990099 device_current
I(R3) : 0.00183333 device_current
I(R2) : 0.000990099 device_current
I(R1) : 0.000990099 device_current
I(V3) : 0.00183333 device_current
I(V2) : 2.26534e-012 device_current
I(V1) : -0.000990099 device_current

```

c)

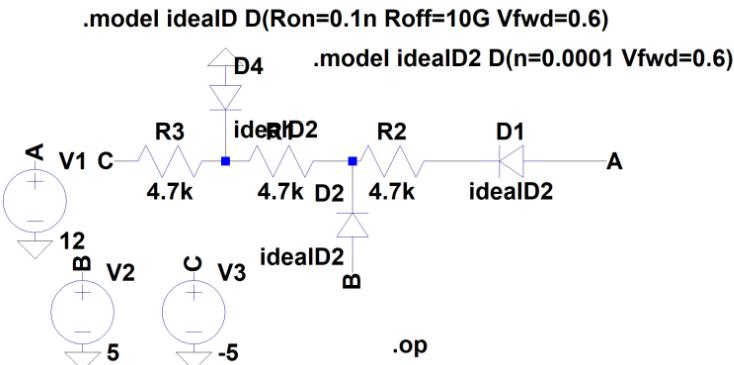


--- Operating Point ---

```

V(n001) : 0.466666 voltage
V(n002) : 5.93333 voltage
V(n003) : 11.4 voltage
V(a) : 12 voltage
V(b) : 5 voltage
V(c) : -5 voltage
I(D4) : -9.33333e-013 device_current
I(D1) : 0.00116312 device_current
I(D2) : -1.86667e-012 device_current
I(R3) : -0.00116312 device_current
I(R2) : -0.00116312 device_current
I(R1) : -0.00116312 device_current
I(V3) : 0.00116312 device_current
I(V2) : 1.86667e-012 device_current
I(V1) : -0.00116312 device_current

```

d)

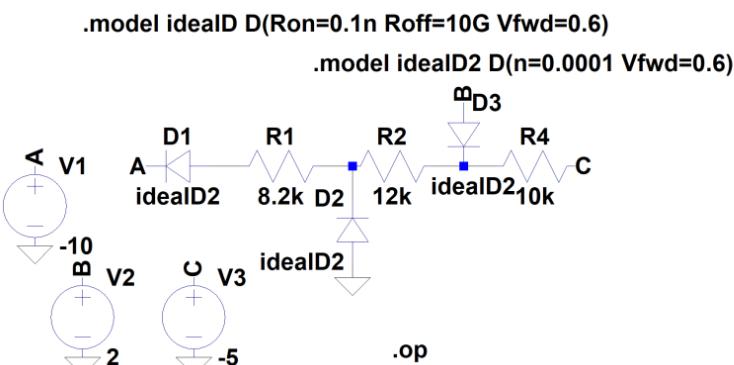


--- Operating Point ---


V(n001) :	-9.4	voltage
V(n002) :	-0.600001	voltage
V(n003) :	1.4	voltage
V(a) :	-10	voltage
V(b) :	2	voltage
V(c) :	-5	voltage
I(D1) :	0.00107317	device_current
I(D3) :	0.000806667	device_current
I(D2) :	0.000906504	device_current
I(R4) :	0.00064	device_current
I(R2) :	-0.000166667	device_current
I(R1) :	-0.00107317	device_current
I(V3) :	0.00064	device_current
I(V2) :	-0.000806667	device_current
I(V1) :	0.00107317	device_current

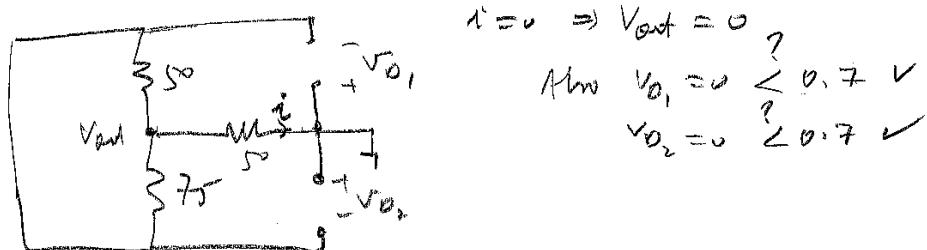Q3 Solution.

When $V_s = 0$ both diodes are OFF. Let's check this.



For small V_s

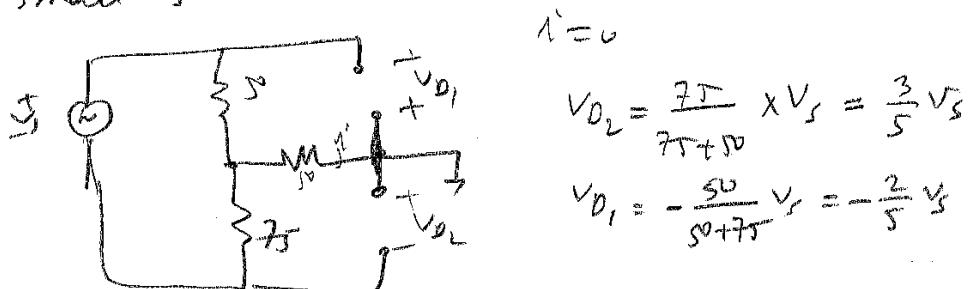

As V_s increases in the +ve direction D_1 is OFF and
 D_2 is ON if $V_{D2} < 0.7$.


$$\Rightarrow \frac{3}{5} V_s < 0.7 \quad V_s < 0.7 \times \frac{5}{3} = \frac{3.5}{3} = 1.1667 \text{ V.}$$

This happens when $8 \sin \omega t = 1.1667$

$$\sin \omega t = \frac{1.1667}{8} \quad \omega t = 0.1464 \text{ rad}$$

$$t = \frac{0.1464}{2\pi \times 10000} = 2.33 \mu\text{sec.}$$

After this time D_2 is ON

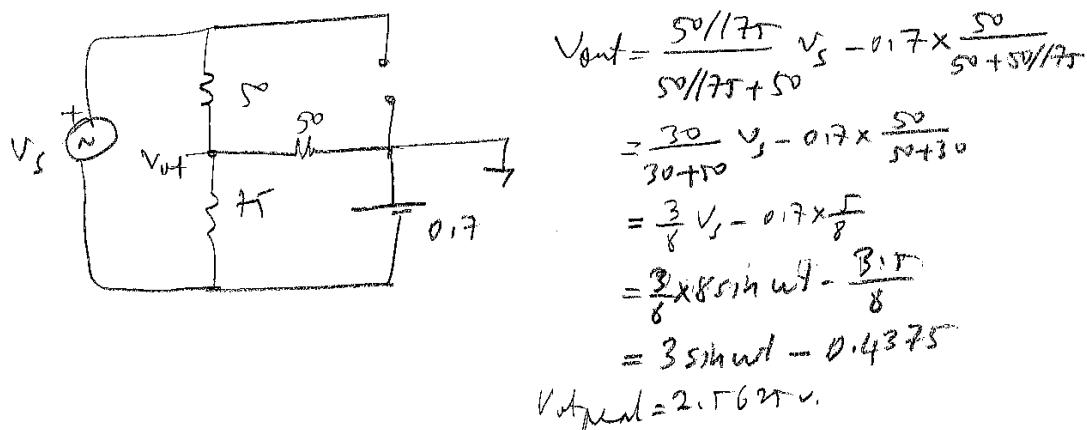

During the negative half cycle as v_s decreases D_2 is off but D_1 is off as long as $V_{D1} = \frac{2}{3} v_s < 0.7$


$$v_s > \frac{5 \times 0.7}{2} = \frac{3.5}{2} = 1.75$$

This happens when $\sin \omega t = 1.75$

$$\omega t = \arcsin\left(\frac{1.75}{5}\right) = 0.2205$$

$\Rightarrow t = 3.5 / \omega$ sec (We have assumed that $t=0$ at the beginning of the -ve cycle)

For more negative values D_1 is on

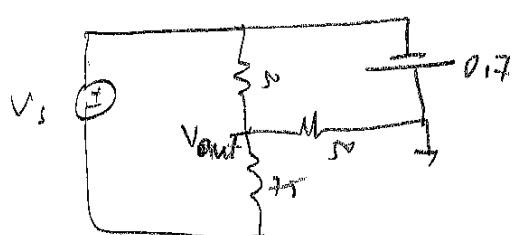


$$\begin{aligned} V_{out} &= -\frac{50/150}{50/150 + 1/175} v_s - 0.7 \times \frac{50}{50 + 50/175} \\ &= \frac{25}{100} v_s - 0.7 \times \frac{50}{80} \quad \frac{3.5}{8} \\ &= -\frac{1}{4} v_s - 0.4375 \end{aligned}$$


If we start time at the beginning of -ve cycle

$$\begin{aligned} V_{out}(t) &= -\frac{1}{4}(-8 \sin \omega t) - 0.4375 \\ &= 2 \sin \omega t - 0.4375 \end{aligned}$$


$$V_{out\text{peak}} = 1.5625$$

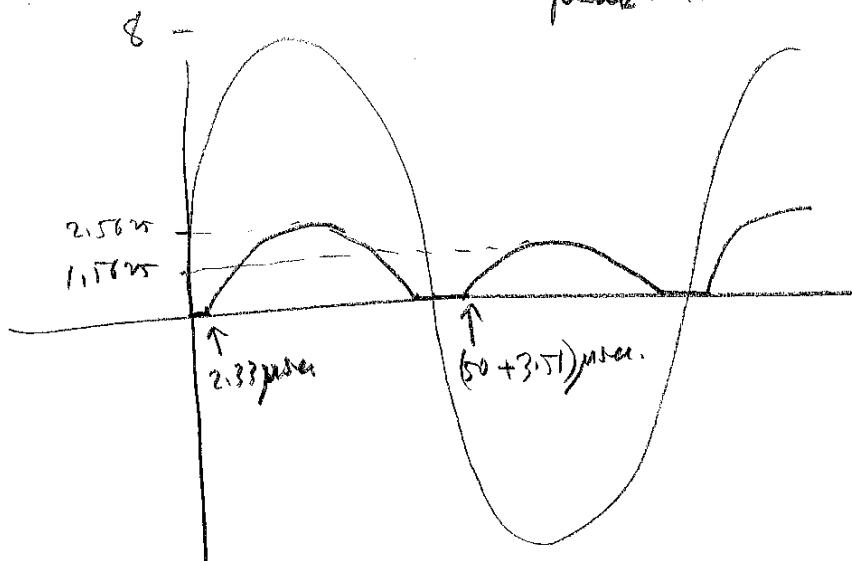

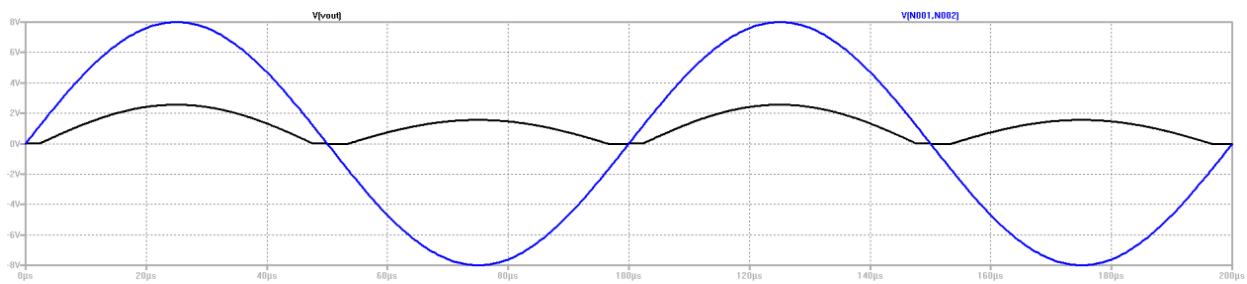
Although not required, we have also solved the problem Q3 using LTSpice and the results are the same



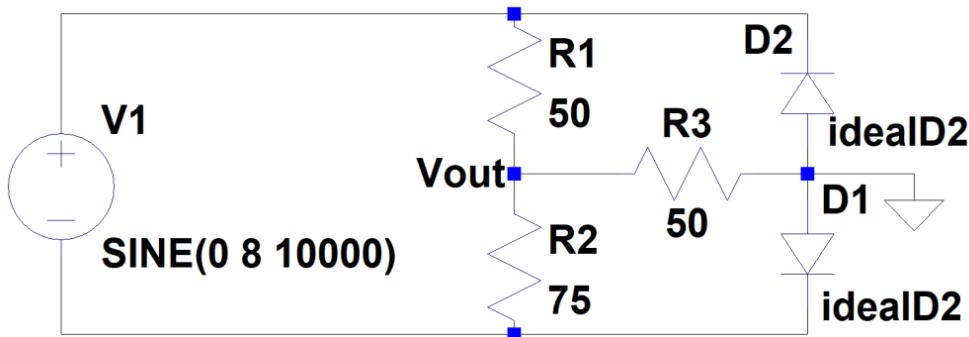
```
.model idealID D(Ron=0.1n Roff=10G Vfwd=0.6)
.model idealID2 D(n=0.0001 Vfwd=0.7)
```



```
.tran 0 0.2m 0 0.00001m
```

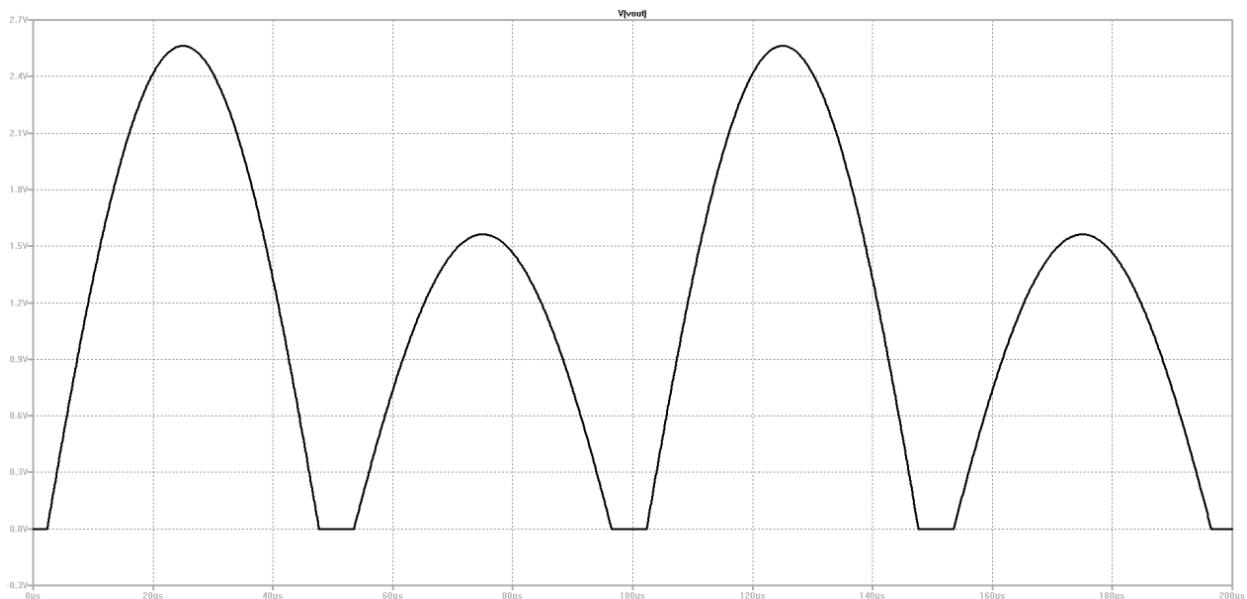

R4 solution

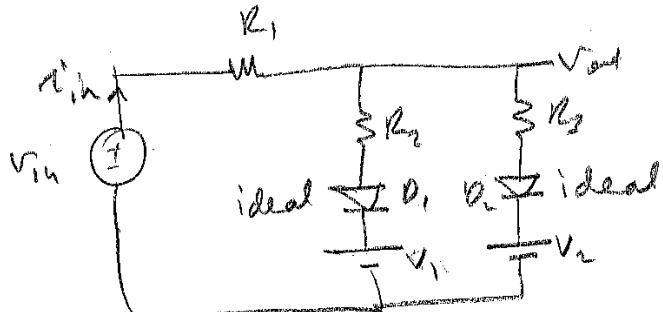

Let us take $V_1 = -5$ and $V_2 = 10\text{V}$. Then

for $V_{in} < -5$, $i_{in} = 0$

For $V_{in} > -5$, R_1 is ON

$$i_{in} = \frac{V_{in} - (-5)}{R_1 + R_2} = \frac{V_{in}}{R_1 + R_2} + \frac{5}{R_1 + R_2}$$

$$\text{slope } \frac{1}{R_1 + R_2} = \frac{3.75}{13.75 - (-5)} = \frac{3.75}{18.75} = \frac{1}{5}$$

$$\Rightarrow R_1 + R_2 = 5k \quad i_{in} = \frac{V_{in}}{5} + 1$$

$$V_{out} = i_{in} \times R_2 = 5$$

When V_{out} reaches V_2 then R_2 also turns on and this is the 2nd break point. At this point $i_{in} = 3.75 \text{ mA}$ and $V_{out} = 3.75 \times R_2 = 5 = V_2$.

After this point, R_3 comes in and changes the slope.

After this point, R_3 comes in and changes the slope.

So let us design until this point.

Since $R_1 = 1k$, let us take $R_2 = 4k$.

Then $3.75 \times 4 = 5 = V_2 = 15\text{V}$. $V_2 = 10\text{V}$

After the break point slope becomes

$$\frac{1}{R_1 + R_2 + R_3} = \frac{6 - 3.75}{19.75 + 5} = \frac{2.25}{24.75} = \frac{9}{21}$$

$$\frac{1}{1 + 4/R_3} = \frac{9}{21} = \frac{1}{1 + 4/R_3} = \frac{4 + R_3}{4 + 4R_3 + 4R_3} = \frac{4 + R_3}{4 + 8R_3} = \frac{9}{21}$$


$$36 + 45R_3 = 84 + 21R_3$$

$$24R_3 = 48 \quad \boxed{R_3 = 2k}$$

O4 solution continued

Alternative solution:

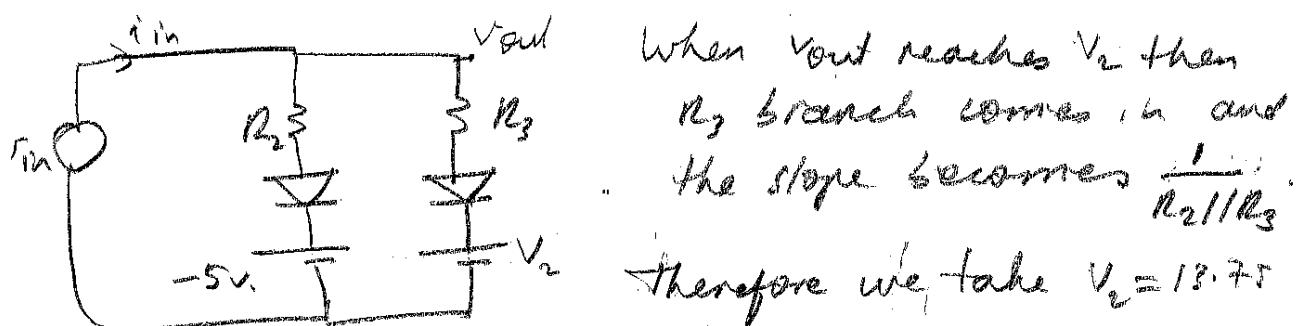As you may have noticed $R_1 + R_2 = 5$ and we have many choices. Let us take $R_1 = 0$ and $R_2 = 5$




$$\text{and } \frac{1}{R_2/R_3} = \frac{9}{21} \quad \frac{R_2 + R_3}{R_2 R_3} = \frac{9}{21} \quad \frac{5 + R_2}{5 R_2} = \frac{9}{21}$$

$$105 + 21 R_2 = 45 R_2$$


$$105 = 24 R_2$$

$$R_2 = \frac{105}{24} = 4.375 \text{ k}\Omega$$

Q5 Solution

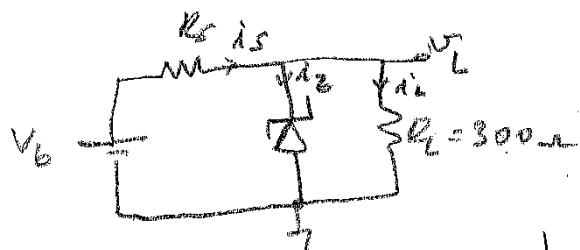

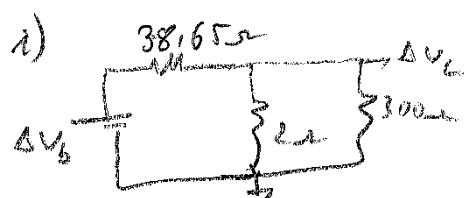
$$b) R_S = \frac{32 \cdot 2 + 4 \cdot 1}{2} = 38.65 \text{ ohms}$$




$$\text{S.R.} = \frac{\Delta V_o}{\Delta V_b} \times 100 = \frac{1.987}{1.987 + 38.65} \times 100 = 4.89\%$$

ii) No load condition:

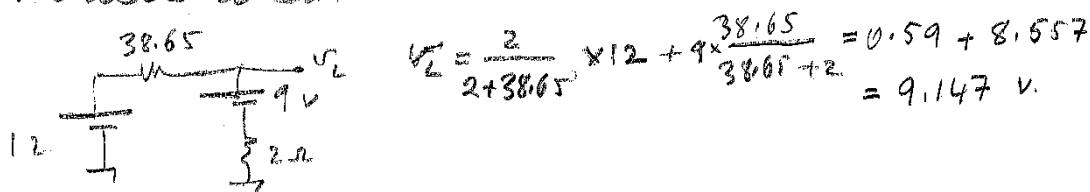


Full load condition

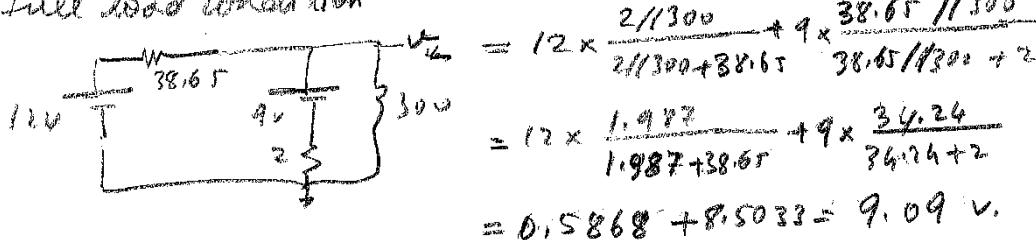


$$\text{L.R.} = \frac{9.147 - 9.09}{9.09} \times 100$$

$$= 0.63\%$$

Q.6 solution

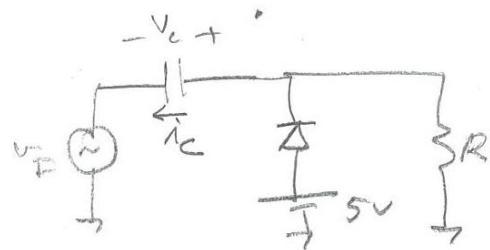

a) During the charging of the capacitor

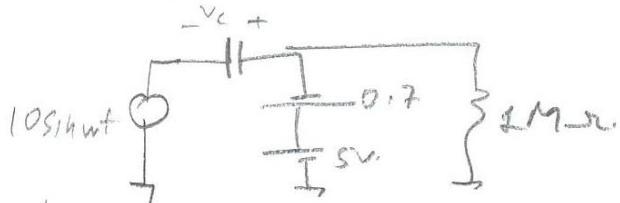

Later on capacitor charges again when V_F becomes less than zero and the formula for capacitor voltage becomes

$$V_C(t) = -0.7 + 5 - (-10 \sin \omega t) \quad (\text{by taking } V_F=0 \text{ as the time } t=0)$$

At the peak V_C becomes $15 - 0.7 = 14.3 \text{ V}$.

During this time $i_C = C \frac{dV_C}{dt} = C \times 10 \omega \cos \omega t$

$$\text{and } i_C \text{ peak} = C \times 10 \omega = 10^{-6} \times 10 \times 100\pi = 3.14 \times 10^{-3} = 3.14 \text{ mA}$$



LTS nice notes

(Please pay attention on the polarities for V_C and i_C we have shown on the circuit above)

Note: In specifying the value of the capacitor we write $1\mu F \text{ } i_C=0$ to also specify that the initial value of the capacitor voltage is 0 v o H.c.


Q6 LTSpice results are given below:


a)

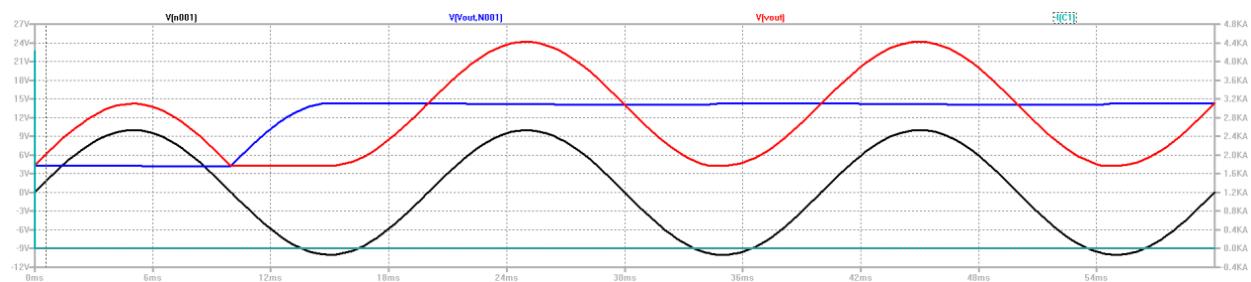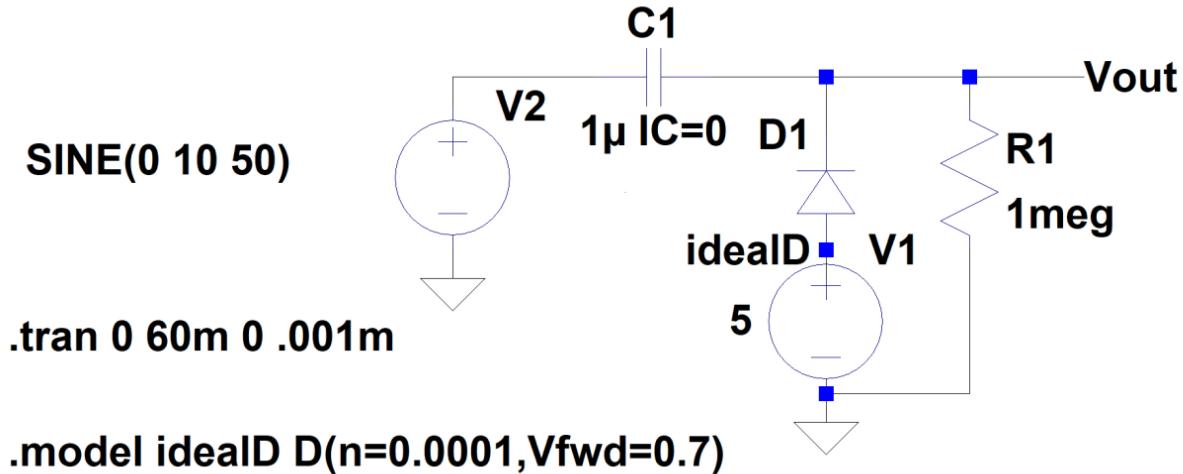

In the figure drawn above the capacitor current is very very large at time $t=0$.

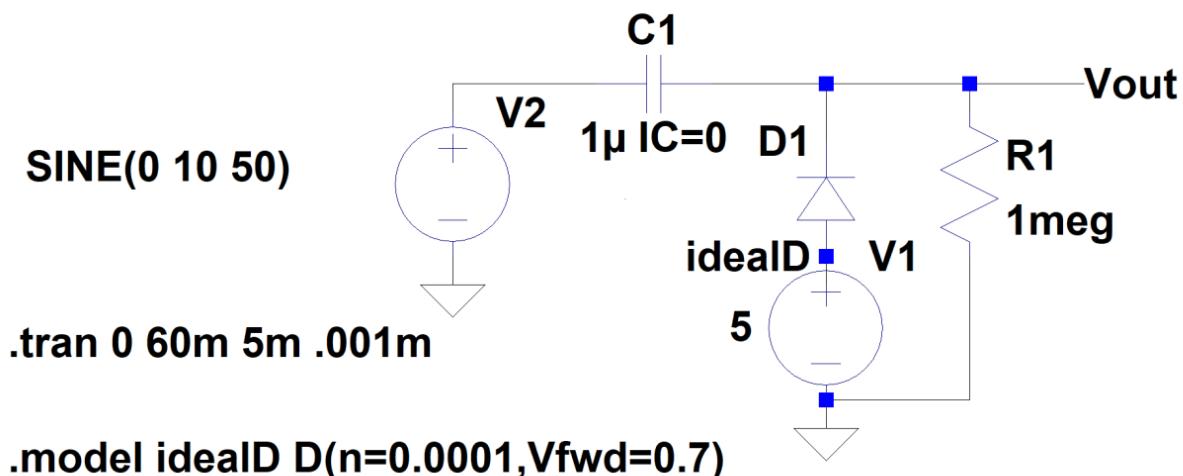To see the current at later times we must decrease the scale . To achieve this we plot the graph starting from $t=5\text{msec}$ which is shown below.



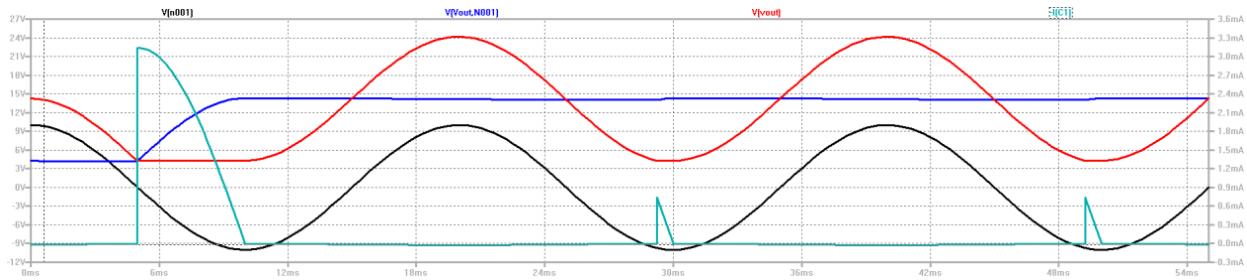

Now the peak current during the second time charging is about 3.14 mA as expected. Later due to discharge through the resistor the cap must recharge at every cycle and the peak current is 73 microA.

b)

When the capacitor is made 100Mohms the peak current at later cycles becomes 74 microA as shown below because ripple on the capacitor is less. Other results are very close.

