
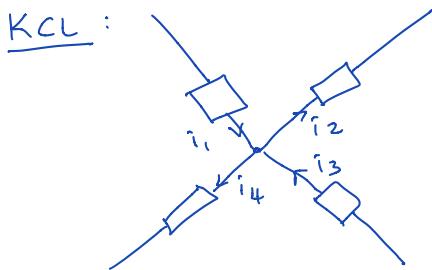


CHAPTER 10 -  $s$ -DOMAIN CIRCUIT ANALYSES


$$-i_1(+)+i_2(+)-i_3(+)+i_4(+) = 0 \quad \text{uniqueness & linearity}$$
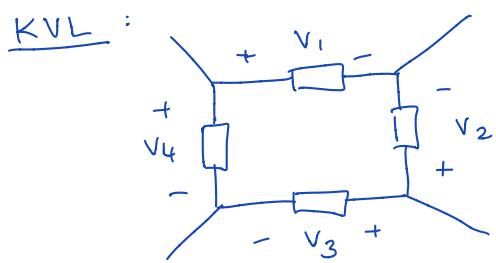
$$\Rightarrow -I_1(s) + I_2(s) - I_3(s) + I_4(s) = 0$$




$$v_1(+) - v_2(+) + v_3(+) - v_4(+) = 0 \quad \text{uniqueness & linearity}$$

$$\Rightarrow V_1(s) - V_2(s) + V_3(s) - V_4(s) = 0$$

\* KCL and KVL retain their form in  $s$ -domain.

### Branch Relations:

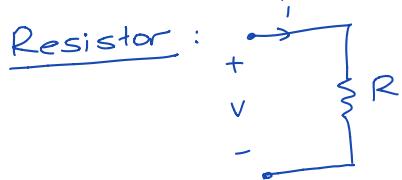


$$v(+) = R i(+)$$

$$V(s) = R \cdot I(s)$$

$\Rightarrow$  resistor retains its form

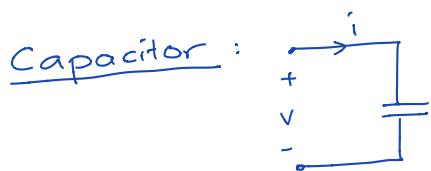In general: any algebraic relation retains its form in  $s$ -domain, due to linearity of Laplace transform.



$$i(+) = C \frac{dv(+)}{dt}$$


$$I(s) = C \cdot [s V(s) - v(0)]$$

$$I(s) = s C V(s) - C v(0)$$

useful for node analysis


$$V(s) = \frac{1}{sC} I(s) + \frac{1}{s} v(0)$$

useful for mesh analysis

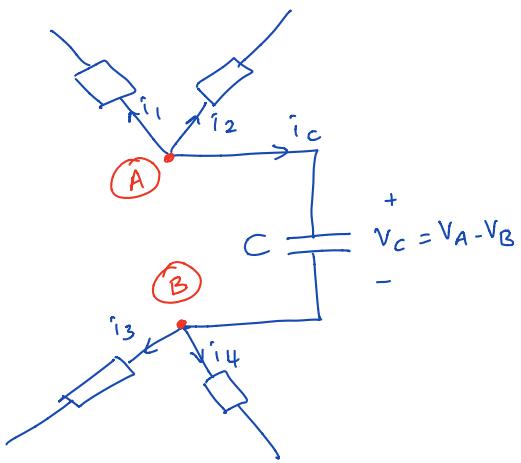Example :KCL at A :

$$I_1 + I_2 + I_c = 0$$


$$I_1 + I_2 + \left[ \frac{1}{SC} (V_A - V_B) - C V_c(0) \right] = 0$$

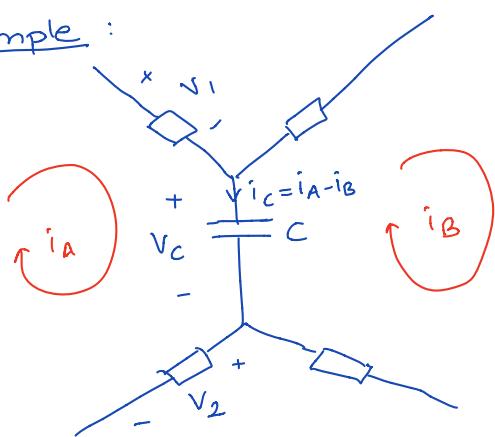Example :KVL at mesh A :

$$\dots + V_1 + V_C + V_2 + \dots = 0$$

$$\dots + V_1 + \left[ \frac{1}{SC} (I_A - I_B) + \frac{1}{S} V_c(0) \right]$$

$$+ V_2 + \dots = 0$$

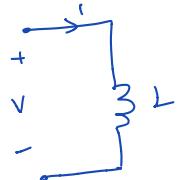Inductor :

$$v(+)=L \frac{di(+)}{dt}$$


$$V(s) = L (s I(s) - i(0))$$

$$V(s) = sL I(s) - L \cdot i(0)$$

useful for mesh analysis


$$I(s) = \frac{1}{sL} V(s) + \frac{1}{s} i(0)$$

useful for node analysis

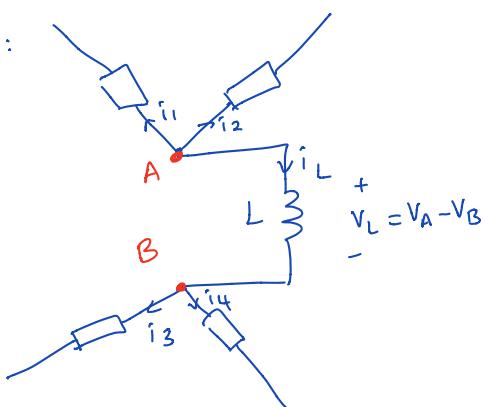Example :KCL at A :

$$I_1 + I_2 + I_L = 0$$


$$I_1 + I_2 + \left[ \frac{1}{sL} (V_A - V_B) + \frac{1}{s} i(0) \right] = 0$$

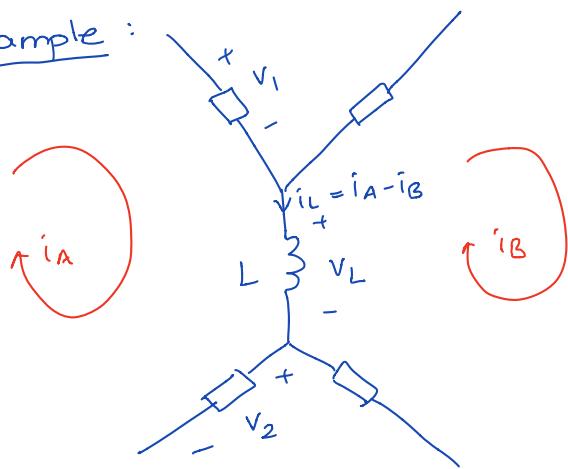Example :KVL at mesh A :

$$\dots + V_1 + V_L + V_2 + \dots = 0$$

$$\dots + V_1 + [sL(I_A - I_B) - L i(0)]$$

$$+ V_2 + \dots = 0$$

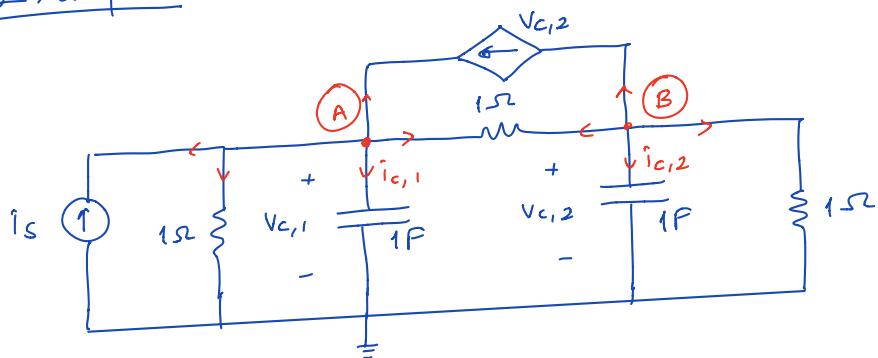Example : Node analysis, General 2<sup>nd</sup>-order circuit

$$V_{c,1}(0) = 2V$$

$$V_{c,2}(0) = 1V$$

$$i_s(t) = v(t) \quad A$$

$$V_{c,2}(t) = ? \quad \text{for } t > 0$$

$$V_{c,2}(t) = V_B(t)$$

$$I_s(s) = \frac{1}{s} \quad , \quad \text{For capacitors: } I(s) = sC V(s) - C V(0)$$

$$\underline{\text{KCL @ A}} : -I_s + \frac{V_A}{1} + \left[ sC_1 V_A - C_1 V_{c,1}(0) \right] - \frac{V_{c,2}}{1} + \frac{V_A - V_B}{1} = 0$$

$$-\frac{1}{s} + V_A + sV_A - 2 - V_B + V_A - V_B = 0$$

$$(s+2)V_A - 2V_B = 2 + \frac{1}{s} = \frac{2s+1}{s}$$

$$\underline{\text{KCL @ B}} : \frac{V_B - V_A}{1} + \frac{V_{c,2}}{V_B} + \left[ sC_2 V_B - C_2 V_{c,2}(0) \right] + \frac{V_B}{1} = 0$$

$$V_B - V_A + V_B + sV_B - 1 + V_B = 0$$

$$V_A = (s+3)V_B - 1$$

\* Insert into first equation:

$$(s+2)[(s+3)V_B - 1] - 2V_B = \frac{2s+1}{s}$$

$$(s^2 + 5s + 6 - 2)V_B = (s+2) + \frac{2s+1}{s}$$

$$(s^2 + 5s + 4)V_B = \frac{s^2 + 4s + 1}{s}$$

(4)

$$V_B(s) = \frac{s^2 + 4s + 1}{s(s^2 + 5s + 4)} = \frac{s^2 + 4s + 1}{s(s+1)(s+4)}$$

$$= \frac{k_1}{s} + \frac{k_2}{s+1} + \frac{k_3}{s+4}$$


$$k_1 = s V_B(s) \Big|_{s=0} = \frac{s^2 + 4s + 1}{(s+1)(s+4)} \Big|_{s=0} = \frac{1}{4}$$

$$k_2 = (s+1)V_B(s) \Big|_{s=-1} = \frac{s^2 + 4s + 1}{s(s+4)} \Big|_{s=-1} = \frac{1 - 4 + 1}{-1 \cdot 3} = \frac{2}{3}$$

$$k_3 = (s+4)V_B(s) \Big|_{s=-4} = \frac{s^2 + 4s + 1}{s(s+1)} \Big|_{s=-4} = \frac{16 - 16 + 1}{-4 \cdot (-3)} = \frac{1}{12}$$

Then,


$$v_{c,2}(t) = v_B(t) = \left[ \underbrace{\frac{1}{4}}_{\text{forced response}} + \underbrace{\frac{2}{3}e^{-t}}_{\text{natural response}} + \underbrace{\frac{1}{12}e^{-4t}}_{\text{natural response}} \right] u(t) \quad \checkmark$$

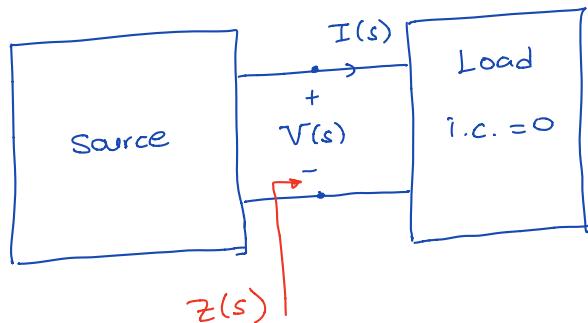Impedance: For zero initial conditions

$$Z(s) = \frac{V(s)}{I(s)} : \text{impedance in s-domain}$$

$$Y(s) = \frac{I(s)}{V(s)} : \text{admittance in s-domain}$$


$$Z(s) = \frac{1}{Y(s)}$$

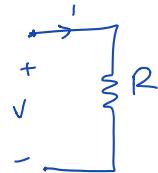Resistor:

$$V(s) = R \cdot I(s)$$

$$Z_R(s) = R$$


$$Y_R(s) = \frac{1}{R}$$

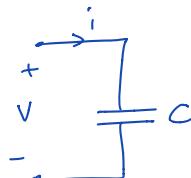Capacitor:

$$I(s) = sC V(s) - C V(0) \quad \text{assume zero i.c.}$$

$$Z_C(s) = \frac{1}{sC}$$

$$Y_C(s) = sC$$

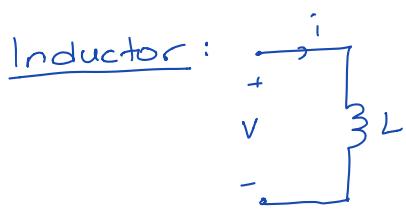

$$V(s) = sL I(s) - L \dot{I}(0) \rightarrow \text{assume zero i.c.}$$


$$Z_L(s) = sL$$

$$Y_L(s) = \frac{1}{sL}$$


(5)

- \* Series/parallel connection: works the same as in resistive circuits.
- \* voltage / current division: works the same as in resistive circuits.

Example:

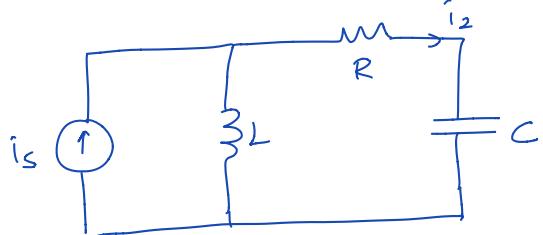

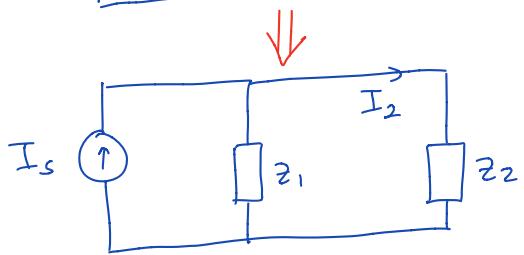Find  $I_2(s)$  assuming zero initial conditions.



$$Z_2 = R + \frac{1}{sC}$$

$$Z_1 = sL$$

$$I_2(s) = \frac{Z_1}{Z_1 + Z_2} \cdot I_s(s) \quad (\text{current divider})$$

$$= \frac{sL}{\frac{RSC+1}{SC} + sL} \cdot I_s(s) = \frac{s^2LC}{s^2LC + sRC + 1} \cdot I_s(s)$$

Superposition in s-domain


any solution = (zero-state solution) + (zero-input solution)

zero-state solution = initial conditions are zero,  
only the inputs are effective

zero-input solution = inputs are zero,  
only initial conditions are effective

## How to deal with the initial conditions

Capacitor :

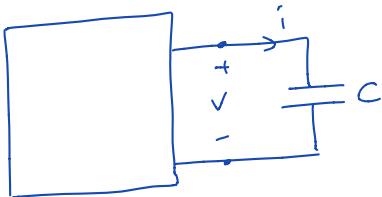


$$i(t) = C \frac{dV(t)}{dt}$$

$$I(s) = C [sV(s) - v(0)]$$

$$I(s) = \underbrace{sC}_{\text{admittance of capacitor}} V(s) - C v(0)$$

admittance of capacitor

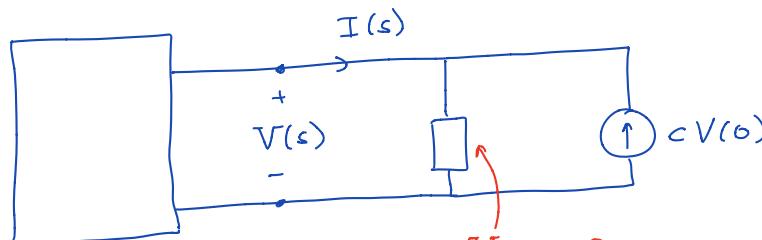

Norton model


$$Y_c = sC \quad Z_c = \frac{1}{sC}$$

capacitor with zero i.c.


$$* \text{ OR, equivalently : } V(s) = \underbrace{\frac{1}{sC} I(s)}_{\text{impedance of capacitor}} + \underbrace{\frac{1}{s}}_{v(0)} v(0)$$

impedance of capacitor

Thevenin model

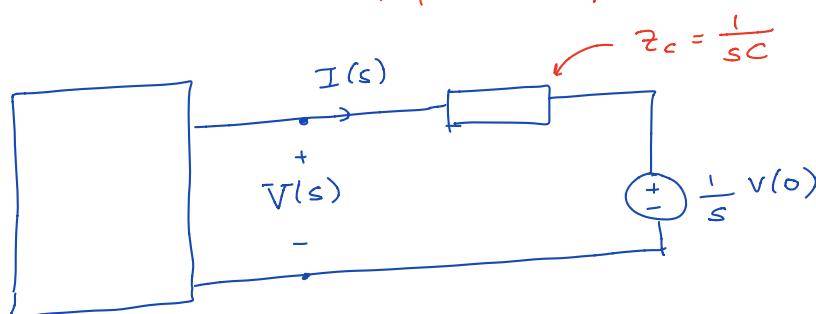

Inductor :

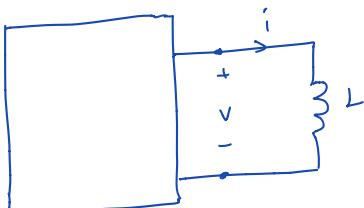


$$v(t) = L \frac{di(t)}{dt}$$

$$V(s) = L [sI(s) - i(0)]$$

$$V(s) = \underbrace{sL}_{\text{impedance of inductor}} I(s) - L i(0)$$


impedance of inductor

Thevenin model

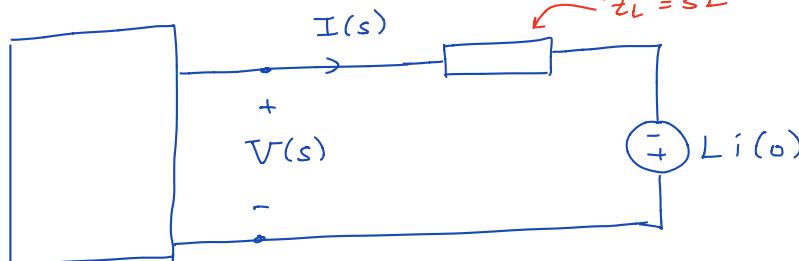

\* OR, equivalently :  $I(s) = \frac{1}{sL} \cdot V(s) + \frac{1}{s} i(0)$

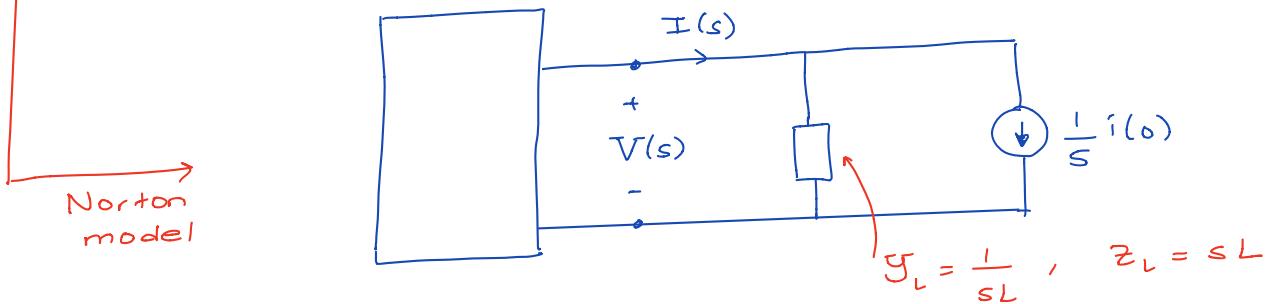$\underbrace{\hspace{1cm}}$   
admittance of inductor




\* These transformations are known as initial condition transformations.

\* Application of superposition as follows:

- Apply an appropriate initial condition transformation.  
- Treat initial conditions as equivalent independent sources in s-domain.


- Apply superposition to this circuit in s-domain.  
- The contributions of equivalent sources due to initial conditions give the zero-input response.  
- The contributions of actual independent sources give the zero-state response.

Example :

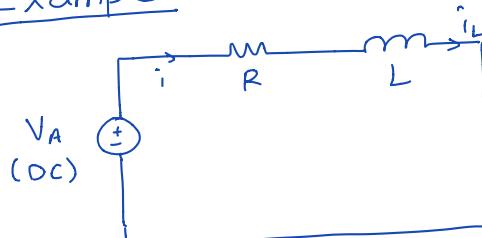


$i_L(0)$  is given.

Find  $i(+), t \geq 0$ .

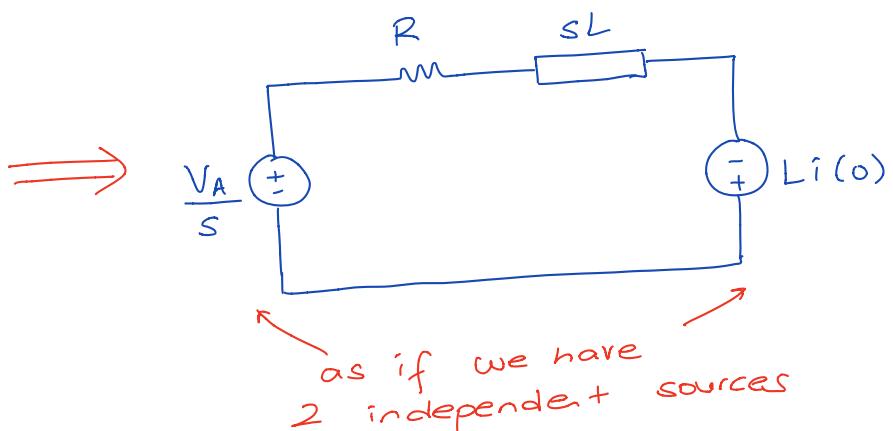

Apply superposition:


\* Contribution of  $V_A$ :

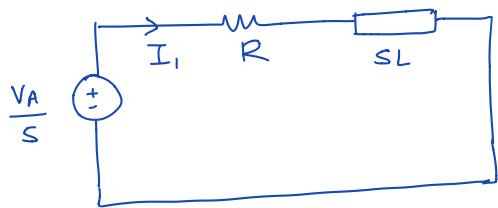

$$I_1 = \frac{V_A/s}{R + sL} = \frac{V_A}{s(sL + R)}$$

$$= \frac{V_A/L}{s(s + \frac{R}{L})}$$

\* Contribution of  $i_L(0)$ :

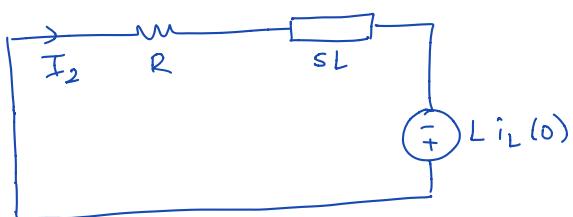

$$I_2 = \frac{L i_L(0)}{R + sL}$$

$$= \frac{i_L(0)}{s + \frac{R}{L}}$$

\* Now,

$$I(s) = I_1(s) + I_2(s) = \frac{V_A/L}{s(s + R/L)} + \frac{i_L(0)}{s + R/L}$$

$\underbrace{\qquad\qquad\qquad}_{\text{zero-state}}$        $\underbrace{\qquad\qquad\qquad}_{\text{zero-input}}$

$$I(s) = \frac{k_1}{s} + \frac{k_2}{s + R/L} + \frac{i_L(0)}{s + R/L}$$

$$k_1 = s I_1(s) \Big|_{s=0} = \frac{V_A/L}{s + R/L} \Big|_{s=0} = \frac{V_A}{R}$$

$$k_2 = (s + R/L) \cdot I_1(s) \Big|_{s=-R/L} = \frac{V_A/L}{s} \Big|_{s=-R/L} = -\frac{V_A}{R}$$


\* Finally,

$$i(t) = \left[ \underbrace{\frac{V_A}{R}}_{\text{zero-state response}} - \underbrace{\frac{V_A}{R} \cdot e^{-\frac{R}{L}t}}_{\text{natural response}} + i_L(0) \cdot e^{-\frac{R}{L}(t)} \right] u(t)$$

$\underbrace{\qquad\qquad\qquad}_{\text{forced}}$        $\underbrace{\qquad\qquad\qquad}_{\text{natural response}}$


$\underbrace{\qquad\qquad\qquad}_{\text{zero input response}}$

Example :

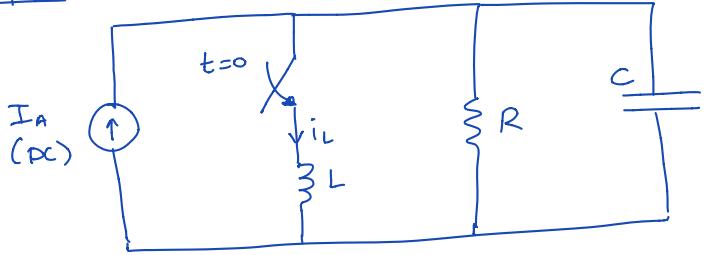


$$i_L(0) = 0, \quad V_C(0) = I_A \cdot R$$


$$V_C(+)=? \text{ for } + \geq 0.$$

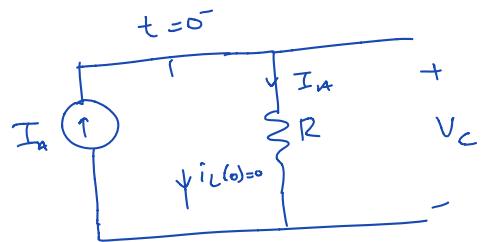


↓ to s-domain

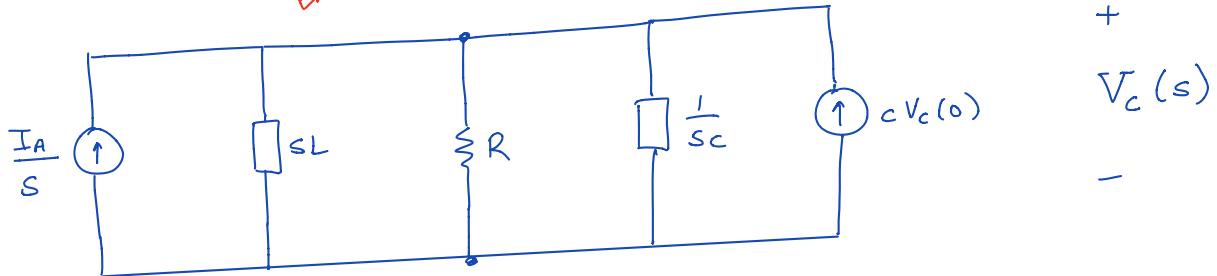


Thevenin-Norton Equivalent Circuits :

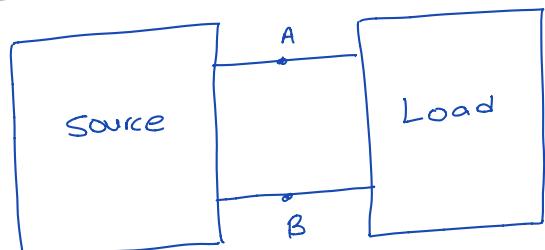


≡

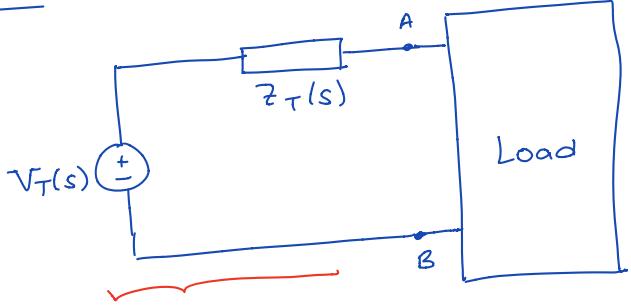

Thevenin equivalent

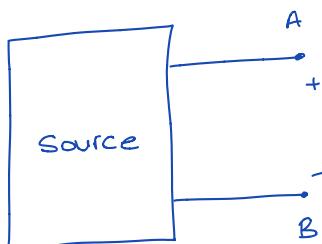

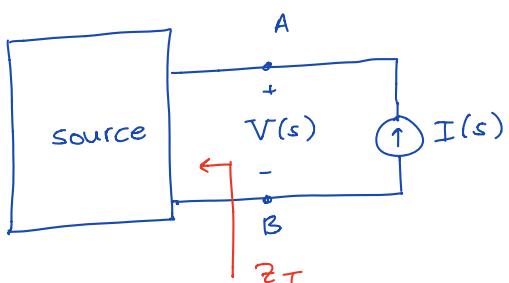
$V_T(s)$  : open circuit voltage in s-domain.  
Keep all independent sources inside the source part, including initial condition sources.



Kill all independent sources inside the source part, including initial condition sources.


$$Z_T(s) = \frac{V(s)}{I(s)}$$

Norton equivalent :

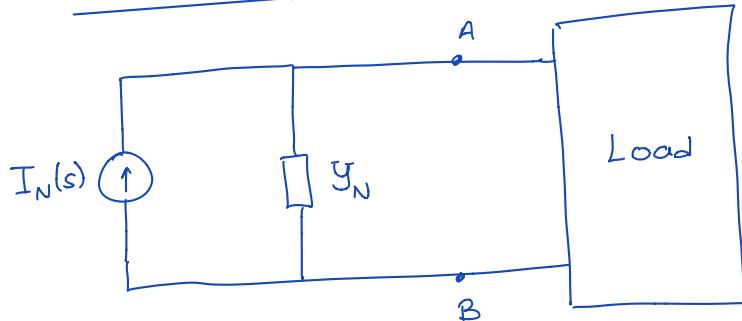


$$Z_T = \frac{1}{Y_N} = Z_N$$

$$Z_T = \frac{V_T(s)}{I_N(s)}$$

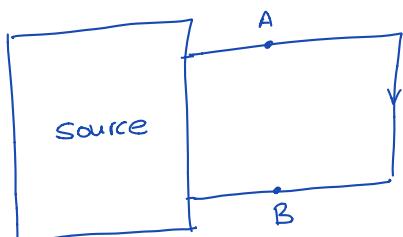

$I_N(s)$  : short circuit current in  $s$ -domain.  
Keep all independent sources inside the source part, including the initial condition sources.

Example :

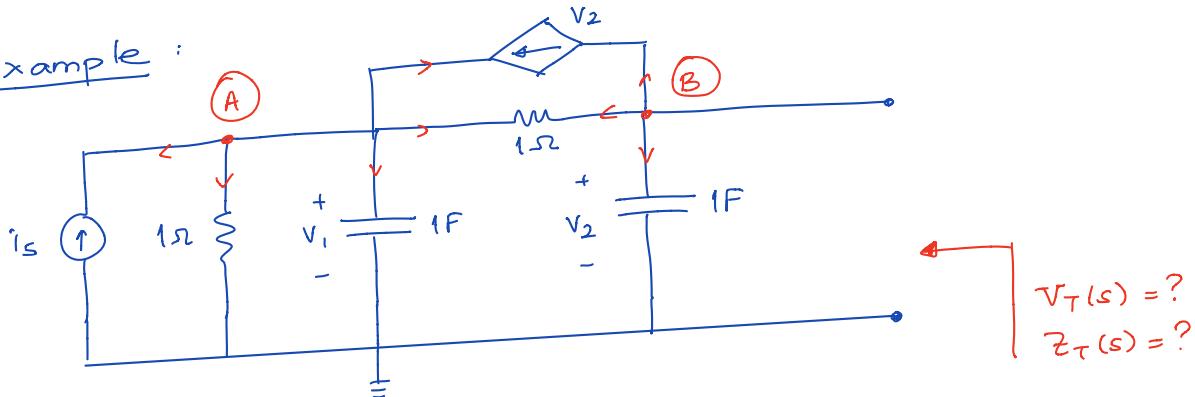

Assume zero-state (i.e., zero initial conditions)

$$V_2 = V_B$$

\*  $V_T(s)$  :

$$V_T = V_B$$

$$\text{KCL @ A} : -I_s + \frac{V_A}{1} + \frac{V_A}{\frac{1}{s \cdot 1}} + \frac{V_A - V_B}{1} - V_B = 0$$

$$(s+2)V_A - 2V_B = I_s \quad \dots \quad (\text{Eqn. 1})$$

$$\text{KCL @ B} : V_B + \frac{V_B - V_A}{1} + \frac{V_B}{\frac{1}{s \cdot 1}} = 0$$

$$(s+2)V_B = V_A$$


Insert into Eqn. 1:

$$(s+2)(s+2)V_B - 2V_B = Is$$

$$(s^2 + 4s + 2)V_B = Is$$

$$V_T(s) = V_B(s) = \frac{Is(s)}{s^2 + 4s + 2}$$

\*  $Z_T$ : kill all independent sources

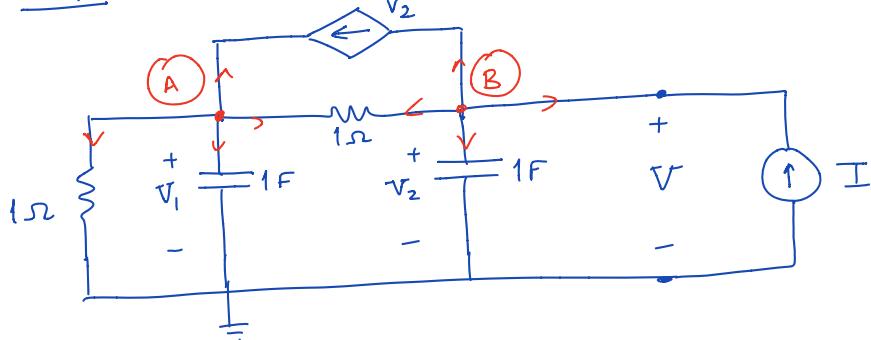

$$V_2 = V_B = V$$

$$Z_T(s) = \frac{V(s)}{I(s)}$$

$$\text{KCL at } A: \frac{V_A}{1} + \frac{V_A}{\frac{1}{s \cdot 1}} + \frac{V_A - V_B}{1} - V_B = 0$$

$$(s+2)V_A = 2V_B = 2V \Rightarrow V_A = \frac{2V}{s+2}$$

$$\text{KCL at } B: \frac{V_B - V_A}{1} + V_B + \frac{V_B}{\frac{1}{s \cdot 1}} - I = 0$$

$$(s+2)V_B - V_A = I$$


$$(s+2)V - \frac{2V}{s+2} = I$$

$$\frac{(s^2 + 4s + 2)}{s+2} V = I$$

$$Z_T(s) = \frac{V}{I} = \frac{s+2}{s^2 + 4s + 2}$$

\* If we had initial conditions :

12)

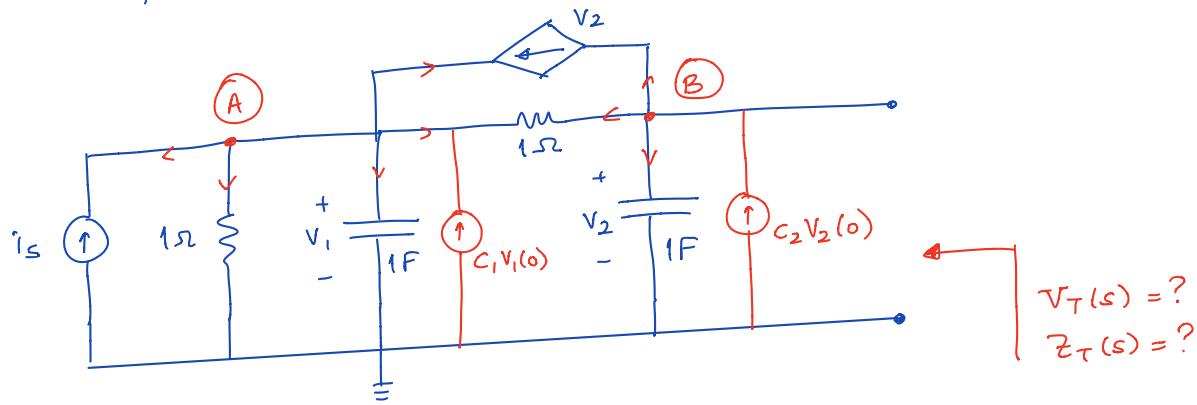

- \* Now,  $V_T(s)$  will depend on  $v_1(0), v_2(0)$ , and  $I_{S(s)}$ .
- \*  $Z_T(s)$  remains the same as in zero initial condition case.