
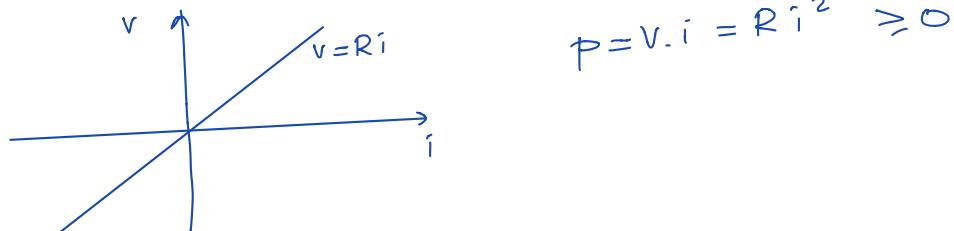


CHAPTER 4 : ACTIVE CIRCUITS

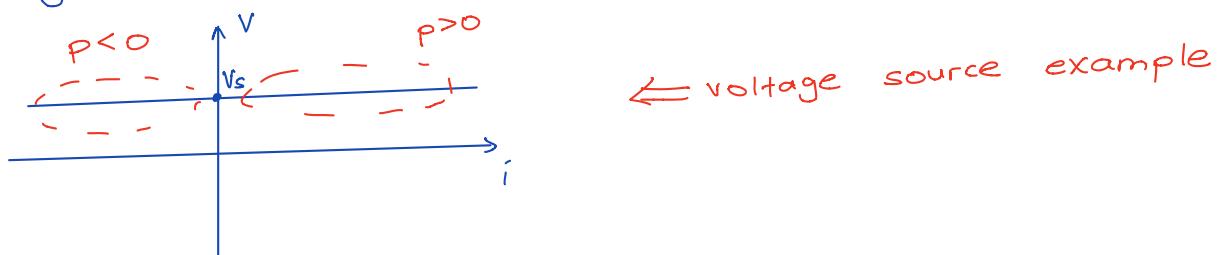
- * A circuit element is called passive if for all possible cases we have $p = v \cdot i \geq 0$. Otherwise, it is called an active element.
- * Hence, an active element satisfies $p < 0$ for some cases (not necessarily for all possible cases).
- * Typical passive element : Linear resistor with $R \geq 0$



- * Typical active element : independent sources



Dependent Sources :

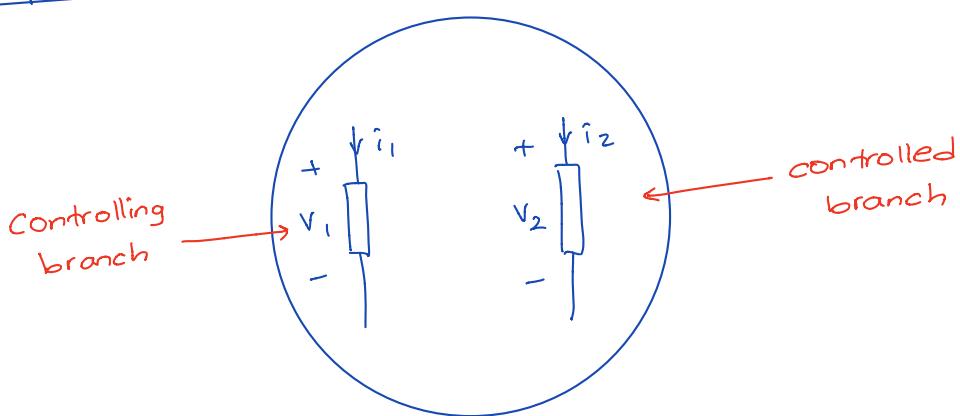

- * A branch voltage/current (v_2, i_2) depends on another branch voltage/current (v_1, i_1).


* mathematically, this can be expressed in matrix form as:

$$\begin{bmatrix} v_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} k_{11} & k_{12} \\ k_{21} & k_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ i_1 \end{bmatrix}$$

* In this class, we will represent dependent sources using a diamond symbol.

There are 4 possibilities:

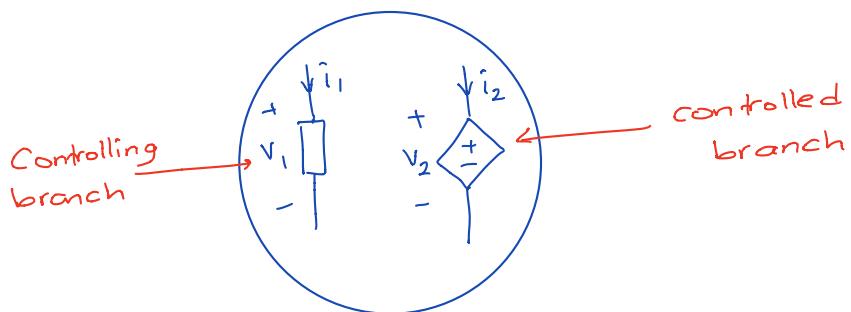
1) Current Controlled Voltage Source (CCVS)



Controlling variable : i_1
Controlled variable : v_2

$$\left. \begin{array}{l} \\ \end{array} \right\} v_2 = r \cdot i_1$$

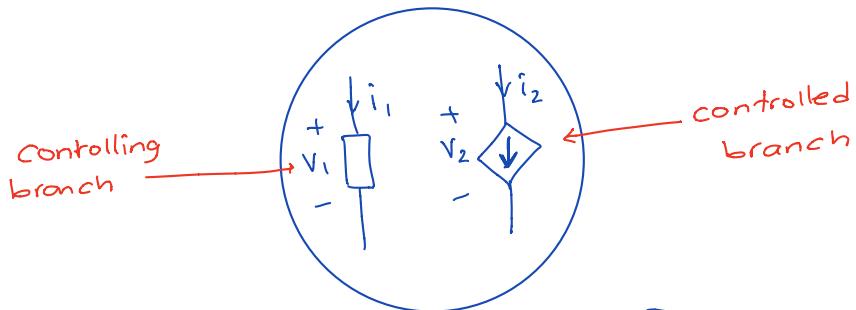
2) Current Controlled Current Source (CCCS)



Controlling variable : i_1
Controlled variable : i_2
Controlled variable : v_2


$$\left. \begin{array}{l} \\ \end{array} \right\} i_2 = \beta \cdot i_1$$

Example : BJT transistors

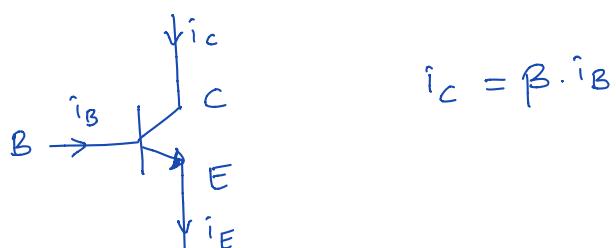

$$i_C = \beta \cdot i_B$$

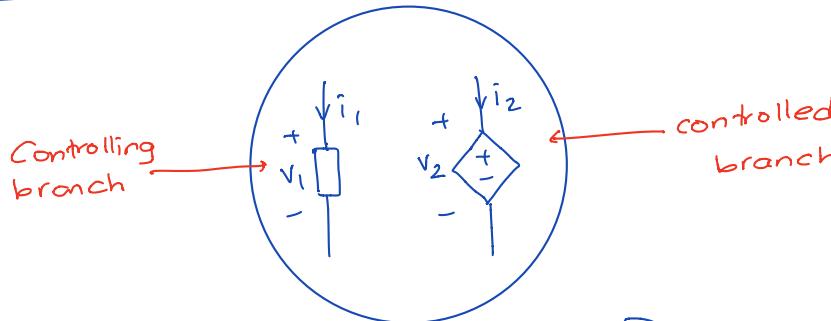
3) Voltage Controlled Voltage Source (VCVS)




Controlling variable: v_1
Controlled variable: v_2

$$\} \quad v_2 = \mu \cdot v_1$$

Example : OPAMP

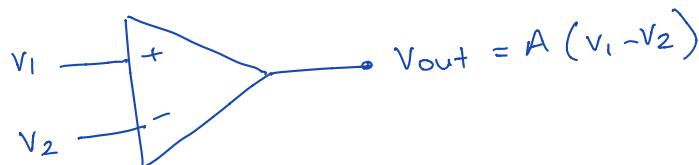

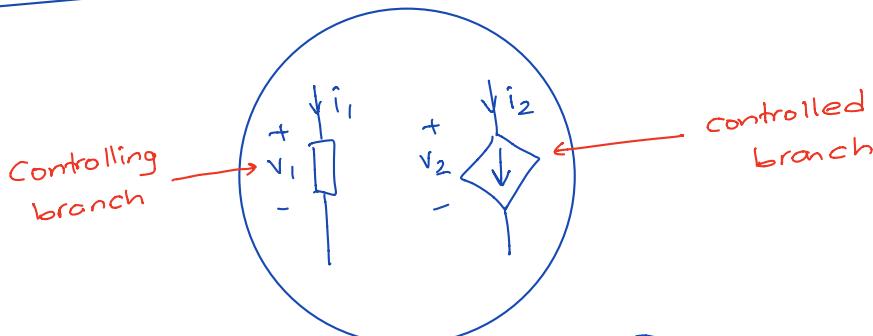4) Voltage Controlled Current Source (VCCS)





Controlling variable: v_1
Controlled variable: i_2

$$\} \quad i_2 = g \cdot v_1$$

* KCL and KVL can be written the same way.
For element relations: $Mv + Ni = u$,
only the entries of M and/or N will change.
 \Rightarrow Linearity is preserved.

Consequence: Superposition, Thévenin / Norton equivalence still apply.

Example :

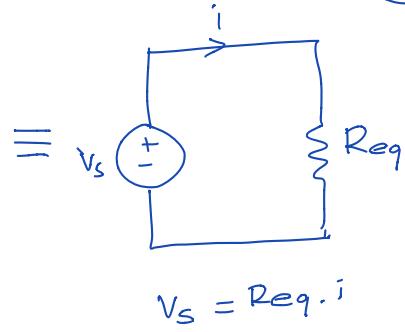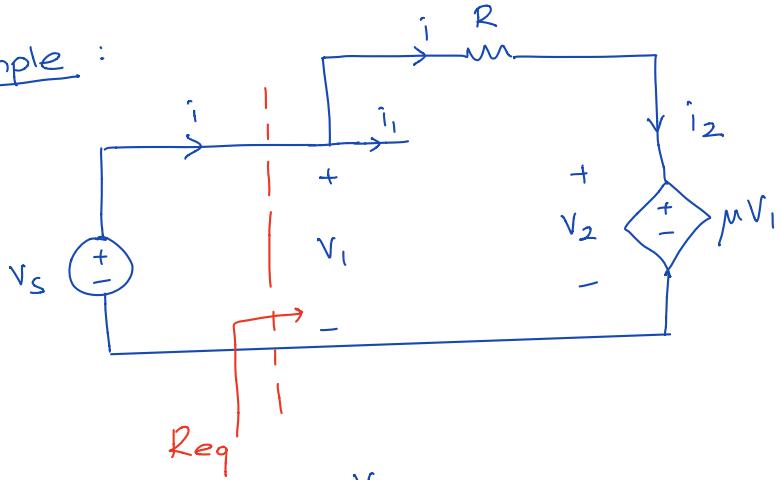

$$* \text{ Find } \text{Req} = \frac{v_s}{i}$$

$$\underline{\text{KVL}} : v_1 = R \cdot i + \mu v_1 \Rightarrow (1 - \mu) v_1 = R \cdot i$$

$$\text{Also} : v_1 = v_s$$

$$\text{so, } (1 - \mu) v_s = R \cdot i$$

$$\text{Req} = \frac{v_s}{i} = \frac{R}{1 - \mu}$$

Note : if $\mu > 1 \Rightarrow \text{Req} < 0 \Rightarrow \text{negative resistance!!}$

$$* P_2 = v_2 \cdot i_2 = \mu v_s \cdot i = \mu v_s \cdot \frac{(1 - \mu) v_s}{R}$$

$$= \frac{\mu (1 - \mu) v_s^2}{R}$$

$$P_2 < 0 \text{ when } \mu > 1$$


$$(\text{Note that } P_2 > 0 \text{ when } 0 < \mu < 1)$$

Node Analysis with Dependent Sources

Basic steps are the same as before.

modification : Add element relations for dependent sources to the list of KCL equations.

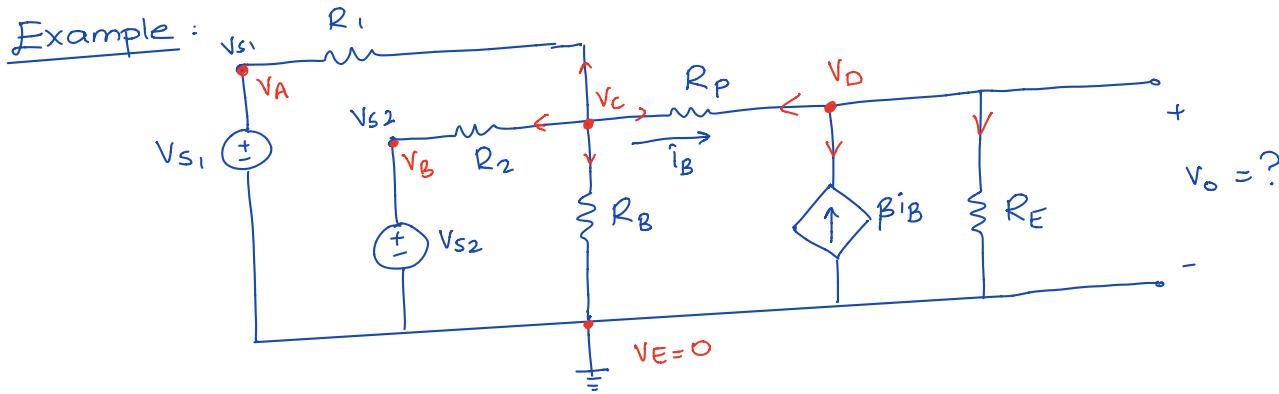Result : We will have $(n-1+x)$ equations in terms of $(n-1)$ node voltages + x new equations for dependent sources.



$$V_A = V_{S1}$$

$$V_B = V_{S2}$$

$$\text{KCL at } C : G_1(V_C - V_A) + G_2(V_C - V_B) + G_B \cdot V_C + G_P \cdot (V_C - V_D) = 0$$

$$(G_1 + G_2 + G_B + G_P)V_C - G_P V_D = G_1 \cdot V_{S1} + G_2 \cdot V_{S2}$$

$$\text{KCL at } D : G_P(V_D - V_C) - \beta \cdot i_B + G_E \cdot V_D = 0$$

$$\text{Extra equation: } i_B = G_P \cdot (V_C - V_D)$$

Insert into second equation:

$$G_P(V_D - V_C) - \beta \cdot G_P(V_C - V_D) + G_E \cdot V_D = 0$$

$$-G_P(1+\beta)V_C + [G_P(1+\beta) + G_E] \cdot V_D = 0$$

Write in matrix form:

$$\begin{bmatrix} (G_1 + G_2 + G_B + G_P) & -G_P \\ -G_P(1+\beta) & G_P(1+\beta) + G_E \end{bmatrix} \begin{bmatrix} V_C \\ V_D \end{bmatrix} = \begin{bmatrix} G_1 \cdot V_{S1} + G_2 \cdot V_{S2} \\ 0 \end{bmatrix}$$

* Note that the symmetry of the conductance matrix is broken when there are dependent sources.

mesh Analysis with Dependent Sources



Basic steps are the same as before

modification: Add the element relations for the dependent sources to the list of KVL equations.

Result : We will have $(b-n+1+y)$ equations

in terms of $(b-n+1)$ mesh currents
+ y new equations for dependent sources.

Example :

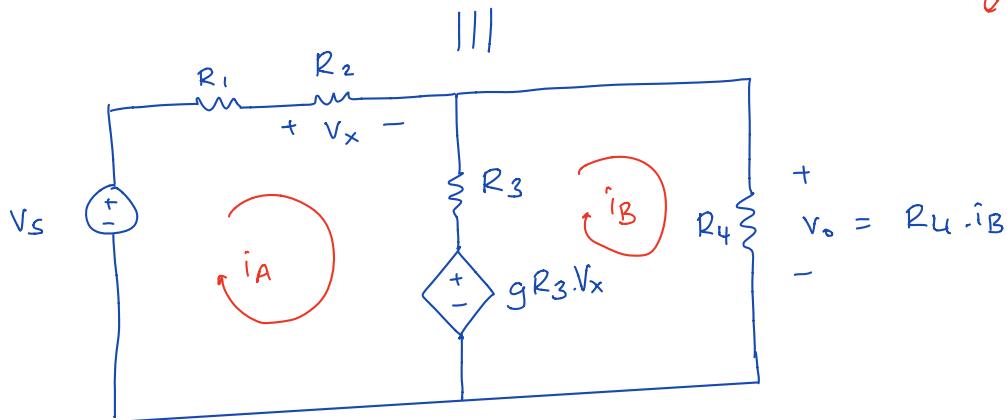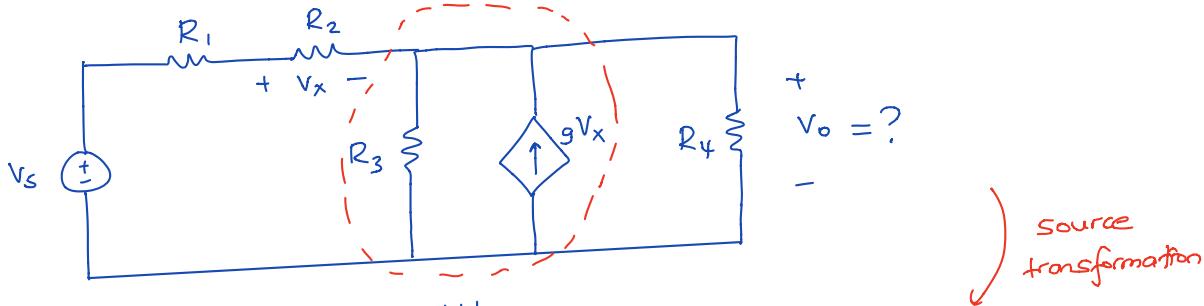

After reduction:

$$\text{mesh A: } R_1 \cdot i_A + R_2 \cdot i_A + R_3(i_A - i_B) + gR_3 V_x - V_s = 0$$

$$(R_1 + R_2 + R_3)i_A - R_3 i_B + gR_3 V_x = V_s$$

$$\text{mesh B: } R_4 \cdot i_B - gR_3 V_x + R_3(i_B - i_A) = 0$$

$$-R_3 \cdot i_A + (R_3 + R_4)i_B - gR_3 V_x = 0$$

$$\text{Extra equation: } V_x = R_2 \cdot i_A$$

$$\text{Re-write: mesh A: } (R_1 + R_2 + R_3 + gR_2 R_3)i_A - R_3 i_B = V_s$$

$$\text{mesh B: } -(R_3 + gR_2 R_3)i_A + (R_3 + R_4)i_B = 0$$

Write in matrix form:

$$\begin{bmatrix} R_1 + R_2 + R_3 + gR_2R_3 & -R_3 \\ -(R_3 + gR_2R_3) & (R_3 + R_4) \end{bmatrix} \begin{bmatrix} i_A \\ i_B \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \end{bmatrix}$$


7

* Note that the symmetry of the resistance matrix is broken when there are dependent sources.


Superposition, Thévenin, Norton with Dependent Sources

* Same as before, but keep in mind that dependent sources should be treated as ordinary circuit elements (e.g., like resistors), not as independent sources.

Example :

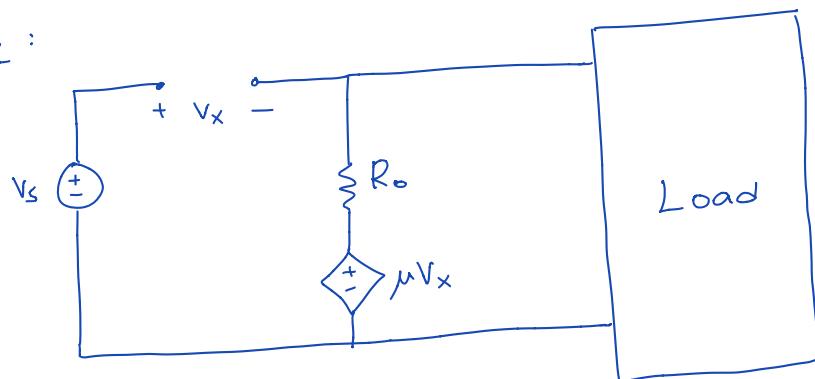

* To find V_T : open circuit voltage

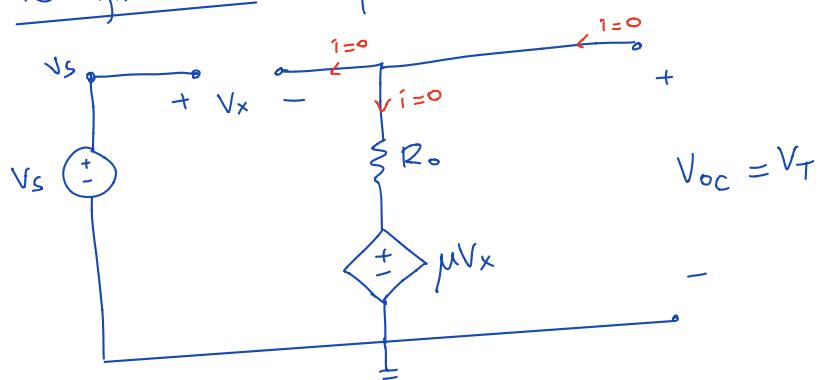

$$\text{From KVL: } V_T = \mu \cdot V_x$$


$$V_x = V_s - V_T$$

$$\left. \right\} V_T = \mu (V_s - V_T)$$


$$(1 + \mu) V_T = \mu \cdot V_s$$

$$V_T = \frac{\mu}{1 + \mu} \cdot V_s$$

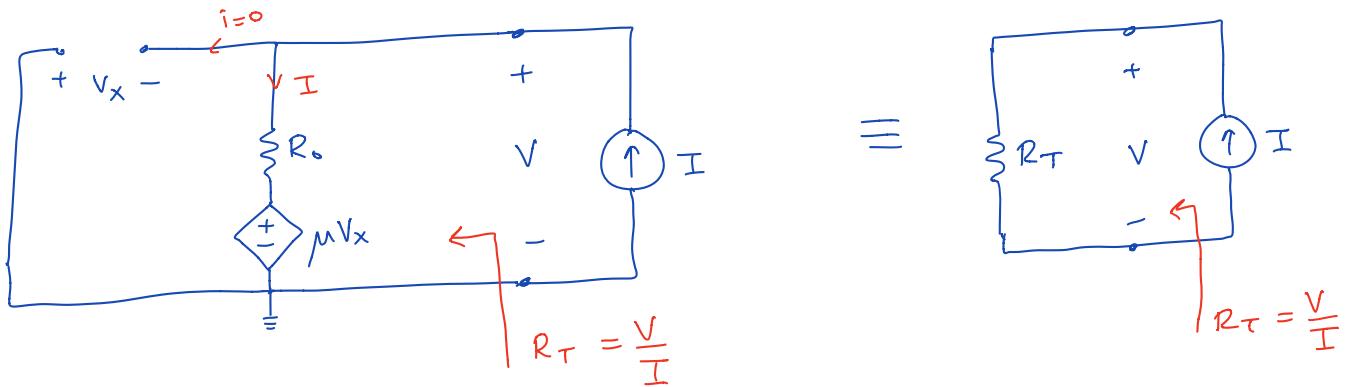
* To find R_T : Kill all independent sources, but keep dependent source as it is.



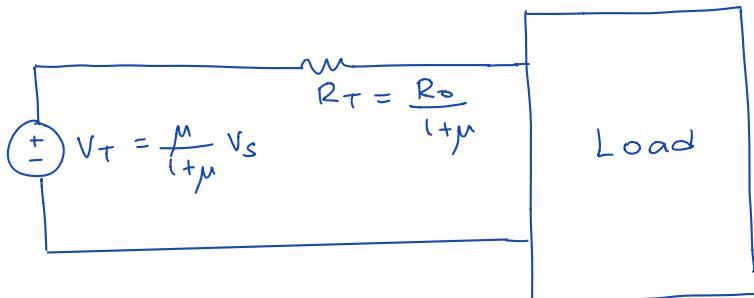
$$\begin{aligned} \text{KVL: } V &= R_o \cdot I + \mu V_x \\ V_x &= -V \end{aligned} \quad \left. \begin{array}{l} V = R_o \cdot I - \mu \cdot V \\ (\mu + 1)V = R_o \cdot I \\ R_T = \frac{V}{I} = \frac{R_o}{\mu + 1} \end{array} \right.$$



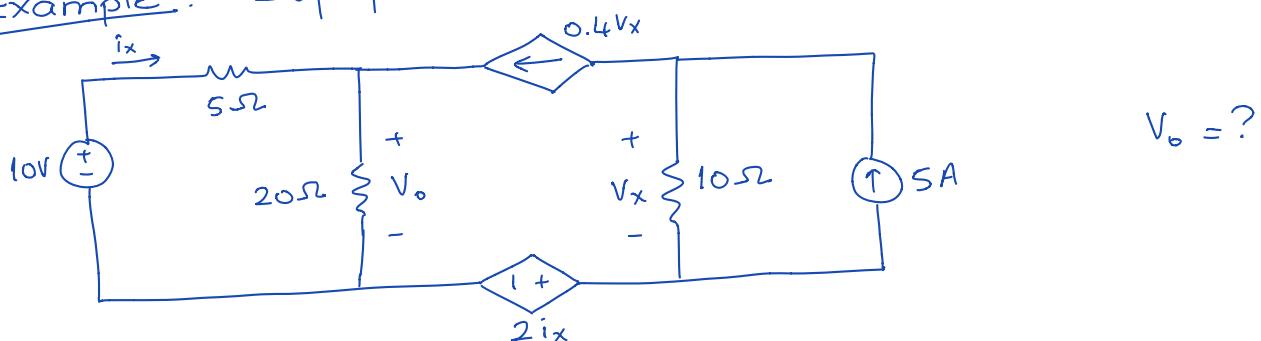Example: Superposition with dependent sources



1) Due to voltage source:

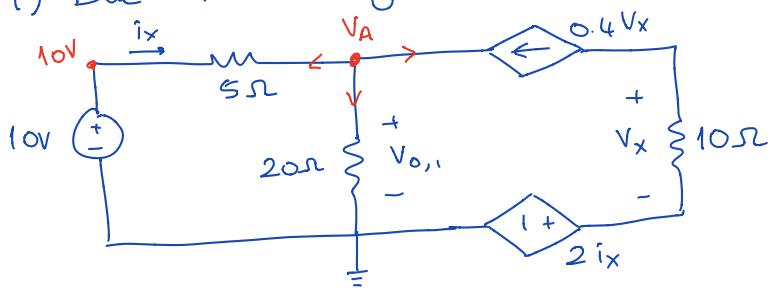


$$\text{KCL at A : } \frac{V_A - 10}{5} + \frac{V_A}{20} - 0.4V_x = 0 \quad (4) \quad (20)$$

$$5V_A = 40 + 8V_x$$

$$\text{Additional eq. : } V_x = 10, (-0.4V_x) = -4V_x \\ 5V_x = 0 \Rightarrow V_x = 0$$

$$\text{Then, } 5V_A = 40 \Rightarrow \boxed{V_A = V_{o,1} = 8V}$$

2) Due to current source:

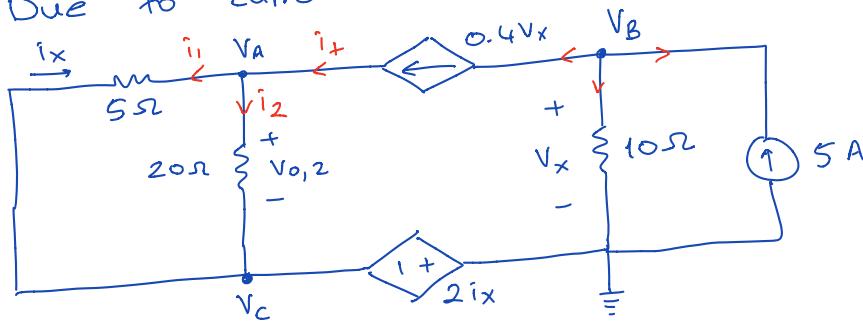

$$\text{KCL at B : } 0.4V_x + \frac{V_B}{10} - 5 = 0 \quad (10) \quad (10)$$

$$V_B = 50 - 4V_x \quad \left. \right\} \quad V_B = 50 - 4V_B$$

$$\text{Additional Eq. : } V_x = V_B \quad 5V_B = 50 \quad V_B = 10V$$


$$* i_t = 0.4V_x = 0.4V_B = 4A \\ i_2 = \frac{5}{5+20} \cdot 4A = 0.8A \quad (\text{current divider})$$

$$\text{Then, } \boxed{V_{o,2} = 20 \cdot i_2 = 16V}$$

$$* \text{ Finally, } V_o = V_{o,1} + V_{o,2} = 8 + 16 = \boxed{24V}$$

OPERATIONAL AMPLIFIERS (OPAMPS)

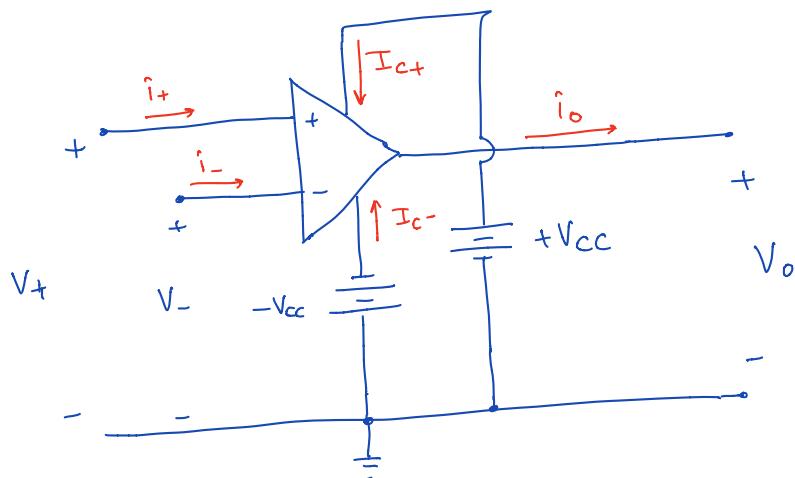
- * OPAMP is an integrated circuit, which is an important building block in many electronic circuits.
- * To operate the OPAMP, we need to connect $+V_{cc}$ and $-V_{cc}$ DC sources to appropriate terminals. Including these connections, an OPAMP has 5 terminals.




$$\text{KCL for OPAMP:} \\ i_o = I_{c+} + I_{c-} + i_+ + i_-$$

So, output current comes from the supply voltages.

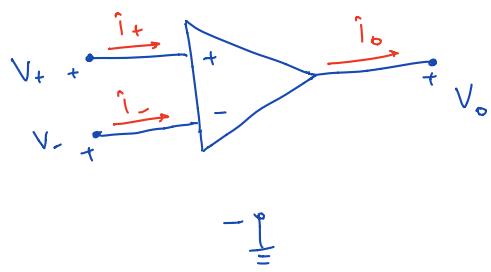- * OPAMP is usually drawn as a 3-terminal device, omitting supplies.



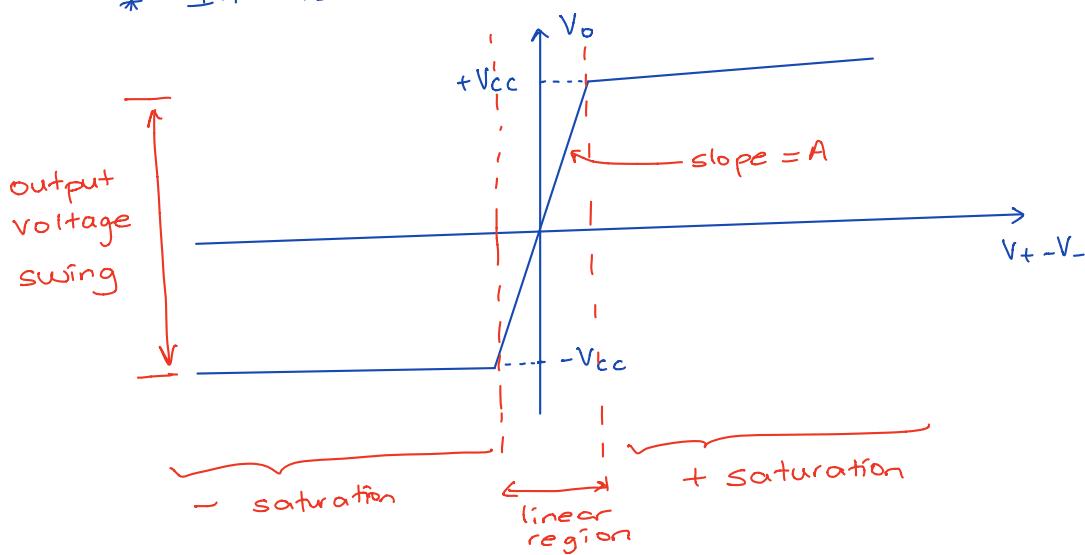- * If turns out, v_o depends on $v_d = v_+ - v_-$.




There are 3 operating modes for an OPAMP:

- * + Saturation: $V_o = +V_{cc}$, when $A(V_+ - V_-) > V_{cc}$
- * Linear Region: $V_o = A(V_+ - V_-)$, when $-V_{cc} < V_o < V_{cc}$
- * - Saturation: $V_o = -V_{cc}$, when $A(V_+ - V_-) < -V_{cc}$

For each mode, we can represent/model the OPAMP by using the elements we have seen so far.



Finite Gain Model:

* In Linear Region:

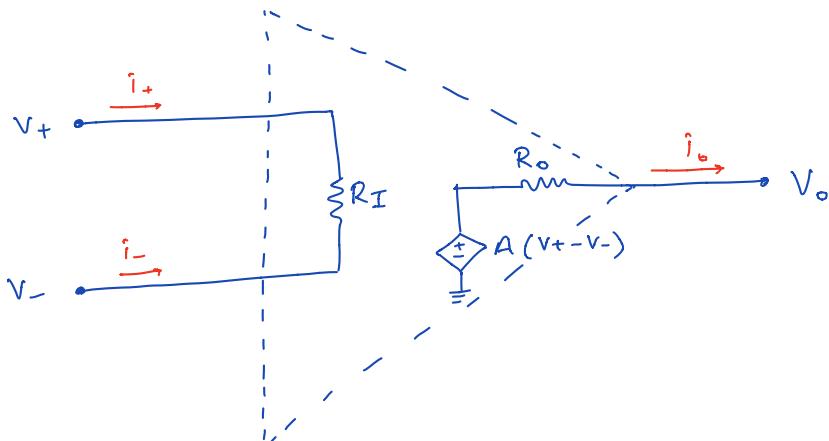

- * A : finite gain $\Rightarrow 10^5 < A < 10^8$ (very large)
- * R_I : input resistance $\Rightarrow 10^6 < R_I < 10^{12} \Omega$ (very large)
- * R_o : output resistance $\Rightarrow 10 < R_o < 100 \Omega$ (small)

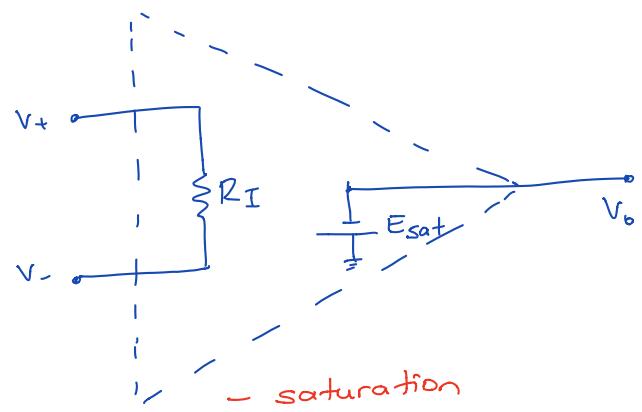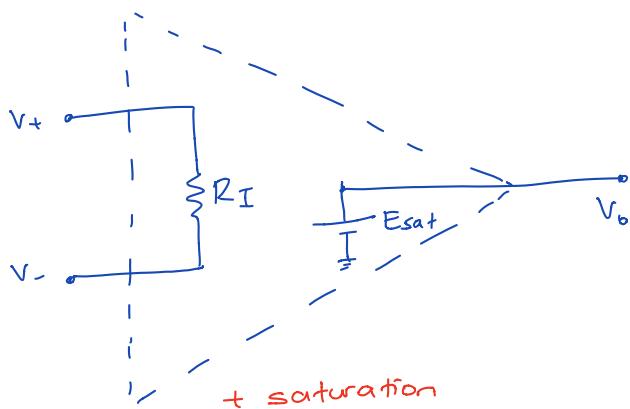* In \pm Saturation: Output behaves like a $\pm E_{sat}$ DC source.



Ideal OPAMP model : a.k.a. infinite gain model

Can be obtained from the finite gain model
by taking the limits:

$$R_I \rightarrow \infty, R_o \rightarrow 0, A \rightarrow \infty$$

Logical conclusions:

$$* R_I \rightarrow \infty \Rightarrow i_+ = i_- = 0 \quad (R_I \text{ is open circuit})$$

Then, there are 3 operating modes:

$$* + \text{ Saturation: } V_o = +V_{cc}, \text{ when } (v_+ - v_-) > \frac{V_{cc}}{A} \rightarrow 0 \\ \text{i.e., when } (v_+ - v_-) > 0$$

$$* \text{ Linear Region: } V_o = A(v_+ - v_-) \Rightarrow v_+ - v_- = \frac{V_o}{A} \rightarrow 0 \\ \boxed{v_+ - v_- = 0}$$

$$\text{when } -V_{cc} < V_o < V_{cc}$$

$$* - \text{ Saturation: } V_o = -V_{cc}, \text{ when } (v_+ - v_-) < -\frac{V_{cc}}{A} \rightarrow 0 \\ \text{i.e., when } (v_+ - v_-) < 0$$

To summarize, in ideal OPAMP model:

$$i_+ = i_- = 0 \quad (\text{in all regions})$$

$$* \text{ Linear region: } v_+ = v_-, \text{ when } -V_{cc} < V_o < V_{cc}$$

$$* + \text{ Saturation: } V_o = +V_{cc}, \text{ when } (v_+ - v_-) > 0$$

$$* - \text{ Saturation: } V_o = -V_{cc}, \text{ when } (v_+ - v_-) < 0$$



* In most applications, OPAMP is used in the linear region.

* We will use $\pm E_{sat}$ for saturation voltage instead of V_{cc} .


Typically $E_{sat} < V_{cc}$ (slightly).

Example : OPAMP in saturation mode : Comparator

(13)

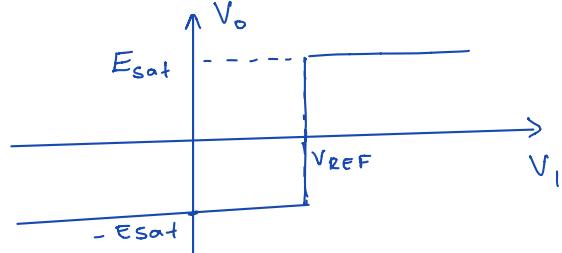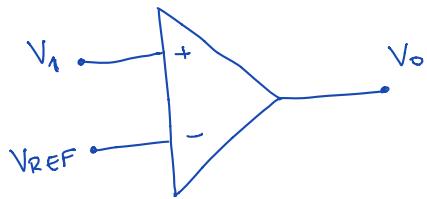


Example :

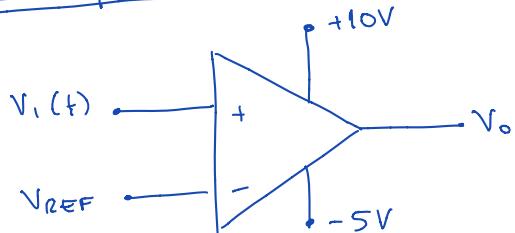


$$V_i(+) = 5 \cdot \sin(2\pi f t) \text{ V}$$

$$V_{REF} = 2 \text{ V}$$

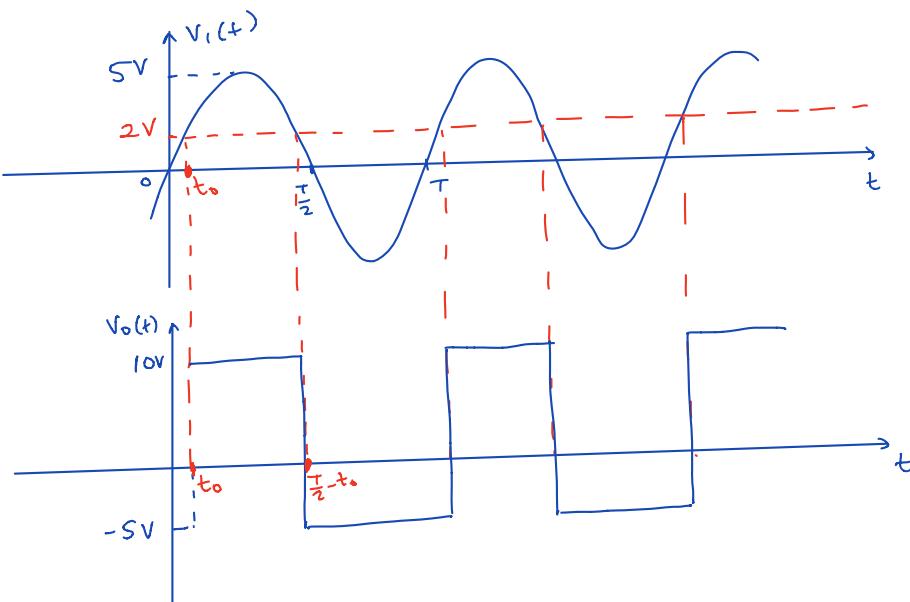

$$\begin{aligned} 5 \sin(2\pi f t_0) &= 2 \\ 2\pi f t_0 &= \arcsin(2/5) \\ t_0 &= \frac{1}{2\pi f} \arcsin(2/5) \end{aligned}$$

Voltage Follower: Buffer

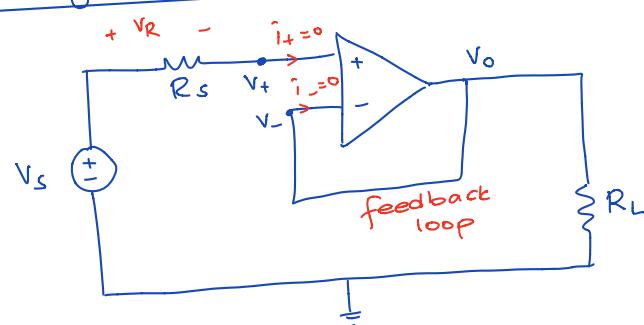

$$V_R = 0$$

$$V_+ = V_s \quad (\text{KVL})$$

$$V_- = V_o$$

In linear region: $V_+ = V_-$

$$\Rightarrow \boxed{V_o = V_s}, \text{ if } -E_{sat} < V_o < E_{sat}$$


$$\Rightarrow -E_{sat} < V_s < E_{sat}$$

to be in linear region

\Rightarrow Prevents loading the source. We use the voltage source V_s without drawing any power from it.



Application of Buffer:

Compare with :

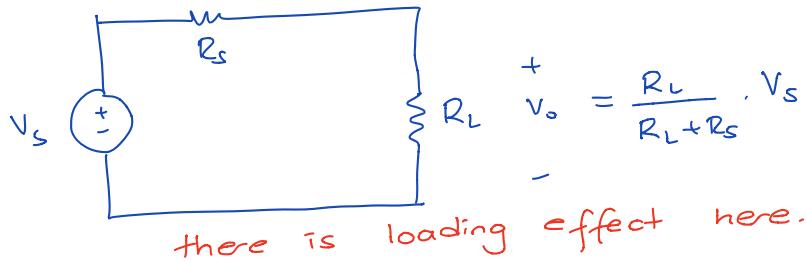

Alternative interpretation: in the linear region, independent of anything else, we can use this circuit as a VCVS with unit gain.

* We can isolate building blocks from each other by putting a buffer in between.

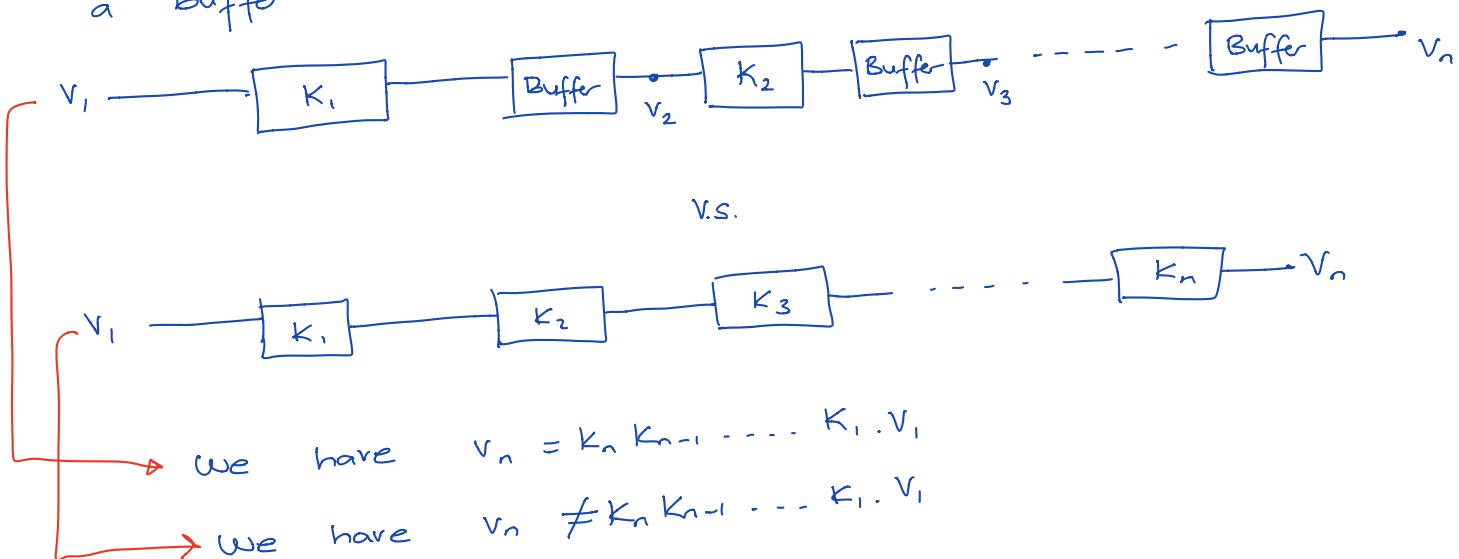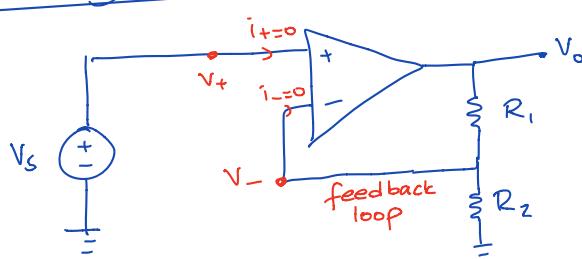Noninverting amplifier:

$$V_+ = V_S$$

$$V_- = \frac{R_2}{R_1 + R_2} \cdot V_o \quad (\text{voltage divider})$$

In linear region: $V_+ = V_-$
 $V_S = \frac{R_2}{R_1 + R_2} \cdot V_o$


$$\Rightarrow V_o = \left(\frac{R_1 + R_2}{R_2} \right) \cdot V_S$$

"closed-loop" gain

if $-E_{sat} < V_o < E_{sat}$
 $-\frac{R_2}{R_1 + R_2} \cdot E_{sat} < V_S < \frac{R_2}{R_1 + R_2} \cdot E_{sat}$

Effects of Finite OPAMP Gain (finite A) :

15

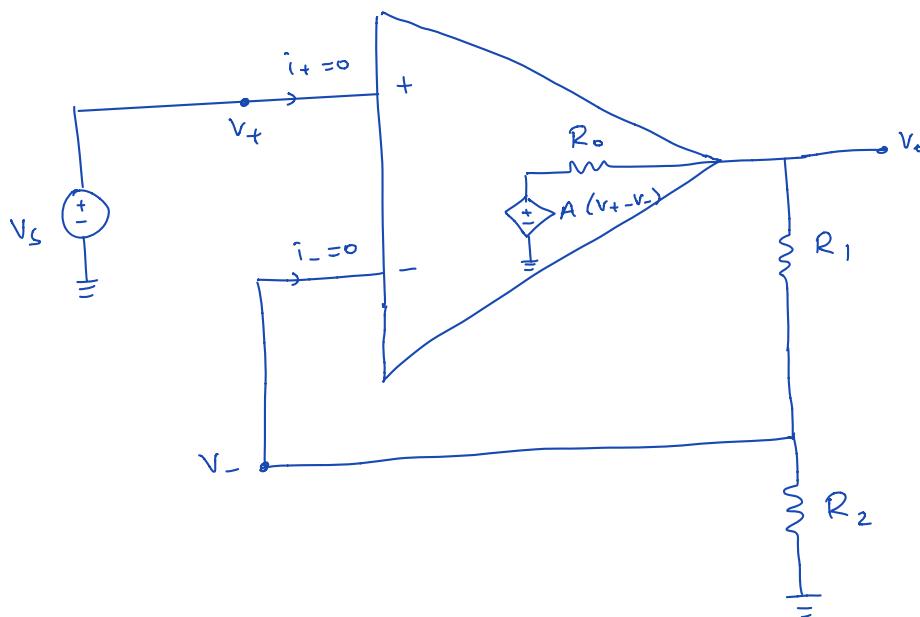

$$R_I \sim 10^6 \Omega - 10^{12} \Omega \Rightarrow \text{ignore it (OPEN CIRCUIT)}$$

Then,

$$v_+ = v_s$$

$$v_- = \frac{R_2}{R_1 + R_2} \cdot v_o$$

$$v_o = \frac{R_1 + R_2}{R_0 + R_1 + R_2} \cdot A(v_+ - v_-)$$

so,

$$v_o = \frac{R_1 + R_2}{R_0 + R_1 + R_2} \cdot A \left(v_s - \frac{R_2}{R_1 + R_2} \cdot v_o \right)$$

$$v_o = \frac{(R_1 + R_2) \cdot A}{R_0 + R_1 + R_2} v_s - \frac{R_2 \cdot A}{R_0 + R_1 + R_2} \cdot v_o$$

$$(R_0 + R_1 + R_2 + R_2 A) v_o = (R_1 + R_2) A \cdot v_s$$

$$v_o = \frac{A(R_1 + R_2)}{R_0 + R_1 + R_2(1+A)} \cdot v_s$$

* In the limit as $A \rightarrow \infty$

$$v_o = \frac{R_1 + R_2}{R_2} \cdot v_s = K \cdot v_s$$

↑ closed-loop gain

* Re-write V_o for finite gain case:

$$V_o = \frac{A \cdot \frac{R_1 + R_2}{R_2}}{\frac{R_o + R_1 + R_2}{R_2} + A} \cdot V_s \approx \frac{A \cdot \frac{R_1 + R_2}{R_2}}{\frac{R_1 + R_2}{R_2} + A} \cdot V_s$$

$$V_o = \frac{A \cdot K}{K + A} \cdot V_s$$

$$\boxed{V_o = \frac{K}{1 + K/A} \cdot V_s}$$

(assuming R_o is sufficiently small)

- * One practical rule of thumb is to limit K (closed-loop gain) to less than 1% of the OPAMP open loop gain (A).

i.e., $K < \frac{A}{100}$.


- * Despite large variations in A , closed-loop gain remains constant as long as $K \ll A$. \Rightarrow importance of feedback loop !!

Applications:

1) An amplifier with gain $\frac{R_1 + R_2}{R_2}$

2) A VCVS with $\mu = \frac{R_1 + R_2}{R_2} > 1$


3) Realization of a negative resistance.

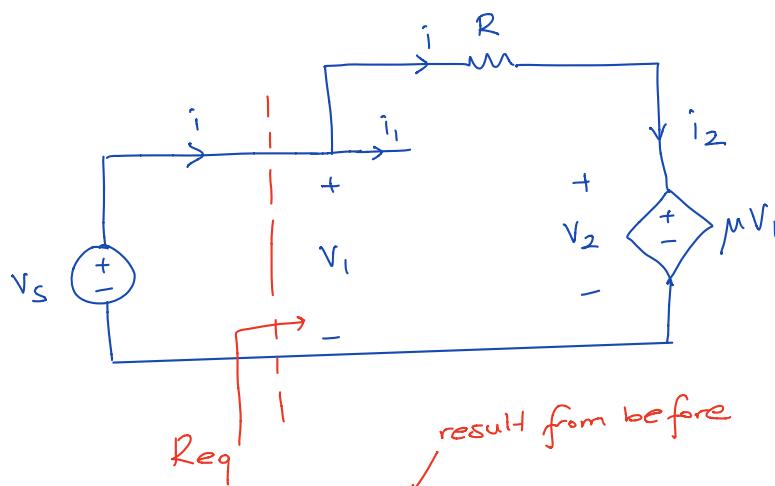

$$Req = \frac{R}{1-\mu}, \text{ for non-inverting}$$

$$Req = -\frac{R \cdot R_2}{R_1} < 0$$

* used in oscillators and active filters

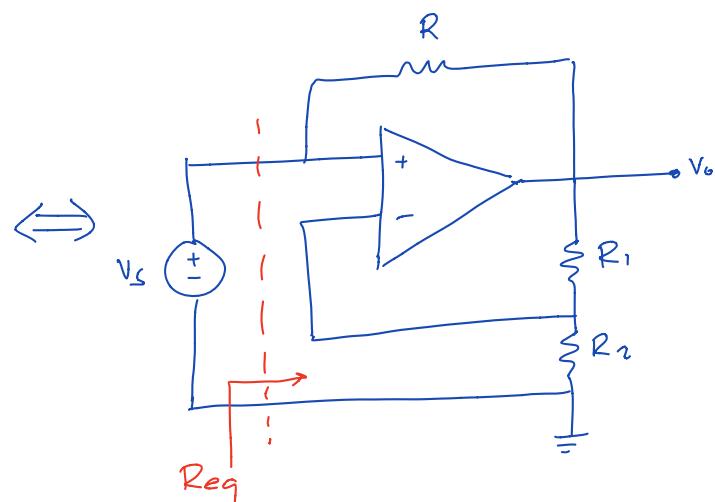


OPAMP part, $\mu = \frac{R_1 + R_2}{R_2}$

$$\Rightarrow 1-\mu = -\frac{R_1}{R_2}$$

About the negative feedback loop:

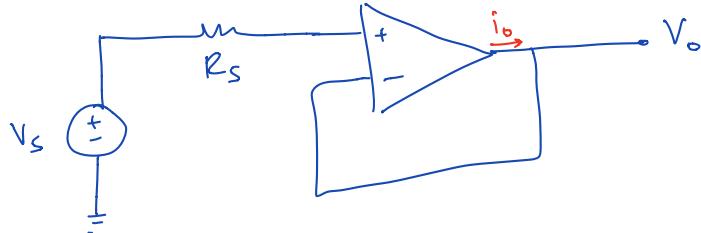- * For stability, feedback loop should enter the negative input of the OPAMP



$$\downarrow V_o = A(V_+ - V_-)$$

✓ stable

non-inverting input


inverting input

- * If we use positive feedback : $\uparrow V_o = A(V_+ - V_-)$ X not wanted

Using Node Equations for OP-AMP Circuits

- *** write node equations at all non-reference nodes except for the OPAMP output node.
(Note that $i_o \neq 0$ in general)
- * By using OPAMP equations, solve the node equations.

Example :

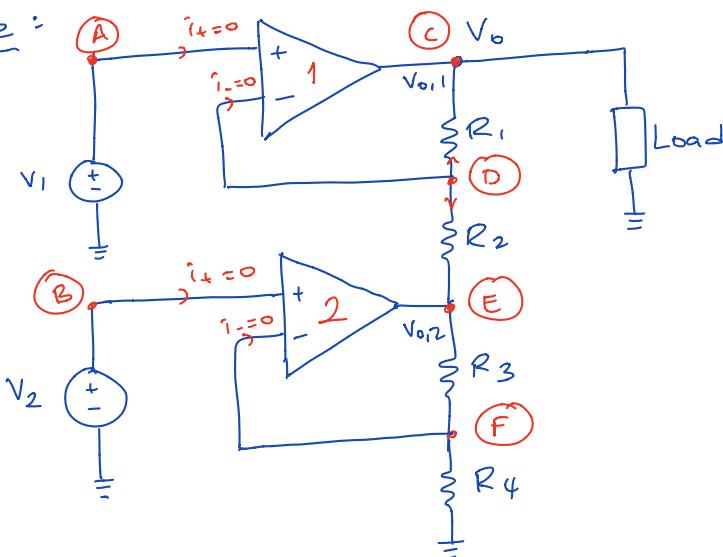

$$V_A = V_1, \quad V_B = V_2$$

Do not write node equations at nodes C and E.

KCL at D : $\frac{V_D - V_o}{R_1} + \frac{V_D - V_E}{R_2} = 0$

$$(R_1 + R_2)V_D - R_2V_o - R_1V_E = 0$$

Assuming OPAMP 1 is in linear region : $V_A = V_D = V_1$

$$(R_1 + R_2)V_1 - R_2V_o - R_1V_E = 0$$

KCL at F: $V_F = \frac{R_4}{R_3+R_4} V_E$

Assuming OPAMP 2 is in linear region: $V_B = V_F = V_2$

$$V_2 = \frac{R_4}{R_3+R_4} V_E \Rightarrow V_E = \frac{R_3+R_4}{R_4} V_2 = V_{o,2}$$

* Insert into first equation:

$$(R_1 + R_2)V_1 - R_2V_o - R_1 \cdot \frac{(R_3+R_4)}{R_4} \cdot V_2 = 0$$

$$\boxed{V_o = \frac{R_1+R_2}{R_2} \cdot V_1 - \frac{R_1 \cdot (R_3+R_4)}{R_2 \cdot R_4} \cdot V_2}$$

if both OPAMPS
are in linear
region.

* if we choose $R_1 = R_4 = R_A$
 $R_2 = R_3 = R_B$

Then,

$$\boxed{V_o = \frac{R_A+R_B}{R_B} (V_1 - V_2)}$$

This relation is valid when:

$$-E_{sat} < V_{o,1} < E_{sat}, \quad -E_{sat} < V_{o,2} < E_{sat}$$

$$-\frac{R_B}{R_A+R_B} \cdot E_{sat} < V_1 - V_2 < \frac{R_B}{R_A+R_B} \cdot E_{sat}, \text{ for OPAMP 1 to be in linear region}$$

$$-\frac{R_A}{R_A+R_B} \cdot E_{sat} < V_2 < \frac{R_A}{R_A+R_B} \cdot E_{sat}, \text{ for OPAMP 2 to be in linear region}$$

* Let's say $E_{sat} = 10V$ } for both OPAMPS
 $-E_{sat} = -10V$

$$R_1 = R_4 = R_A = 1k\Omega$$

$$R_2 = R_3 = R_B = 2k\Omega$$

In linear region: $V_E = V_{o,2} = \frac{R_A+R_B}{R_A} \cdot V_2 = 3V_2$

$$V_o = V_{o,1} = \frac{R_A+R_B}{R_B} (V_1 - V_2) = \frac{3}{2} (V_1 - V_2)$$

Case 1 : if $v_1 = 2V$, $v_2 = 3V$

$$V_E = V_{o,2} = 9V \quad \checkmark \text{ in linear region}$$

$$V_o = V_{o,1} = \frac{3}{2} (v_1 - v_2) = -\frac{3}{2} V \quad \checkmark \text{ in linear region}$$

Case 2 : if $v_1 = 2V$, $v_2 = 4V$

$$V_E = V_{o,2} = 12V \quad \times \text{ cannot happen!}$$

OPAMP 2 is saturated

$$\boxed{V_E = V_{o,2} = 10V}$$

Then, $V_o = V_{o,1} = \frac{3}{2} (v_1 - v_2)$ is no longer valid !!

Side note : $V_{+,2} = V_2 = 4V$

$$V_{-,2} = V_F = \frac{R_4}{R_3 + R_4} \cdot V_E = \frac{1}{3} \cdot 10 \approx 3.33V \quad \left. \begin{array}{l} V_{+,2} > V_{-,2} \\ \text{+ saturation} \end{array} \right\}$$

Re-write KCL at D : Assuming that OPAMP 1 is not saturated : $V_o = V_A = V_1$

$$\frac{V_1 - V_o}{R_1} + \frac{V_1 - V_E}{R_2} = 0$$


$$R_2 V_o = (R_1 + R_2) V_1 - R_1 V_E$$

$$V_o = \left(\frac{R_1 + R_2}{R_2} \right) V_1 - \frac{R_1}{R_2} V_E$$

$$= \frac{3}{2} V_1 - \frac{1}{2} V_E$$

$$= 3 - 5 = \boxed{-2V}$$

\checkmark in linear region

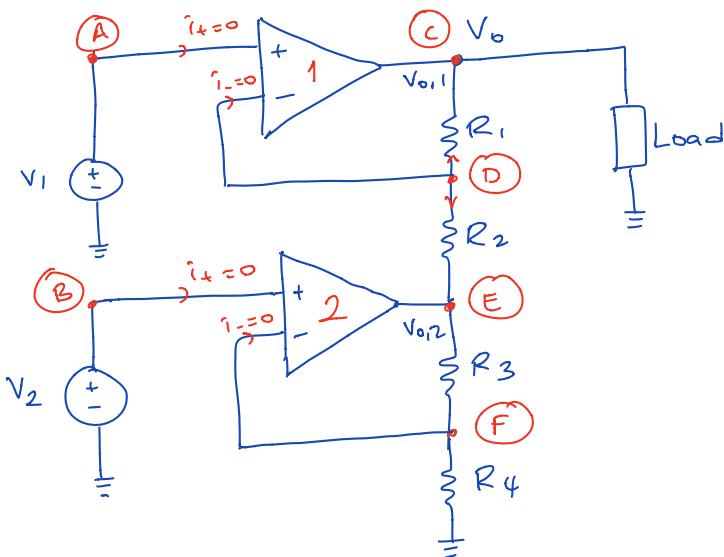

* In general :

- Assume a region of operation for each OPAMP.

- Solve the circuit.

- Check the validating inequalities for the solution obtained.

If they are satisfied, the solution is correct.
Otherwise, choose another operating region for the OPAMP(s) and solve the circuit again.