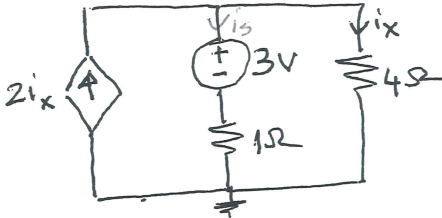


EEE 202 CIRCUIT THEORY
First Midterm, Spring 2013-14

No credits will be given for unjustified answers. Good luck.


Prob. 1 : (24 pt.s)

i : Find the current i_x in the following circuit.



$$i_s = i_x \Rightarrow 3 + i_x = 4i_x \Rightarrow 3i_x = 3 \Rightarrow i_x = 1A$$

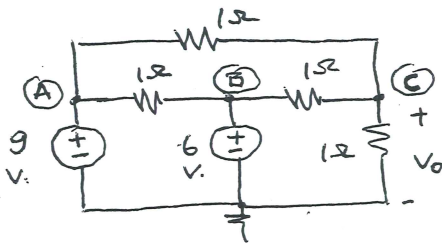ii : Find the voltage v_0 in the following circuit.




node at
C

$$\frac{v_C - v_A}{1} + \frac{v_C - v_B}{1} + \frac{v_C}{1} = 0$$

$$\Rightarrow -9 - 6 + 3v_C = 0 \Rightarrow 3v_C = 15$$

$$\Rightarrow v_C = v_0 = 5V$$

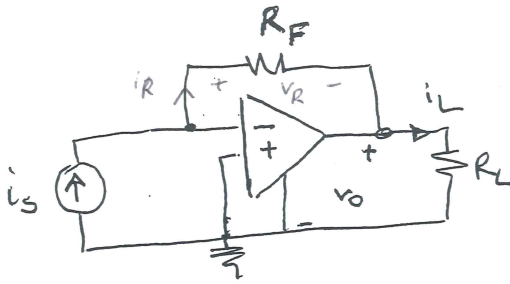iii : Consider the following circuit. Assume that the op-amp is ideal and operates in the linear region. Find i_L .





$$i_R = i_s \quad (02)$$


$$v_R = -v_o = R_F i_R = R_F i_s \Rightarrow v_o = -R_F i_s \quad (02)$$

$$i_L = \frac{v_o}{R_L} = -\frac{R_F}{R_L} i_s \quad (02)$$

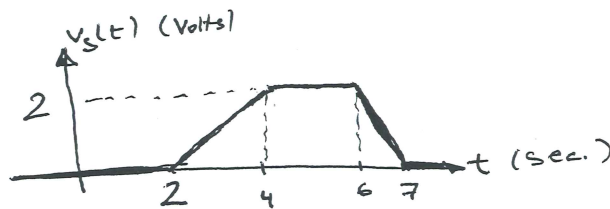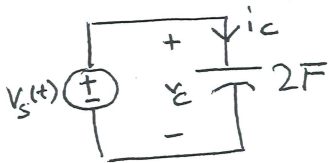iv : Consider the following circuit. Let the voltage waveform of $v_s(t)$ is as given below. Assume that $v_C(0) = 0$ V. Find and plot $i_C(t)$.




$$v_C = v_s \Rightarrow i_C = C \frac{dv_C}{dt} \quad (02)$$

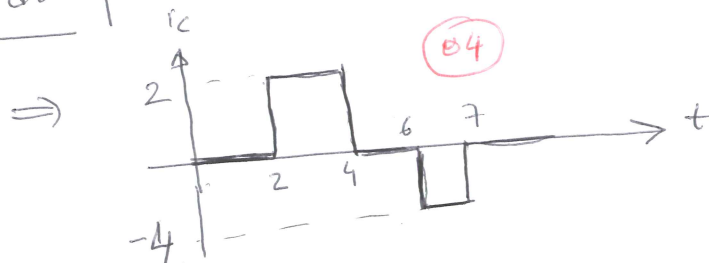

Prob. 2 : (26 pt.s)

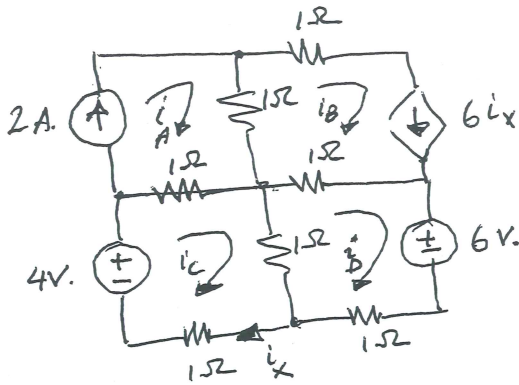i : Consider the following circuit. Find the mesh currents i_A, i_B, i_C, i_D .



$$\begin{aligned} \text{mesh A} &\Rightarrow i_A = 2 \quad (01) \\ \text{mesh B} &\Rightarrow i_B = 6i_x = 6i_C \quad (02) \\ \text{mesh C} &\Rightarrow -i_A - i_B + 3i_C = 4 \\ \text{mesh D} &\Rightarrow -i_B - i_C + 3i_D = -6 \end{aligned}$$

$$\Rightarrow \begin{cases} 3i_C - i_D = 6 \\ -7i_C + 3i_D = -6 \end{cases} \quad (04) \quad (02)$$


$$\Rightarrow 2i_C = 12 \Rightarrow i_C = 6 \text{ A}$$

$$\Rightarrow i_D = 12 \text{ A} \quad (02)$$

$$\Rightarrow i_B = 36 \text{ A} \quad (03)$$

$$i_A = 2 \text{ A}$$

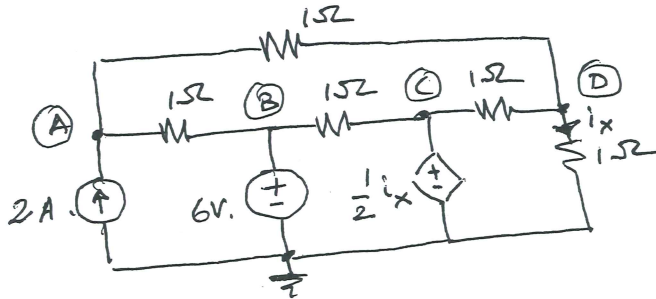ii : Consider the following circuit. Find the node voltages v_A, v_B, v_C, v_D .



$$\begin{aligned} \text{node B} &\Rightarrow v_B = 6 \quad (01) \\ \text{node C} &\Rightarrow v_C = \frac{1}{2} i_x = \frac{1}{2} v_D \quad (02) \end{aligned}$$

$$\text{A} \Rightarrow -v_B + 2v_A - v_D = 2 \rightarrow$$

$$\text{D} \Rightarrow -v_C - v_A + 3v_D = 0 \rightarrow$$

$$\Rightarrow \begin{cases} 2v_A - v_D = 8 \\ -v_A + \frac{5}{2}v_D = 0 \end{cases} \quad (04)$$

$$4v_D = 8 \Rightarrow v_D = 2 \quad (02)$$


$$v_A = 5 \quad (02)$$

$$v_C = \frac{1}{2}v_D = 1 \text{ V} \quad (02)$$


$$v_B = 6 \text{ V}$$

Prob. 3 : (25 pt.s)

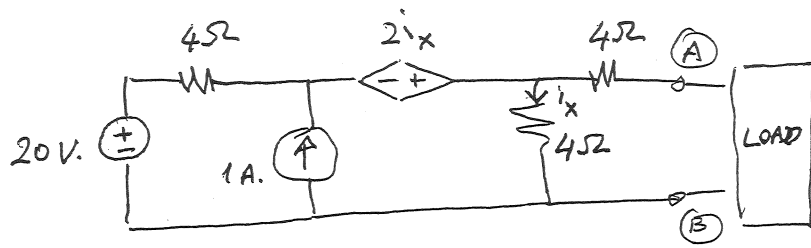i : Consider the following circuit. Find the Thévenin equivalent circuit seen by the load.



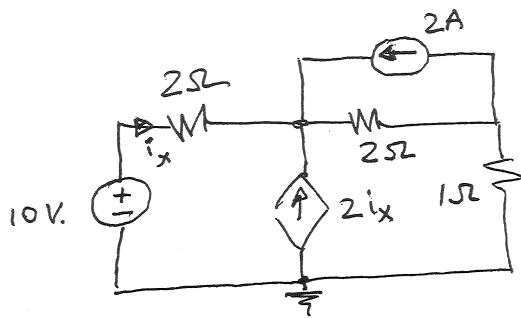ii : Consider the following circuit. By using **superposition**, find the current i_x .



Prob. 4 : (25 pt.s) Consider the following circuit. Assume that the op-amp is ideal and operates in the linear region. Find the equivalent resistance R_{eq} seen by the voltage source, i.e. $R_{eq} = v_s/i$. Can we use this circuit as a negative resistance? If yes, find the condition for which the circuit acts as a negative resistance.

