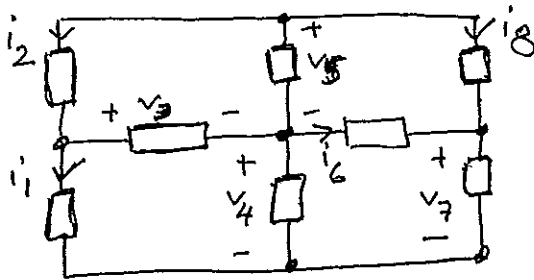


EEE 202 CIRCUIT THEORY  
First Midterm, Spring 2012-13

No credits will be given for unjustified answers.

Prob. 1 : (20 pt.s)

For part i and ii, consider the circuit shown in the following figure. Here, boxes represent arbitrary circuit elements. Some voltage and current reference directions are shown in the figure. For other voltage/current reference directions, use passivity sign convention.



i : (4 pt.s) Consider the circuit given above. We have  $i_1 = 4 \text{ A}$ ,  $i_2 = 5 \text{ A}$ ,  $i_6 = 3 \text{ A}$ ,  $i_8 = 2 \text{ A}$ . Find as many remaining currents as you can.

$$-i_2 + i_1 + i_3 = 0 \Rightarrow i_3 = i_2 - i_1$$

$$i_3 = 1 \text{ A. (01)}$$

$$-i_1 - i_4 - i_7 = 0 \Rightarrow i_4 = -i_1 - i_7$$

$$i_4 = -9 \text{ A. (01)}$$

$$-i_6 - i_8 + i_7 = 0 \Rightarrow i_7 = i_6 + i_8$$

$$i_7 = 5 \text{ A. (01)}$$

$$-i_3 - i_5 + i_4 + i_6 = 0 \Rightarrow i_5 = -i_3 + i_4 + i_6$$

$$i_5 = -7 \text{ A. (01)}$$

ii : (4 pt.s) Consider the circuit given above. We have  $v_3 = 5 \text{ V}$ ,  $v_4 = 4 \text{ V}$ ,  $v_5 = 3 \text{ V}$ ,  $v_7 = 2 \text{ V}$ . Find as many remaining voltages as you can.

$$-v_1 + v_3 + v_4 = 0 \Rightarrow v_1 = v_3 + v_4$$

$$v_1 = 9 \text{ V. (01)}$$

$$v_6 + v_7 - v_4 = 0 \Rightarrow v_6 = v_4 - v_7$$

$$v_6 = 2 \text{ V. (01)}$$

$$v_5 - v_3 - v_2 = 0 \Rightarrow v_2 = v_5 - v_3$$

$$v_2 = -2 \text{ V. (01)}$$

$$v_8 - v_6 - v_5 = 0 \Rightarrow v_8 = v_5 + v_6$$

$$v_8 = 5 \text{ V. (01)}$$

$$\begin{aligned} V_A &= V_0 \\ -V_A + 2V_B + V_C &= 0 \quad (Q2) \\ -V_A - V_B + 3V_C &= I_0 \end{aligned}$$

$$\begin{cases} 2i_A - i_B - i_C = V_1 \\ -i_A + i_B + i_C = 0 \\ -i_A - i_B + 3i_C = -V_2 \end{cases} \quad (02)$$

Prob. 2 : (25 pt.s)

i : (12 pt.s) Consider the circuit shown in Figure 1. Let  $v_A, v_B, v_C$  represent the node voltages of nodes A, B, C. Use node analysis and find the voltages  $v_o$  and  $v_x$ .

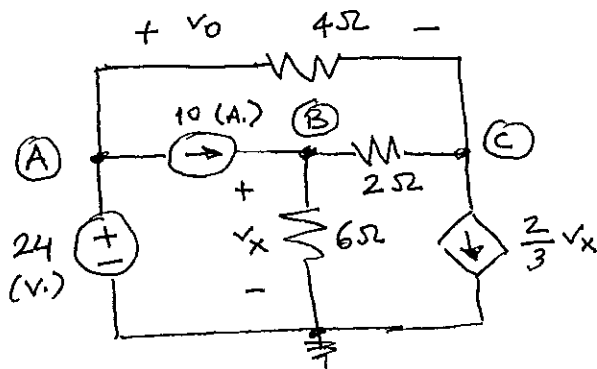


Fig.1

$$\begin{aligned}
 v_A &= 24 \\
 \left( \frac{1}{6} + \frac{1}{2} \right) v_B - \frac{1}{2} v_C &= 10 \quad (0.4) \\
 -\frac{1}{4} v_A - \frac{1}{2} v_B + \left( \frac{1}{2} + \frac{1}{4} \right) v_C &= -\frac{2}{3} v_x \\
 v_x &= v_B
 \end{aligned}$$

$$\begin{aligned}
 \frac{2}{3} v_B - \frac{1}{2} v_C &= 10 \\
 \left( \frac{2}{3} - \frac{1}{2} \right) v_B + \frac{3}{4} v_C &= 6
 \end{aligned}$$

$$\begin{aligned}
 \frac{2}{3} v_B - \frac{1}{2} v_C &= 10 \\
 \frac{1}{6} v_B + \frac{3}{4} v_C &= 6
 \end{aligned} \quad (0.4)$$

$$\begin{aligned}
 v_C &= 4V \\
 v_B &= 18V
 \end{aligned}$$

$$v_x = v_B = 18V \quad (0.2)$$

$$\begin{aligned}
 v_o &= v_A - v_C \\
 v_o &= 20V \quad (0.2)
 \end{aligned}$$

ii : (13 pt.s) Consider the circuit shown in Figure 2. Let  $i_A, i_B, i_C$  represent the mesh currents as indicated in the Figure 2. Use mesh analysis and find  $v_x$  and  $v_o$ .

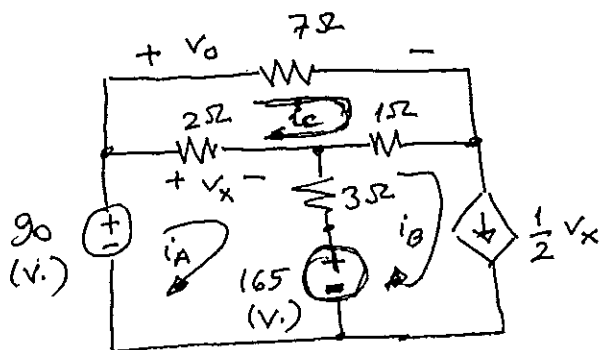


Fig.2

$$\begin{aligned}
 5i_A - 3i_B - 2i_C &= -75 \\
 i_B &= \frac{1}{2} v_x \quad (0.3) \\
 -2i_A - i_B + 10i_C &= 0 \\
 v_x &= 2(i_A - i_C)
 \end{aligned}$$

$$\begin{aligned}
 5i_A - 3i_B - 2i_C &= -75 \\
 i_B &= i_A - i_C \\
 -2i_A - i_B + 10i_C &= 0
 \end{aligned}$$

$$\begin{aligned}
 2i_A + i_C &= -75 \\
 -3i_A + 11i_C &= 0
 \end{aligned} \quad (0.4)$$




$$\begin{aligned}
 i_C &= -9A \quad (0.1) \\
 i_A &= -33A \quad (0.1)
 \end{aligned}$$

$$\begin{aligned}
 v_x &= 2(i_A - i_C) \\
 v_x &= 48V \quad (0.2)
 \end{aligned}$$

$$\begin{aligned}
 v_o &= 7i_C \\
 v_o &= -63V \quad (0.2)
 \end{aligned}$$

Prob. 3 : (30 pt.s)


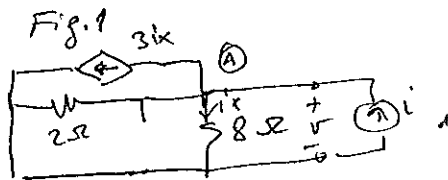
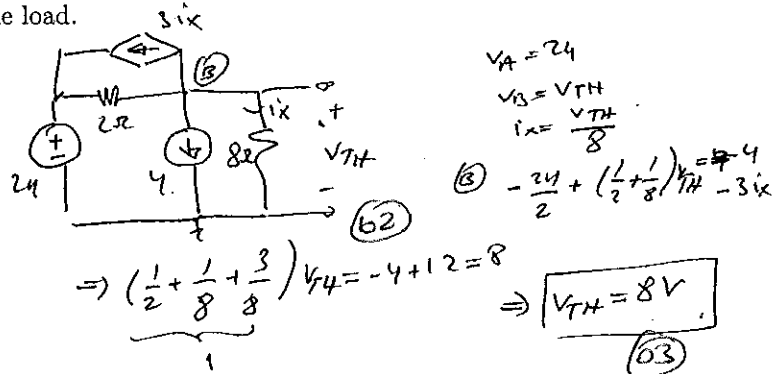
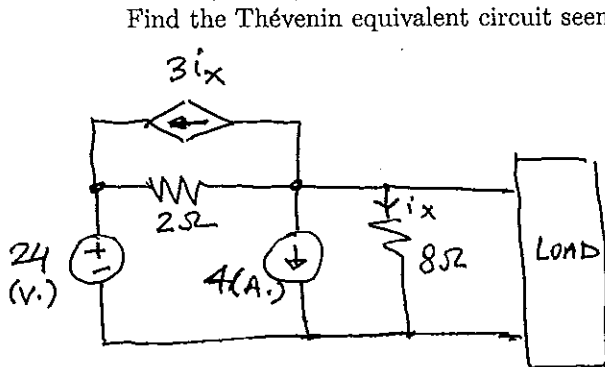
i : (10 pt.s) Consider the circuit shown in Figure 1. Here the load represents an arbitrary circuit. Find the Thévenin equivalent circuit seen by the load.





$v_A = 0 \Rightarrow \left(\frac{1}{8} + \frac{1}{2}\right)v = i - 3i_x \quad i_x = \frac{v}{8}$   
 $\Rightarrow \left(\frac{1}{8} + \frac{1}{2} + \frac{3}{8}\right)v = i \Rightarrow R_T = \frac{v}{i} = 1\Omega$



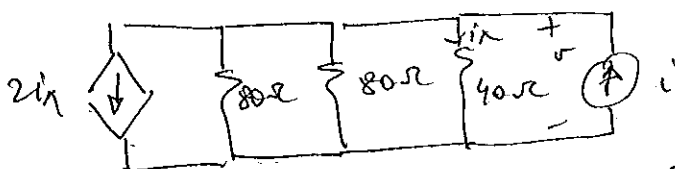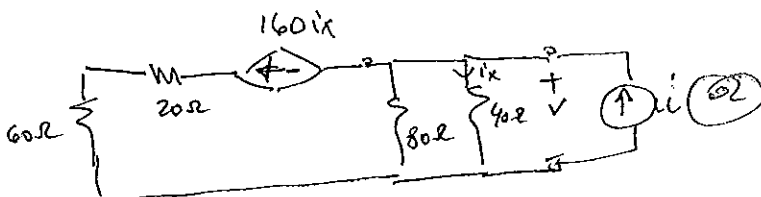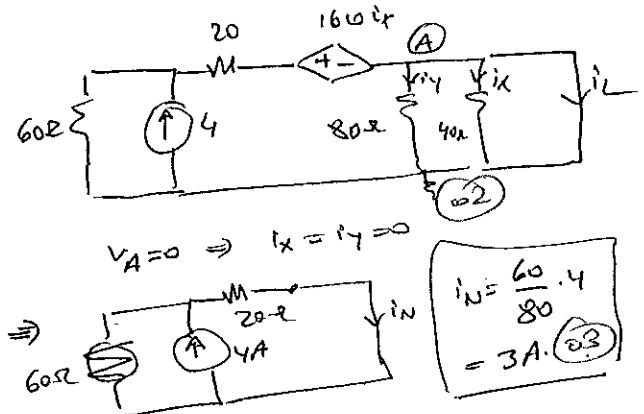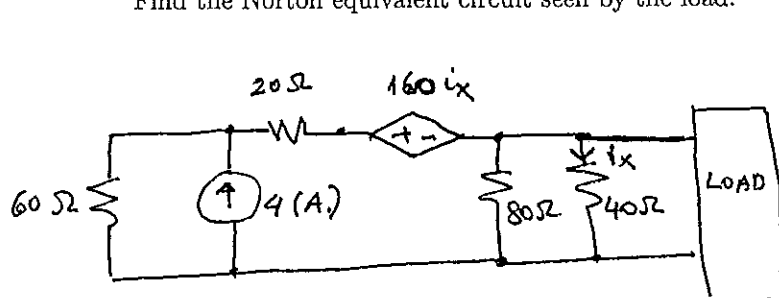ii : (10 pt.s) Consider the circuit shown in Figure 2. Here the load represents an arbitrary circuit. Find the Norton equivalent circuit seen by the load.



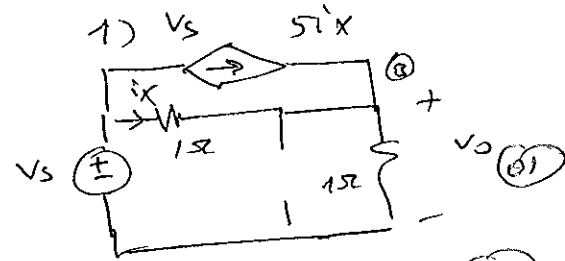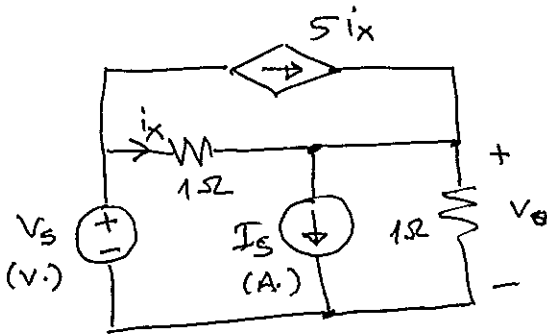
iii : (10 pt.s) Consider the circuit shown below. By using superposition, find  $v_o$ .



$$i_x = \frac{V_s - v_o}{1} = V_s - v_o \quad (01)$$

Node at (B)  $\rightarrow -\frac{V_s}{1} + 2v_o = 5i_x = 5(V_s - v_o) \quad (02)$
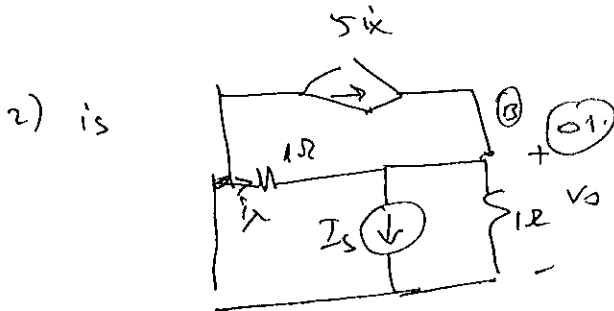
$$\rightarrow 7v_o = 6V_s \rightarrow \boxed{v_o = \frac{6}{7} V_s} \quad (02)$$



$$i_x = -v_o \quad (01)$$

(B)  $\rightarrow 2v_o = 5i_x - I_s = -5v_o - I_s$


$$7v_o = -I_s \rightarrow \boxed{v_o = -\frac{1}{7} I_s} \quad (02)$$

$$\boxed{v_o = \frac{6}{7} V_s - \frac{1}{7} I_s} \quad (02)$$

Prob. 4 : (25 pt.s) Consider the following circuit. Here the op-amps are linear and operate in their linear regions; the load represents an arbitrary circuit. Note that in case you use node analysis, use the notation indicated in the Figure.

i : Find  $v_o$  in terms of  $v_1$ ,  $v_2$  and the resistances.

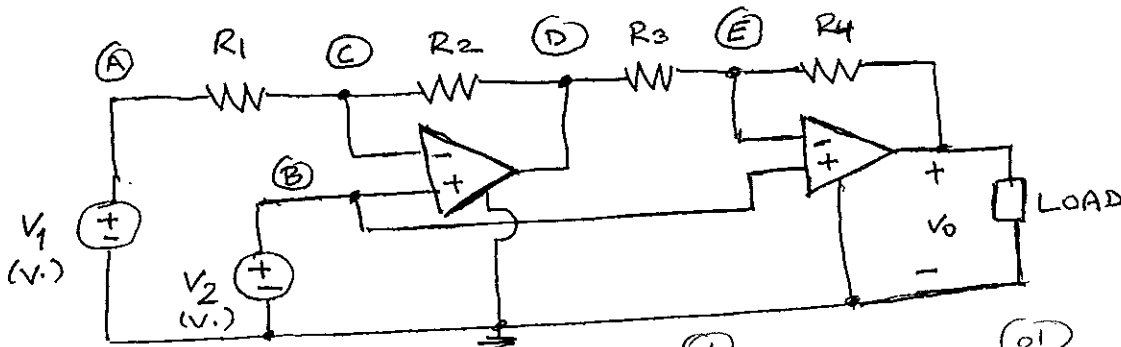ii : Assume that the saturation voltage  $E_{sat}$  is  $E_{sat} = 15\text{ V}$  for both op-amps. Let  $R_1 = R_2 = R_3 = R_4 = 1\ \Omega$  and  $v_2 = 1\text{ V}$ . Find the range of  $v_1$  so that both op-amps operate in the linear region.



i)

$$\boxed{V_A = v_1} \quad \boxed{V_B = v_2} \quad \boxed{V_C = V_B = v_2} \quad \boxed{V_E = v_2}$$

C

$$-\frac{1}{R_1} V_A + \left(\frac{1}{R_1} + \frac{1}{R_2}\right) V_C - \frac{1}{R_2} V_D = 0 \Rightarrow \boxed{V_D = \left(1 + \frac{R_2}{R_1}\right) v_2 - \frac{R_2}{R_1} v_1}$$

E

$$-\frac{1}{R_3} V_D + \left(\frac{1}{R_3} + \frac{1}{R_4}\right) V_E - \frac{1}{R_4} V_o = 0 \Rightarrow \boxed{V_o = \left(1 + \frac{R_4}{R_3}\right) v_2 - \frac{R_4}{R_3} V_D}$$

$$V_o = \left(1 + \frac{R_4}{R_3}\right) v_2 - \frac{R_4}{R_3} \left(1 + \frac{R_2}{R_1}\right) v_2 + \frac{R_4}{R_3} \cdot \frac{R_2}{R_1} v_1 = \left[1 - \frac{R_4 R_2}{R_3 R_1}\right] v_2 + \frac{R_4 R_2}{R_3 R_1} v_1$$

$$\Rightarrow \boxed{V_o = \frac{R_1 R_3 - R_4 R_2}{R_3 R_1} v_2 + \frac{R_4 R_2}{R_3 R_1} v_1}$$

ii)

$$v_o = 2v_2 - v_1 = 2 - v_1 \Rightarrow -15 < 2 - v_1 < 15 \Rightarrow \boxed{-13 < v_1 < 17}$$

$$v_o = v_1 \Rightarrow \boxed{-15 < v_1 < 15}$$

$$\boxed{-13 < v_1 < 15}$$