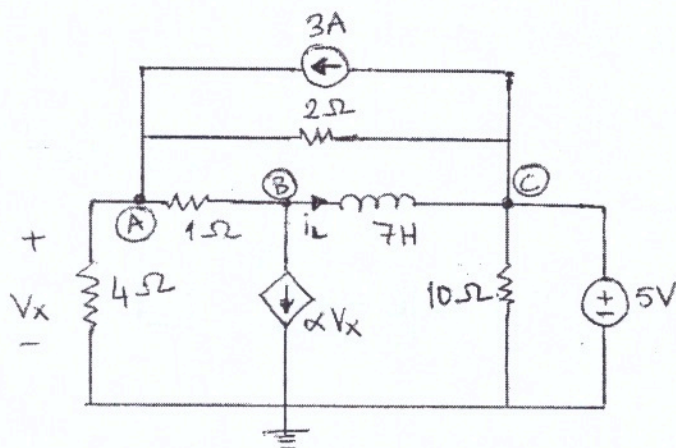


FALL 2016-2017
— MIDTERM #2 SOLUTIONS —

Question 1. [25 points]

Consider the following circuit. Let $i_L(0) = 3A$.

- Find the value of α so that the time constant τ of the circuit is $\tau = 3 \text{ sec}$. (If this is not possible, explain why.)
- Let $\alpha = 0.5$. Find $i_L(t)$.
- Again for $\alpha = 0.5$, find $v_x(t)$.



- a) Find resistance seen by the inductor. Kill all independent sources.

$$V_C = 0, \quad V_x = V_A$$

$$V = V_B - V_C = V_B$$

$$\text{KCL at node A: } \frac{V_A}{4} + \frac{V_A - V_B}{1} + \frac{V_A}{2} = 0$$

$$7V_A = 4V_B \Rightarrow V_A = \frac{4}{7}V_B$$

$$\text{KCL at node B: } \alpha V_x + \frac{V_B - V_A}{1} - i = 0$$

$$\alpha \cdot \frac{4}{7}V_B + V_B - \frac{4}{7}V_B = i$$

$$(3 + 4\alpha)V_B = 7i$$


$$R_{eq} = \frac{V}{i} = \frac{V_B}{i} = \frac{7}{3 + 4\alpha}$$

$$\text{* For } \tau = \frac{L}{R_{eq}} = \frac{7}{R_{eq}} = 3 \text{ s} \Rightarrow R_{eq} = \frac{7}{3} \Omega = \frac{7}{3 + 4\alpha} \Rightarrow \boxed{\alpha = 0}$$

$$\text{b) if } \alpha = 0.5 \Rightarrow R_{eq} = \frac{7}{3 + 2} = \frac{7}{5} \Omega \Rightarrow \tau = \frac{L}{R} = \frac{7}{7/5} = \boxed{5 \text{ sec}}$$

* Find Norton current \Rightarrow set inductor to short circuit.

$$V_B = V_C = 5V, \quad V_x = V_A$$

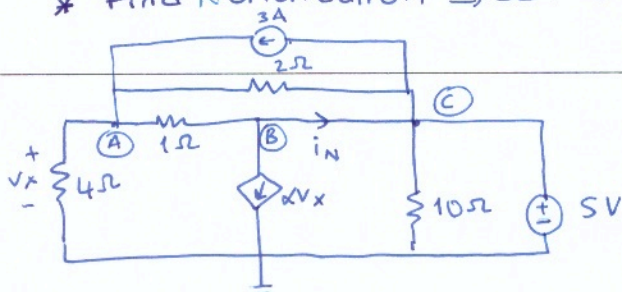

$$\text{KCL at A: } \frac{V_A}{4} + \frac{V_A - 5}{1} + \frac{V_A - 5}{2} - 3 = 0$$

$$7V_A - 20 - 10 - 12 = 0$$

$$7V_A = 42$$


$$\boxed{V_A = 6V}$$

KCL at B: $i_N + 0.5V_x + \frac{V_B - V_A}{1} = 0$

$i_N + 0.5 \times 6 + 5 - 6 = 0$

$\Rightarrow \boxed{i_N = -2A}$

So, the circuit is simplified to:

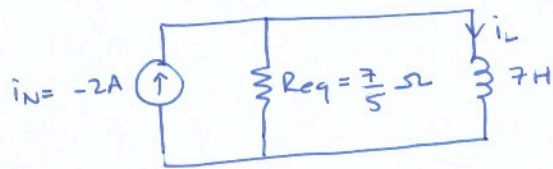

$$i_L(t) = i(\infty) + [i(0) - i(\infty)]e^{-t/\tau}$$

$$= -2 + (3 - (-2))e^{-t/5} \text{ A}$$

$$\boxed{i_L(t) = -2 + 5e^{-t/5} \text{ A}}$$

c) use KCL at B: $i_L + 0.5V_x + \frac{V_B - V_A}{1} = 0$

$V_x = 2(i_L + V_B)$


$V_B = V_C + V_L = 5 + L \frac{di_L}{dt} = 5 + 7.5 \cdot \left(-\frac{1}{5}\right) \cdot e^{-t/5} = 5 - 7.5e^{-t/5} \text{ V}$

$V_x = 2 \left[-2 + 5e^{-t/5} + 5 - 7.5e^{-t/5} \right] = \boxed{6 - 4e^{-t/5} \text{ V}}$

Question 2. [25 points]

Consider the following circuit.

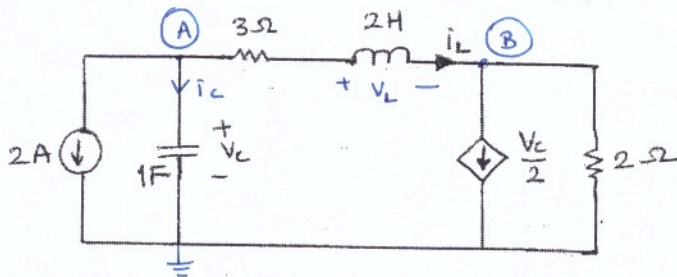- a) Find a second-order differential equation for i_L .
 b) Find $i_L(t)$ for $t > 0$, if $i_L(0) = 0$ A and $v_C(0) = 1$ V.



a) KCL at A: $2 + i_C + i_L = 0$

$$\boxed{i_C = -2 - i_L = C \dot{V}_C = \dot{V}_C} \quad (\text{Eq. 1})$$

KCL at B: $-i_L + \frac{V_C}{2} + \frac{V_B}{2} = 0$

$$-2i_L + V_C + V_B = 0$$

* Also, $V_A - V_B = 3i_L + V_L$

$V_B = V_C - 3i_L - V_L$

$-2i_L + V_C + V_C - 3i_L - V_L = 0$

$2V_C - V_L - 5i_L = 0$

$$\boxed{2V_C - 2\dot{i}_L - 5i_L = 0} \quad (\text{Eq. 2})$$

* Take derivative of Eq. 2:

$2\dot{V}_C - 2\ddot{i}_L - 5\dot{i}_L = 0$

use Eq. 1

$2(-2 - i_L) - 2\ddot{i}_L - 5\dot{i}_L = 0$

$$\boxed{2\ddot{i}_L + 5\dot{i}_L + 2i_L = -4}$$

b) * First, find the natural response: $2\ddot{i}_L + 5\dot{i}_L + 2i_L = 0$

Characteristic polynomial: $2s^2 + 5s + 2 = 0$

$(2s+1)(s+2) = 0$

$$\boxed{s_1 = -\frac{1}{2}, s_2 = -2}$$

So,
$$\boxed{i_{L,N}(t) = K_1 e^{-\frac{1}{2}t} + K_2 e^{-2t}}$$

* Next, find the forced response: Assume $i_{L,F} = A$ (a constant)

using $2\ddot{i}_L + 5\dot{i}_L + 2i_L = -4 \Rightarrow 2A = -4 \Rightarrow A = -2 \Rightarrow \boxed{i_{L,F} = -2A}$

* So, overall
$$\boxed{i_L(t) = -2 + K_1 e^{-\frac{1}{2}t} + K_2 e^{-2t}}$$

$i_L(0) = 0 \Rightarrow -2 + K_1 + K_2 = 0 \Rightarrow K_1 + K_2 = 2$

From Eq. 2 above, $2V_C(0) - 2\dot{i}_L(0) - 5i_L(0) = 0$

$2 - 2\dot{i}_L(0) = 0 \Rightarrow \dot{i}_L(0) = 1$

\Rightarrow

$$i_L(t) = -\frac{1}{2}K_1 e^{-\frac{1}{2}t} - 2K_2 e^{-2t}$$

$$i_L(0) = -\frac{1}{2}K_1 - 2K_2 = 1 \quad \Rightarrow \quad \begin{array}{r} K_1 + 4K_2 = -2 \\ - K_1 + K_2 = 2 \\ \hline 3K_2 = -4 \end{array}$$

$$K_2 = -\frac{4}{3}, \quad K_1 = 2 + \frac{4}{3} = \frac{10}{3}$$


so, $\boxed{i_L(t) = -2 + \frac{10}{3}e^{-\frac{1}{2}t} - \frac{4}{3}e^{-2t}} \quad \text{A} \quad \text{for } t > 0$

Question 3. [25 points]

Consider the circuit below. Assume that the OPAMP is ideal and operating in linear mode. Also assume that the circuit is in sinusoidal steady state.

a) Find the transfer function $H(j\omega) = \frac{V_o}{V_{in}}$.

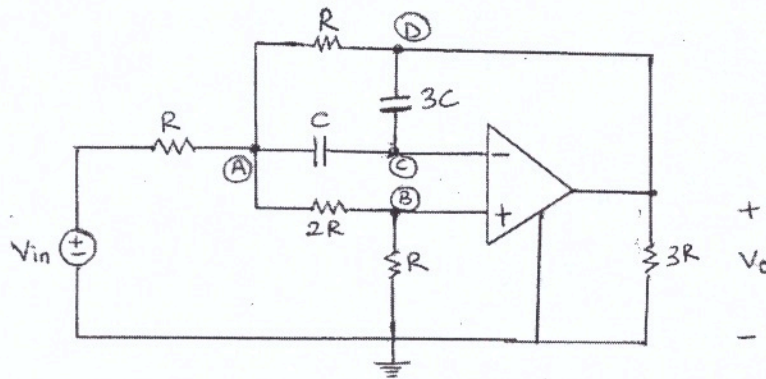b) Assume that $R = 10 \text{ k}\Omega$, $C = 100 \text{ }\mu\text{F}$, and $v_i(t) = 2 \cos(t - \frac{\pi}{6}) + 5 \cos(\frac{10}{3}t)$ V. Find $v_o(t)$.



$$a) \quad V_B = V_C = V_A \cdot \frac{R}{2R+R} = \frac{V_A}{3}, \quad V_D = V_o$$

$$\text{KCL at A: } \frac{V_A - V_{in}}{R} + \frac{V_A}{3R} + \frac{V_A - V_A/3}{\frac{1}{j\omega C}} + \frac{V_A - V_o}{R} = 0$$

(3) (3R) (3)

$$7V_A - 3V_{in} + 2j\omega RC V_A - 3V_o = 0$$

$$(7 + 2j\omega RC) V_A = 3V_{in} + 3V_o \quad \dots \text{ (Eq. 1)}$$

$$\text{KCL at C: } \frac{V_A/3 - V_A}{\frac{1}{j\omega C}} + \frac{V_A/3 - V_o}{\frac{1}{3j\omega C}} = 0$$

$$\frac{V_A}{3} - V_A + V_A - 3V_o = 0$$

$$V_A = 9V_o \quad \dots \text{ (Eq. 2)}$$

Insert Eq. 2 into Eq. 1:

$$(7 + 2j\omega RC) 9V_o = 3V_{in} + 3V_o$$

$$(60 + 18j\omega RC) V_o = 3V_{in}$$

$$\Rightarrow H(j\omega) = \frac{V_o}{V_{in}} = \frac{1}{20 + 6j\omega RC}$$

b) The input has two different frequencies. Apply superposition in time-domain.

$$* \text{ For } v_{in,1}(t) = 2 \cos(t - \frac{\pi}{6}) \Rightarrow \omega_1 = 1, \quad V_{in,1} = 2 \cdot e^{-j\pi/6}$$

$$H(j\omega_1) = \frac{1}{20 + 6j \cdot 10 \cdot 10^3 \cdot 100 \cdot 10^{-6}} = \frac{1}{20 + 6j} = \frac{1}{20.88 \cdot e^{j0.29}}$$

$$V_{out,1} = H(j\omega_1) \cdot V_{in,1} = \frac{2 \cdot e^{-j\pi/6}}{20.88 \cdot e^{j0.26}} = 0.096 \cdot e^{-j0.81}$$

$$V_{out,1}(t) = 0.096 \cdot \cos(t - 0.81) \text{ V}$$

OR,

$$V_{out,1}(t) = 0.096 \cdot \cos(t - 46.7^\circ) \text{ V}$$

* For $V_{in,2}(t) = 5 \cdot \cos\left(\frac{10}{3}t\right) \text{ V} \Rightarrow \omega_2 = \frac{10}{3} \text{ , } V_{in,2} = 5$

$$H(j\omega_2) = \frac{1}{20 + 6j \cdot \frac{10}{3} \cdot 10 \cdot 10^3 \cdot 100 \cdot 10^{-6}} = \frac{1}{20 + j20} = \frac{1}{20\sqrt{2} \cdot e^{j\pi/4}}$$

$$V_{out,2} = H(j\omega_2) \cdot V_{in,2} = \frac{5}{20\sqrt{2} \cdot e^{j\pi/4}} = \frac{e^{j\pi/4}}{4\sqrt{2}} = 0.18 \cdot e^{-j\pi/4}$$

$$V_{out,2}(t) = 0.18 \cdot \cos\left(\frac{10}{3}t - \frac{\pi}{4}\right) \text{ V}$$

OR,

$$V_{out,2}(t) = 0.18 \cdot \cos\left(\frac{10}{3}t - 45^\circ\right) \text{ V}$$



* Finally,

$$V_{out}(t) = V_{out,1}(t) + V_{out,2}(t) = 0.096 \cdot \cos(t - 0.81) + 0.18 \cdot \cos\left(\frac{10}{3}t - 45^\circ\right) \text{ V}$$

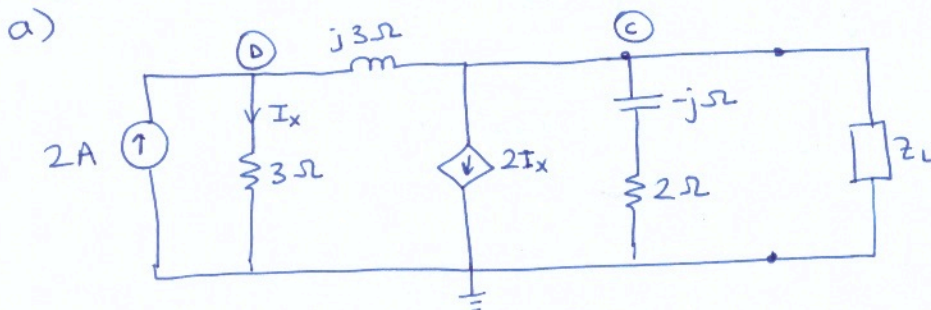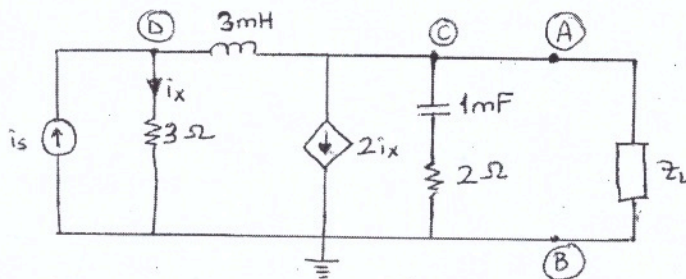Question 4. [25 points]

Assume that the circuit below is in sinusoidal steady state. Here, Z_L represents an arbitrary load, and $i_s(t) = 2 \cos(1000t)$ A.


- Draw the circuit in sinusoidal steady state by using the phasor values of $i_s(t)$ and indicating the impedance values of all circuit elements.
- Assume that Z_L is replaced by a short circuit. Find the short circuit current phasor I_N between nodes A - B and evaluate $i_N(t)$.
- Find the impedance value Z_L that maximizes the power transferred to the load. Find the average power dissipated in the load for that Z_L .



$$\omega = 1000 \text{ rps}$$

$$j\omega L = j10^3 \cdot 3 \cdot 10^{-3} = j3 \Omega$$
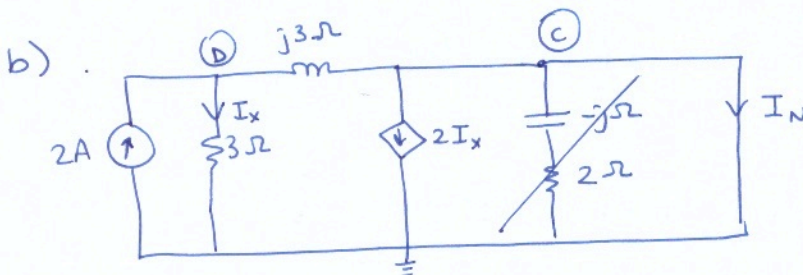
$$\frac{1}{j\omega C} = \frac{1}{j10^3 \cdot 10^{-3}} = -j \Omega$$



$$V_C = 0$$

$$I_x = \frac{V_D}{3}$$

KCL at node D: $\frac{V_D}{3} + \frac{V_D}{j3} - 2 = 0$

$$\frac{V_D}{3} + \frac{V_D}{j3} - 2 = 0 \quad (3)$$

$$\Rightarrow V_D(1-j) = 6$$

$$V_D = \frac{6(1+j)}{1-j(1+j)} = 3+3j$$

KCL at node C: $\frac{-V_D}{j3} + 2I_x + I_N = 0$


$$\frac{-V_D}{j3} + \frac{2V_D}{3} + I_N = 0 \quad (3)$$

$$I_N = -\frac{V_D(2+j)}{3} = -\frac{(3+3j)(2+j)}{3} = -(1+j)(2+j)$$

$$I_N = -2 - 3j + 1 = -1 - 3j = 3.16 \cdot e^{-j1.89} \text{ A}$$

$$i_N(t) = 3.16 \cdot \cos(1000t - 1.89) \text{ A}$$

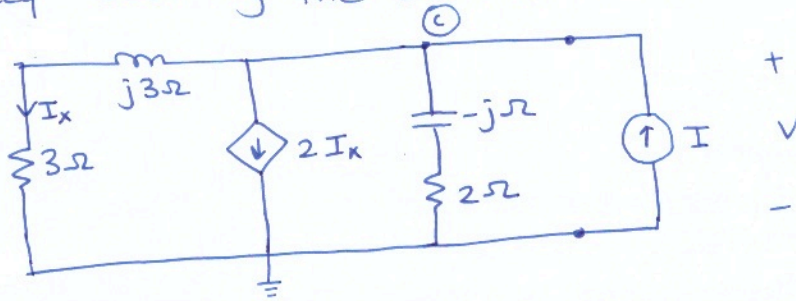c) Find z_{eq} seen by the load. Kill independent sources.



$$I_x = \frac{V_c}{3+3j}, \quad V_c = V, \quad z_{eq} = \frac{V}{I}$$

KCL at c: $\frac{V}{3+3j} + 2 \cdot I_x + \frac{V}{2-j} - I = 0$


$$\frac{V}{3+3j} + \frac{2V}{3+3j} + \frac{V}{2-j} - I = 0$$

$$\frac{V}{1+j} + \frac{V}{2-j} = I$$


$$V \cdot \frac{3}{3+j} = I \Rightarrow z_{eq} = \frac{V}{I} = \frac{3+j}{3} = \boxed{1 + \frac{j}{3} \Omega}$$

For maximum power trans for: $\boxed{z_L = z_{eq}^* = 1 - \frac{j}{3} \Omega}$

Overall circuit is

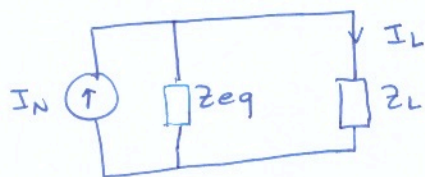

convert
to Thevenin

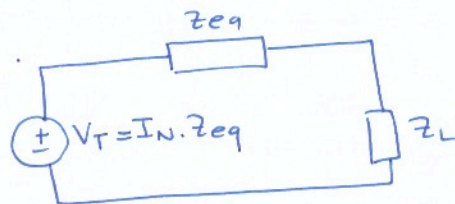

$$V_T = I_N \cdot z_{eq} = (-1-3j) \left(1 + \frac{j}{3}\right) = -1 + 1 - 3j - \frac{j}{3} = -\frac{10j}{3}$$

Then,

$$P_L = \frac{|V_T|^2}{8R_L} = \frac{\left(\frac{10}{3}\right)^2}{8 \cdot 1} = \boxed{1.39 \text{ W}} = \frac{25}{18} \text{ W}$$