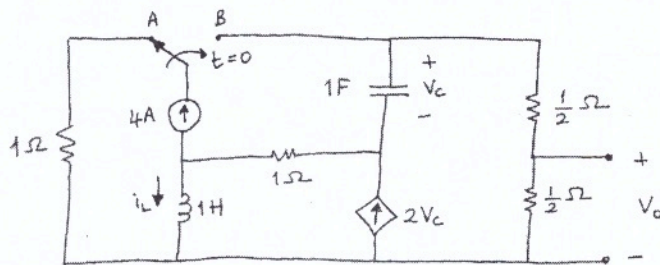


FALL 2016-2017, EEE-202
— FINAL EXAM SOLUTIONS —


Question 1. [25 points]

Consider the following circuit. The switch is kept in position A for a very long time, and moved to position B at $t = 0$.

- Find the values of $i_L(0^-)$ and $v_C(0^-)$.
- Find a second-order differential equation for v_C for $t \geq 0$.
- Using the result from part (b), find $v_C(t)$. Then, find $v_o(t)$.



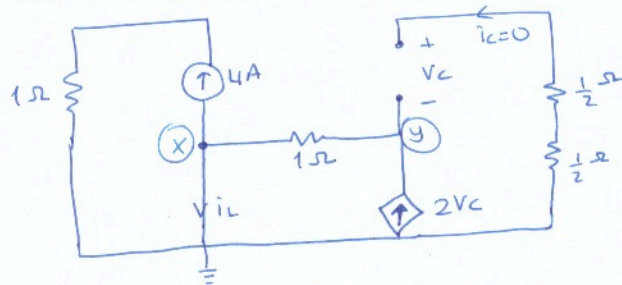a) at $t=0^-$, the circuit looks like the following:



$$v_x = 0$$

$$v_y = -v_C$$


$$\text{KCL at } x: 4 + i_L - 2v_C \Rightarrow 4 + i_L + 2v_y = 0$$

$$\text{KCL at } y: \frac{v_y}{1} - 2v_C = 0 \Rightarrow 3v_y = 0 \Rightarrow v_y = 0$$

So, $v_C(0^-) = 0V$

$i_L(0^-) = -4A$

b) After $t=0$

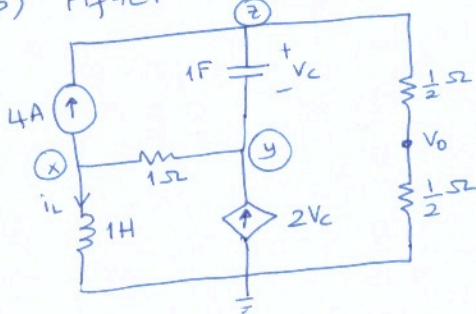

$$\text{KCL at } x: (v_x = L \dot{i}_L)$$

$$i_L + \frac{\dot{i}_L - v_y}{1} + 4 = 0$$

$$\text{KCL at } y:$$

$$v_y - i_L - 2v_C - \dot{v}_C = 0$$

$$\text{KCL at } z:$$

$$\frac{v_y + v_C}{1} + \dot{v}_C - 4 = 0$$

$$i_L = \dot{v}_C + 2v_C - 4$$

$$\downarrow$$

$$\dot{i}_L = \ddot{v}_C + 2\dot{v}_C$$

$$v_C + \dot{v}_C - 4 + \dot{i}_L + 2v_C + \dot{v}_C = 0$$

$$2\dot{v}_C + 3v_C - 4 + \dot{i}_L = 0$$

$$2\dot{v}_C + 3v_C - 4 + \ddot{v}_C + 2\dot{v}_C = 0$$

$$\ddot{v}_C + 4\dot{v}_C + 3v_C = 4$$

c) Characteristic polynomial:

$$s^2 + 4s + 3 = 0$$

$$(s+1)(s+3) = 0 \Rightarrow s_1 = -1, s_2 = -3$$

$$v_N(t) = k_1 e^{-t} + k_2 e^{-3t} \quad (\text{natural response})$$

* Forced response: $v_F = A \Rightarrow$ insert into DDE: $3A = 4 \Rightarrow A = \frac{4}{3} = v_F$

So, $v_C(t) = v_N(t) + v_F = k_1 e^{-t} + k_2 e^{-3t} + \frac{4}{3} V$

* Now use initial conditions.

$$V_c(0^-) = V_c(0) = 0 \Rightarrow \boxed{K_1 + K_2 + \frac{4}{3} = 0}$$

* Using $i_L = \dot{V}_c + 2V_c - 4$ and $i_L(0^-) = i_L(0) = -4A$ $\left\{ \begin{array}{l} i_L(0) = \dot{V}_c(0) + 2V_c(0) - 4 = -4 \\ \dot{V}_c(0) = 0 \end{array} \right.$

$$\dot{V}_c(t) = -K_1 e^{-t} - 3K_2 e^{-3t}$$

$$\dot{V}_c(0) = -K_1 - 3K_2 = 0 \Rightarrow \boxed{K_1 = -3K_2}$$

then,

$$-3K_2 + K_2 + \frac{4}{3} = 0 \Rightarrow$$

$$\boxed{K_2 = \frac{2}{3}, K_1 = -2}$$

So,

$$\boxed{V_c(t) = -2e^{-t} + \frac{2}{3}e^{-3t} + \frac{4}{3} \text{ V}}$$

(check i.c. $V_c(0) = -2 + \frac{2}{3} + \frac{4}{3} = 0$ o.k.)

+ From voltage divider, $V_o = \frac{V_z}{2}$

KCL at z :


$$\frac{V_z}{1} + \dot{V}_c - 4 = 0 \Rightarrow V_o(t) = \frac{4 - \dot{V}_c}{2}$$

$$= \frac{4 - (-2e^{-t} - 2e^{-3t})}{2}$$


$$\boxed{V_o(t) = 2 - e^{-t} + e^{-3t} \text{ V}}$$

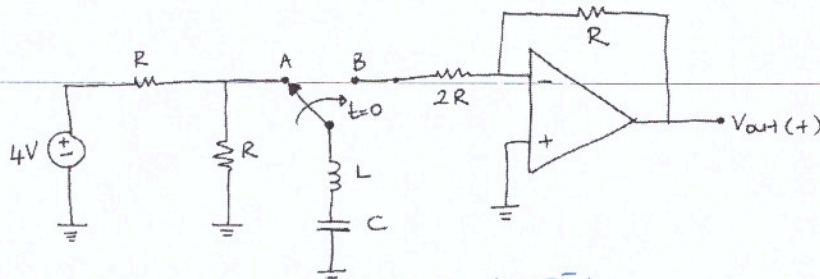Question 2. [25 points]

Consider the circuit below. The OPAMP is ideal and operating in linear mode. $R = 4\Omega$, $L = 6H$ and $C = 0.5F$. The switch is kept in position A for a very long time, and moved to position B at $t = 0$. Using Laplace-domain circuit analysis, find $v_o(t)$.




* Find initial conditions at $t=0^-$:

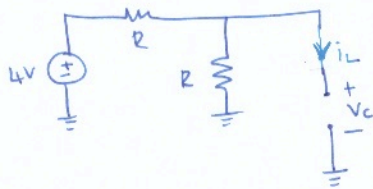

$$i_L(0^-) = 0$$

$$v_c(0^-) = 4 \cdot \frac{R}{R+R} = 2V \quad (\text{voltage divider})$$

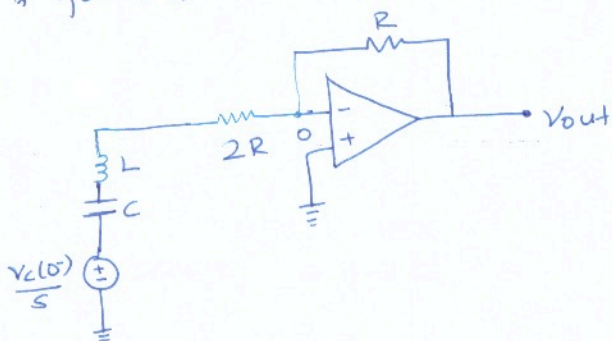* for $t \geq 0$, initial condition transformation simplifies the analysis:



$$v_+ = v_- = 0$$

KCL at (-) input of OPAMP

$$\frac{0 - \frac{v_c(0^-)}{s}}{2R + sL + \frac{1}{sC}} + \frac{0 - v_{out}}{R} = 0$$

$$v_{out} = R \cdot \frac{-\frac{v_c(0^-)}{s} \cdot sC}{s^2LC + 2sRC + 1} = \frac{-v_c(0^-)RC}{s^2LC + 2sRC + 1}$$

$$v_{out}(s) = \frac{-4}{3s^2 + 4s + 1}$$

* Use partial fraction expansion:

$$v_{out} = \frac{-4}{(3s+1)(s+1)} = \frac{-4}{3(s+\frac{1}{3})(s+1)} = \frac{k_1}{s+\frac{1}{3}} + \frac{k_2}{s+1}$$

$$k_1 = \left(s + \frac{1}{3}\right) \cdot v_{out} \Big|_{s=-\frac{1}{3}} = \frac{-4}{3(s+1)} \Big|_{s=-\frac{1}{3}} = -2$$

$$k_2 = (s+1) \cdot v_{out} \Big|_{s=-1} = \frac{-4}{3(s+\frac{1}{3})} \Big|_{s=-1} = 2$$

* So,

$$v_{out}(t) = \left[-2 \cdot e^{-\frac{1}{3}t} + 2e^{-t}\right] \cdot u(t) \quad \text{Volts}$$


Question 3. [25 points]

Consider the following circuit. Assume zero initial conditions. Here, the block given by $H(s)$ represents a linear circuit and $H(s) = \frac{V_o(s)}{V_{in}(s)}$.

a) What is $H(s)$ if the unit step response of the circuit is $v_o(t) = [9 - 10e^{-t} + e^{-10t}] u(t)$?
Hint: Unit step response is the output when the input is the unit step function.

b) Find $v_o(t)$ if the input is given as $v_{in}(t) = 3e^{-t}u(t)$ V.

c) Using asymptotic lines, draw the Bode plot of $|H(j\omega)|$ in logarithmic scale for the transfer function found in part (a). Mark all important frequency points and denote all slopes.

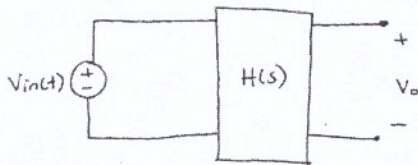

$$\text{a) } V_{in}(s) = \frac{1}{s}$$

$$V_{out}(s) = \frac{9}{s} - \frac{10}{s+1} + \frac{1}{s+10} = \frac{9(s^2+11s+10) - 10(s^2+10s) + s^2+s}{s(s+1)(s+10)} = \frac{90}{s(s+1)(s+10)}$$

$$H(s) = \frac{V_{out}(s)}{V_{in}(s)} = \boxed{\frac{90}{(s+1)(s+10)}}$$

$$\text{b) } V_{in}(s) = \frac{3}{s+1} \Rightarrow V_{out}(s) = H(s) \cdot V_{in}(s) = \frac{270}{(s+1)^2(s+10)}$$

$$= \frac{k_{11}}{(s+1)^2} + \frac{k_{12}}{s+1} + \frac{k_2}{s+10}$$

$$k_{11} = V_{out} \cdot (s+1)^2 \Big|_{s=-1} = \frac{270}{s+10} \Big|_{s=-1} = 30$$

$$k_{12} = \frac{d}{ds} \left\{ V_{out} \cdot (s+1)^2 \right\} \Big|_{s=-1} = \frac{d}{ds} \left(\frac{270}{s+10} \right) \Big|_{s=-1} = -\frac{270}{(s+1)^2} \Big|_{s=-1} = -\frac{10}{3}$$

$$k_2 = V_{out} \cdot (s+10) \Big|_{s=-10} = \frac{270}{(s+1)^2} \Big|_{s=-10} = \frac{10}{3}$$



$$\boxed{V_{out}(t) = \left[30 t \cdot e^{-t} - \frac{10}{3} e^{-t} + \frac{10}{3} e^{-10t} \right] u(t)}$$

$$\text{c) } H(j\omega) = \frac{90}{(j\omega+1)(j\omega+10)} = \frac{9}{(1+j\omega)(1+j\frac{\omega}{10})}$$

$$|H(j\omega)| = \frac{9}{\sqrt{1+\omega^2} \sqrt{1+(\frac{\omega}{10})^2}}$$




$$20 \log_{10} |H(j\omega)| = \underbrace{20 \log_{10} 9}_{\approx 19 \text{ dB}} + 20 \log_{10} \left(\frac{1}{\sqrt{1+\omega^2}} \right) + 20 \log_{10} \left(\frac{1}{\sqrt{1+(\frac{\omega}{10})^2}} \right)$$

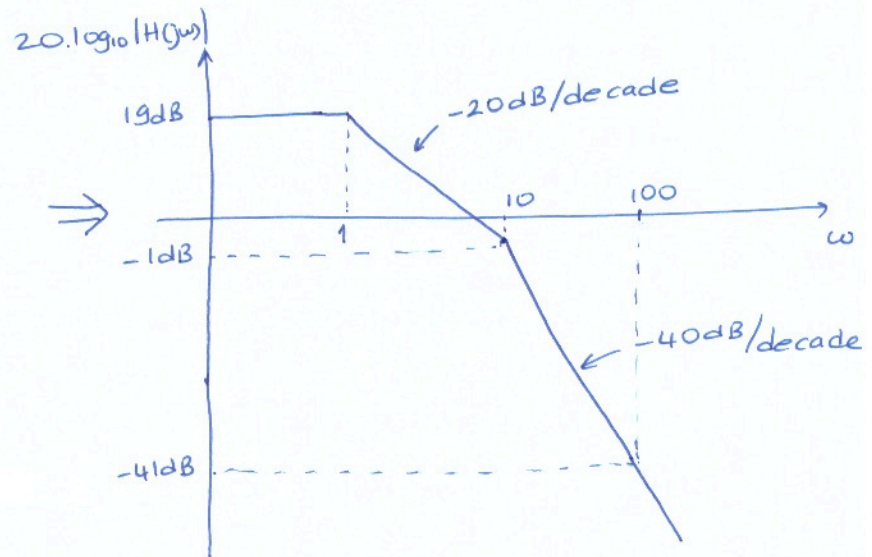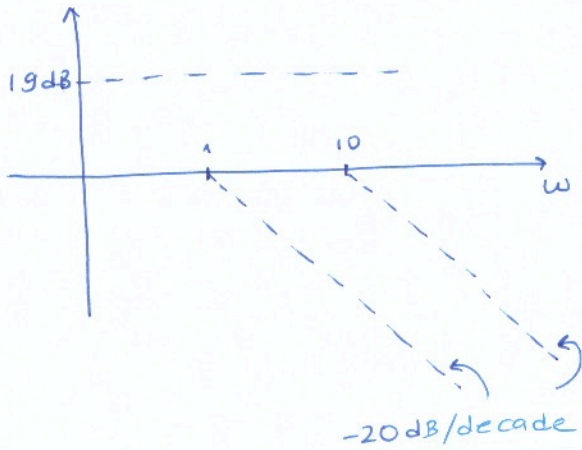

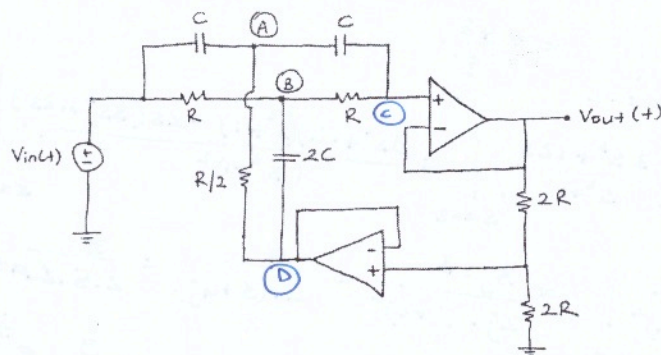Question 4. [25 points]

Consider the circuit below. All OPAMPs are ideal and operating in linear mode. Assume zero initial conditions for all voltages and currents. This circuit represent an implementation of a band-stop filter.

- Find the transfer function in s-domain, $H(s) = \frac{V_{out}(s)}{V_{in}(s)}$, as a function of R and C.
- Check that you found a band-stop filter in part (a). What is the center frequency of the stop-band, in terms of R and C?
- Assume that $R = 2\Omega$ and $C = 0.25F$. Find the output voltage $v_{out}(t)$ if $v_{in}(t) = 3 \cos(t) u(t)$ Volts, where $u(t)$ is the unit step function.
- Assume that the circuit is in sinusoidal steady state. Using phasor analysis and your answer from part (a), find $v_{out}(t)$ if $v_{in}(t) = 3 \cos(t)$ Volts. Is this result consistent with what you found in part (c)?



$V_+ = V_-$ for the OPAMPs.

$$V_C = V_{out}$$

$$V_D = \frac{V_{out} + 2R}{2R + 2R} = \frac{V_{out}}{2}$$

a) KCL at A: $(V_A - V_{in})sC + (V_A - \frac{V_{out}}{2}) \cdot \frac{2}{R} + (V_A - V_{out})sC = 0$

$$V_A(sRC + 2 + sRC) - V_{in} \cdot sRC - V_{out}(1 + sRC) = 0$$

$$V_A = \frac{V_{in} \cdot sRC + V_{out}(1 + sRC)}{2 + 2sRC}$$

KCL at B: $\frac{V_B - V_{in}}{R} + \frac{V_B - V_{out}}{R} + (V_B - \frac{V_{out}}{2}) \cdot 2sC = 0$

$$V_B(2 + 2sRC) - V_{in} - V_{out}(1 + sRC) = 0$$

$$V_B = \frac{V_{in} + V_{out}(1 + sRC)}{2 + 2sRC}$$

KCL at C: $\frac{V_{out} - V_B}{R} + (V_{out} - V_A)sC = 0$

$$V_{out}(1 + sRC) - V_B - V_A \cdot sRC = 0$$

$$V_{out}(1 + sRC) - \frac{[V_{in} + V_{out}(1 + sRC)]}{2 + 2sRC} - \frac{[V_{in} \cdot sRC + V_{out}(1 + sRC)] \cdot sRC}{2 + 2sRC} = 0$$

$$V_{out} \left[2 + 4sRC + 2s^2R^2C^2 - 1 - sRC - sRC - s^2R^2C^2 \right] = V_{in} \left[1 + s^2R^2C^2 \right]$$


$$H(s) = \frac{V_{out}}{V_{in}} = \frac{1 + s^2R^2C^2}{1 + 2sRC + s^2R^2C^2} = \frac{1 + s^2R^2C^2}{(1 + sRC)^2}$$

$$b) H(j\omega) = \frac{1 + (j\omega RC)^2}{(1 + j\omega RC)^2} = \frac{1 - \omega^2 R^2 C^2}{(1 + j\omega RC)^2}$$

$$|H(j\omega)| = \frac{|1 - \omega^2 R^2 C^2|}{1 + \omega^2 R^2 C^2} \Rightarrow \text{at } \omega_0 = \frac{1}{RC}, |H(j\omega_0)| = 0$$

$$\text{at } \omega = 0, |H(j\omega)| = 1$$

$$\text{at } \omega \rightarrow \infty, |H(j\omega)| = 1$$

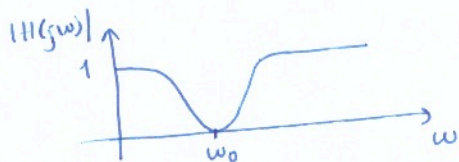

So, this is a band-stop filter.

$$c) R = 2\Omega, C = 0.25F \Rightarrow H(s) = \frac{1 + s^2/4}{(1 + s/2)^2} = \frac{s^2 + 4}{s^2 + 4s + 4}$$

$$V_{in} = \frac{3s}{s^2 + 1} \Rightarrow V_{out} = H(s) \cdot V_{in} = \frac{3s(s^2 + 4)}{(s^2 + 1)(s^2 + 4s + 4)} = \frac{3s(s^2 + 4)}{(s + j)(s - j)(s + 2)^2}$$

$$= \frac{k_1}{(s + 2)^2} + \frac{k_2}{s + 2} + \frac{k}{s - j} + \frac{k^*}{s + j}$$

$$k_1 = V_{out} \cdot (s + 2)^2 \Big|_{s = -2} = \frac{3s(s^2 + 4)}{s^2 + 1} \Big|_{s = -2} = -\frac{48}{5}$$

$$k_2 = \frac{d}{ds} \left(V_{out} \cdot (s + 2)^2 \right) \Big|_{s = -2} = \frac{d}{ds} \left(\frac{3s^3 + 12s}{s^2 + 1} \right) \Big|_{s = -2} = \frac{(9s^2 + 12)(s^2 + 1) - 2s(3s^3 + 12s)}{(s^2 + 1)^2} \Big|_{s = -2} = \frac{48}{25}$$

$$k = V_{out}(s - j) \Big|_{s = j} = \frac{3s(s^2 + 4)}{(s + j)(s + 2)^2} \Big|_{s = j} = \frac{3j \cdot 3}{2j \cdot (j + 2)^2} = \frac{9}{2 \cdot (3 + 4j)} = \frac{9}{2 \cdot 5 \cdot \angle \tan^{-1}(4/3)} = \frac{9}{10} \cdot e^{-j \cdot \tan^{-1}(4/3)}$$

So,

$$V_{out}(t) = \left[\underbrace{-\frac{48}{5} \cdot t \cdot e^{-2t}}_{\text{transient response}} + \underbrace{\frac{48}{25} \cdot e^{-2t}}_{\text{steady-state response}} + \frac{9}{5} \cdot \cos\left(t - \tan^{-1}\left(\frac{4}{3}\right)\right) \right] \cdot u(t) \text{ Volts}$$

0.93 rad, OR 53°

$$d) H(j\omega) = \frac{4 - \omega^2}{-\omega^2 + 4j\omega + 4}, \text{ at } \omega = 1 \Rightarrow H(j) = \frac{3}{3 + 4j}$$

$$V_{in} = 3, \quad V_{out} = H(j) \cdot V_{in} = \frac{9}{3 + 4j} = \frac{9}{5} e^{-j \cdot \tan^{-1}(4/3)}$$

$$V_{out}(t) = \frac{9}{5} \cdot \cos\left(t - \tan^{-1}\left(\frac{4}{3}\right)\right) \text{ Volts}$$

This result is consistent with part (c). Phasor analysis does not give the transient response, but only gives the steady-state response. So, as $t \rightarrow \infty$, the result in (c) converges to the result in (d), as $t \cdot e^{-2t}$ and e^{-2t} terms converge to zero.