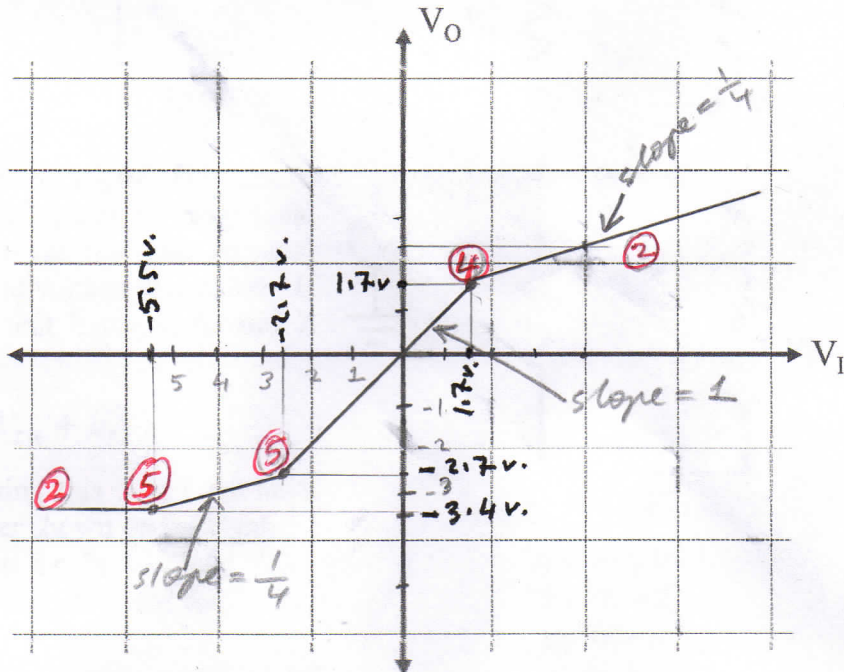
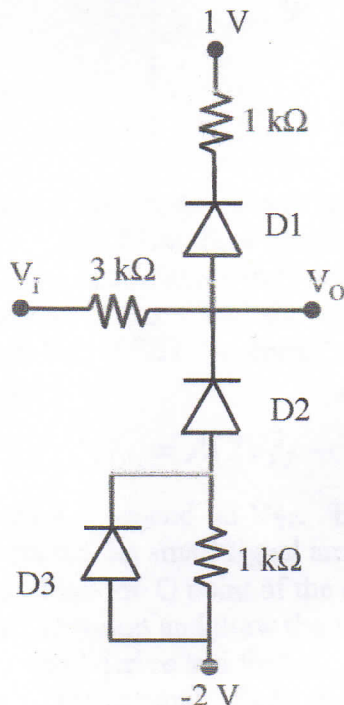


1. (20 points)

For the below circuit, the diodes are ideal with a turn on voltage of $V_{ON}=0.7V$. Find and plot V_O vs V_I for $-8V < V_I < 8V$ in the provided graph template. Calculate and clearly indicate all critical voltage values and verify the states of the diodes.

Hint: When $V_I = -8V$, assume D1 is OFF, and D2 and D3 are ON. D3 turns off when $I_{D3} < 0$.



$V_I = -8V$

$$i_{D2} = \frac{-2 - 0.7 - 0.7 - (-8)}{3k} = 1.13 \text{ mA} > 0 \quad \text{②}$$

$$i_{D3} = i_{D2} - \frac{0.7}{1} = 1.13 - 0.7 = 0.43 \text{ mA} > 0 \quad \checkmark$$

As V_I is increased D3 turns OFF

When $i_{D3} = 0 = \frac{-2 - 0.7 - 0.7 - V_I}{3} - 0.7$

$$0 = \frac{-3.4 - V_I}{3} - 0.7 \Rightarrow V_I = -3.4 - 2.1 = -5.5V$$

$V_{out} = -2 - 0.7 - 0.7 = -3.4V$

$V_I = -5.5 \Rightarrow i_{D2} = \frac{-3.4 - (-5.5)}{3} = 0.7 \text{ mA} > 0 \quad \checkmark$

$V_I > -5.5$

$$i_{D2} = \frac{-2 - 0.7 - V_I}{4} = \frac{-2.7 - V_I}{4}$$

$$V_{out} = V_I + 3\left(\frac{-2.7 - V_I}{4}\right) = \frac{V_I}{4} - 2.025$$

This continues until $I_{D2} = 0$

$$0 = \frac{-2.7 - V_I}{4} \Rightarrow V_I = -2.7$$

when $V_{out} = \frac{-2.7}{4} - 2.025 = -2.7$

$V_I > -2.7$ D2, D3 and D1 are OFF

$V_{out} = V_I$ until $V_I = 1 + 0.7 = 1.7$

$$I_1 = \frac{V_I - 0.7 - 1}{4} = \frac{V_I}{4} - \frac{1.7}{4}$$

$$V_{out} = V_I - 3\left(\frac{V_I}{4} - \frac{1.7}{4}\right) = \frac{V_I}{4} + 1.275$$

e.g. $V_I = 4 \Rightarrow V_{out} = 2.275V$
 $(V_I = 8 \Rightarrow V_{out} = 3.275V)$

Student ID: